

75 cents


hcr

focus
on
communications
technology . . .

ham radio

magazine

APRIL 1973

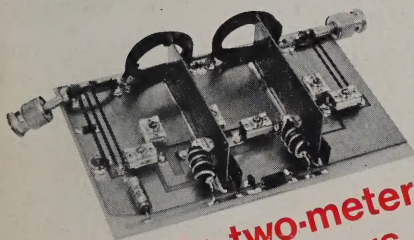

**solid-state two-meter fm
rf power amplifiers**



this month

- vertical antenna 16
- ssb generator 22
- phase-angle meter 28
- printed circuit boards 58

Savoy

HIGH ACCURACY CRYSTALS
FOR OVER 30 YEARS



TYPE 900A

\$3.75

Postpaid in U.S.A.



TYPE 901

Either type for amateur VHF in Regency, Swan, Standard, Drake, Varitronics, Tempo, Yaesu, Galaxy, Trio, Sonar, Clegg, SBE, transmitter or receiver. GE, Motorola, RCA or Oven use \$4.95. Quotes on others.

Specify crystal type, frequency, make of equipment and whether transmit or receive when ordering.



BASSETT VACUUM TRAP ANTENNA SYSTEM

Complete packaged multi-band antenna systems employing the famous Bassett Sealed Resonators and Balun from which air has been removed and replaced with pure helium at one atmosphere. Operating bands are indicated by model designation.

MODEL DGA-4075	\$59.50
MODEL DGA-204075	..	\$79.50
MODEL DGA-2040	\$59.50
MODEL DGA-152040	..	\$79.50

BASSETT VACUUM BALUN



The famous sealed helium filled Balun . . . employed with the DGA Series Antenna Systems. Solderless center insulator and easily handles more than full legal power while reducing unwanted coax radiation. Equipped with a special SO-239 type coax connector and available either 1:1 or 4:1.

MODEL DGA-2000-B . . . \$12.95
Postpaid in U.S.A.

CONTACT YOUR DISTRIBUTOR OR WRITE FOR DATA

Savoy Electronics, Inc.

P.O. Box 7127 - Fort Lauderdale, Florida - 33301

Tel: 305-566-8416 or 305-947-1191



- LOAFS AT CONTINUOUS MAXIMUM LEGAL POWER IN ANY MODE
- DRIVES EASILY WITH ANY POPULAR EXCITER OR TRANSCEIVER
- KEEPS YOUR SIGNAL CLEAN, CRISP, AND OUTSTANDING
- CHANGES BANDS FAST – WITHOUT 'CUT-AND-TRY' TUNE-UP
- STAYS COOL AND WHISPER-QUIET UNDER THE HARDEST USE
- CARRIES THE INDUSTRY'S MOST EXTENSIVE WARRANTY, BACKED BY ETO'S RENOWNED *FAST FACTORY SERVICE*

ETD

april 1973 **hr** 1

It's fun to build quality.



IC-2009
92^{50*}



IC-2108
79^{95*}

Two new Heathkit Calculators.

At left is the totally new Heathkit IC-2009. It's first a self-contained portable, weighing in at 11 oz. and small enough to fit in your coat pocket. But it's a desk-top calculator, too. The internal Nickle-Cadmium battery gives five to eight hours use between charges. Or, the IC-2009 can be left connected to its charger for indefinite operation. And unlike other pocket calculators, the Heathkit IC-2009 is designed to be maintained by you. Plug-in keyboard and display boards, plus a complete troubleshooting section in the manual make it easy — and economical. Add up the features for yourself: 8-digit capacity. Four arithmetic functions. Full floating decimal. Constant key. Chain calculation capability. Clear entry key. Entry and total overflow indicators. Negative answer indicator. Battery-saver circuitry. Low battery indicator. Tactile-feedback keyboard for positive entry indication. Order your IC-2009 now. You'll have it built in two or three evenings. Mailing weight, 3 lbs.

The Heathkit IC-2108 on the right features a sleek, low-profile case with bright 1/2" read-

out tubes in an 8-digit display — one of the largest, most legible in the industry. The color-coded keyboard is human engineered to slope down to the desk so you can rest your arm while using. And the IC-2108 is loaded with features: Four arithmetic functions. Floating and fixed decimal. Constant key. Chain calculation capability. Clear display key. Entry and result overflow indicators. Negative number indicator. 120/240 VAC operation. In addition, the IC-2108 is amazingly simple to build. Two spare evenings will do it. 4 lbs. mailing weight.

HEATH Schlumberger	
HEATH COMPANY, Dept. 122-4 Benton Harbor, Michigan 49022	
<input type="checkbox"/> Please send FREE Heathkit Catalog.	
<input type="checkbox"/> Enclosed is \$_____, plus shipping	
Please send model(s)_____	
Name_____	
Address_____	
City_____	State_____ Zip_____
*Mail order prices; F.O.B. factory. GX-275R	

April, 1973
volume 6, number 4

staff

James R. Fisk, W1DTY
editor

Patricia A. Hawes, WN1QJN
editorial assistant

Nicholas D. Skeer, K1PSR
vhf editor
J. Jay O'Brien, W6GDO
fm editor

Alfred Wilson, W6NIF
James A. Harvey, WA6IAK
associate editors

Wayne T. Pierce, K3SUK
cover

T.H. Tenney, Jr. W1NLB
publisher

Hilda M. Wetherbee
assistant publisher
advertising manager

offices

Greenville, New Hampshire 03048
Telephone: 603-878-1441

ham radio magazine is
published monthly by
Communications Technology, Inc
Greenville, New Hampshire 03048

Subscription rates, world wide
one year, \$7.00, three years, \$14.00
Second class postage
paid at Greenville, N.H. 03048
and at additional mailing offices

Foreign subscription agents
United Kingdom
Radio Society of Great Britain
35 Doughty Street, London WC1, England

All European countries
Eskil Persson, SM5CJP, Frotunagrand 1
19400 Upplands Vasby, Sweden

African continent
Holland Radio, 143 Greenway
Greenside, Johannesburg
Republic of South Africa

Copyright 1973 by
Communications Technology, Inc
Title registered at U.S. Patent Office
Printed by Wellesley Press, Inc
Framingham, Massachusetts 01701, USA

ham radio is available to the blind
and physically handicapped on magnetic tape
from Science for the Blind
221 Rock Hill Road, Bala Cynwyd
Pennsylvania 19440
Microfilm copies of current
and back issues are available
from University Microfilms
Ann Arbor, Michigan 48103

Postmaster: Please send form 3579 to
ham radio magazine, Greenville
New Hampshire 03048

hr

ham
radio
magazine

contents

6 two-meter rf power amplifiers

Arthur R. Hall, W4CGC

16 the vertical radiator

John R. True, W4OQ

22 phasing-type ssb generator

Worthie Doyle, W7CMJ

28 phase-angle meter

R. G. Brearley, VE2AYU

Werner H. Korth

38 sensitive rf indicator

David L. Sprague, WB9DNI

42 www receiver

Courtney Hall, WA5SNZ

48 alaskan wireless

Edmund H. Marriner, W6BLZ

58 printed-circuit boards

A. A. Kelley, K4EEU

68 morse code speed standards

Gaspard Lizee, VE2ZK

4 a second look

110 advertisers index


72 comments

99 flea market

70 ham notebook

74 new products

110 reader service

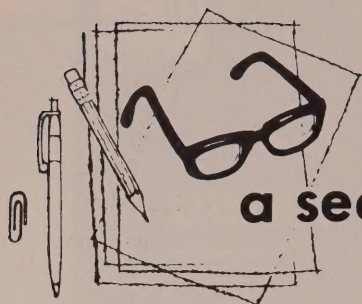

a second look

by **jim
fisk**

Although any amateur who has worked on the high-frequency or vhf bands knows that geomagnetic storms can raise havoc with radio propagation, new evidence indicates that these same geomagnetic storms are linked to changes in our weather.

Upper air circulations over the Gulf of Alaska, which subsequently affect the weather over the North American continent, tend to become more intense after a period of severe geomagnetic disturbance. Although evidence of this phenomenon was reported over ten years ago, it's only been within the past couple of years that the subject has received serious study by scientists from the National Oceanic and Atmospheric Administration (NOAA) and the University Corporation for Atmospheric Research, both in Boulder, Colorado.

The studies to date have been based primarily on statistical studies — the number of high-altitude storms that follow a period of geomagnetic disturbance as opposed to the number of high-altitude storms following non-geomagnetic storm periods. Although the studies are far from complete, all evidence so far points to increased high-altitude storm activity 5 days to a week after a geomagnetic disturbance. If more can be learned about this storm intensification, it may provide a valuable new tool for increasing the accuracy of the 3- to 5-day weather predictions in the United States and Canada.

Although the cause and effect of geomagnetic storm intensification is not yet clearly understood, scientists speculate that it may result from geomagnetic


modulation of the heat radiated to space from the relatively warm Alaskan Gulf during the winter. This may trigger the formation of cirrus clouds, change the ozone content, and result, possibly, in increased thunderstorm activity.

Satellite infrared data which indicates such changes during the winter of 1971/1972 are now being studied to test the idea of geomagnetic control of cirrus clouds, but further work is necessary. However, the study may provide important clues to the physical process by which the miniscule direct energy inputs from geomagnetic activity in the lower stratosphere can cause such large weather patterns that affect millions of people on the North American continent.

Once the mechanism of this phenomenon has been clearly understood, it suggests a possible way in which man might deliberately (or inadvertently) modify large-scale high-altitude air circulation, and hence, the weather. Controlling the weather, like flying and space exploration, has long been among man's fondest dreams. All it may take is a small amount of man-made magnetic energy, in the right amount and in the right place.

If all this comes to pass I can see it now — the skiers will be lobbying for snow, the golfers will be lobbying for sunshine, and ecologists will be asking for moderation. More important to amateurs, perhaps, is that if geomagnetics can be used to control the weather, perhaps the same sort of technique can be used to improve long-distance radio propagation during periods of sunspot minimums.

Jim Fisk, W1DTY
editor

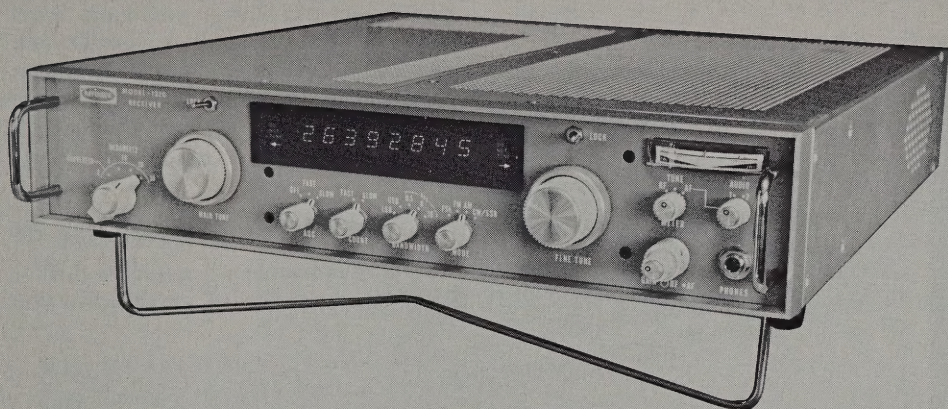

RAYTHEON

**MODEL - 1230
RECEIVER**

THE NEW STANDARD OF RECEIVER EXCELLENCE

- **SYNTHESIZER STABILITY**

(Better than 1 Hz/day at any freq.)

- **CONTINUOUS TUNING (2-30 MHz)**

- **TRACKED PRE-SELECTION ON ALL BANDS**

- **DIRECT DIGITAL READOUT TO NEAREST Hz**

- **PHASE LOCKED DETECTORS FOR AM, FM, FSK**

- **INDEPENDENT SIDEBAND AVAILABLE**


- **ALL SOLID STATE including DISPLAYS**

\$3930

FOR MORE INFORMATION WRITE TO:

RAYTHEON COMPANY

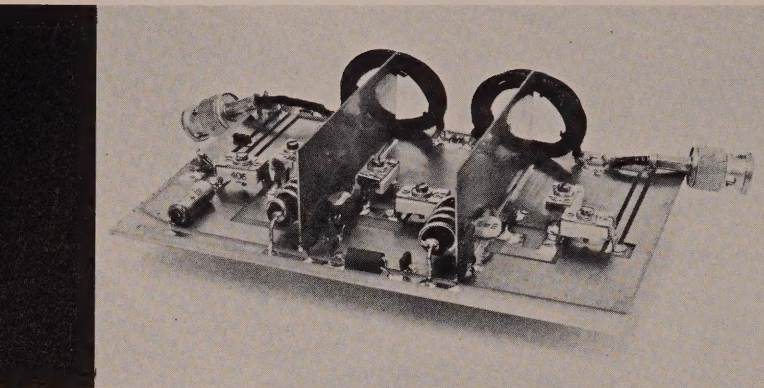MARKETING DEPT. (SPI)
P.O. BOX 1542
GOLETA, CALIFORNIA 93017
AREA CODE 805 967-5511



solid-state two-meter fm rf power amplifiers

Complete design and
construction details
for solid-state
power amplifiers for
two-meter fm

This article describes three solid-state vhf power amplifiers designed for use on two-meter fm. Since many of the fm transceivers now in use are in the one-watt class, such as the Drake TR-22, Motorola HT-220, and some Standard sets, I felt that the greatest need for more

Arthur R. Hall, W4CGC, Woodburn Road, Annandale, Virginia

power would be from the one-watt level to approximately 30 to 35 watts, a power gain of approximately 15 dB. However, some readers are interested in somewhat higher input power ranges, so I have included basic designs for 1-watt in, 10-watts out, and 10-watts in, 35-watts out. Design and construction details, and tune-up procedures are the same as the 1-watt in, 35-watts out amplifier discussed in detail in the text.

Undoubtedly, more amateurs would attempt to build their own power amplifier if they could be assured of success upon completion of the project. With this in mind, I have included several design features that will greatly assist in realizing this goal, including the use of printed circuit inductances, a built-in vswr and relative power indicator to aid in tune-up and operation, and the use of state-of-the-art, high efficiency, rugged, yet low cost transistors. The manufacturer rates these transistors for *infinite* vswr, so you shouldn't burn them out if your antenna isn't what it's supposed to be.


Although it will not be necessary for the builder to do any design work on these amplifiers, I will provide a short dissertation on the basic needs and techniques in dealing with high-power vhf transistor circuit design. I will also go through the complete procedure for designing the 1-watt input/35-watt output amplifier.

35-watt power amplifier

This amplifier is a two-stage solid-state unit with 30 to 35 watts output in the

switching network developed by WB4-JMD and WB4DRB, and described previously.²

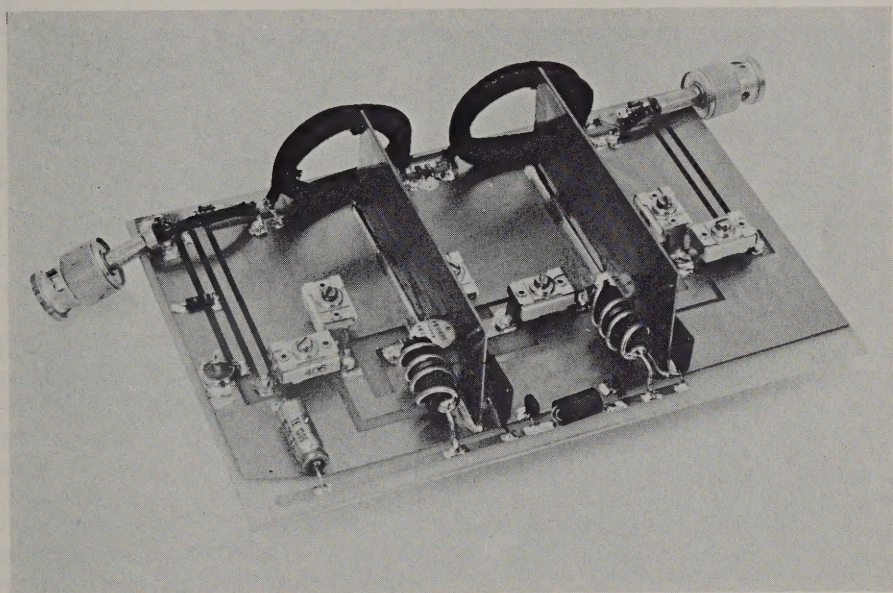The theory of operation of this switching network is as follows: In the receive mode all six diodes are non-conducting and, as such, present high resistance blockage paths. When an incoming signal appears at the output of the amplifier, CR5 and CR6 block the received signal from entering the output circuit of the amplifier. The signal travels through the two quarter wave RG-174/U coaxial lines



The solid-state two-meter power amplifier printed-circuit board includes etched inductors for both stages as well as a built-in swr bridge (upper left). Transmit-receive switching is accomplished with the two coiled quarter-wave lines at the rear of the board.

146- to 148-MHz range when driven by 1 to 1.5 watts input. The 1-watt input is amplified to approximately 10 watts by the first stage, a SD-1198 transistor. This stage drives the final, a SD-1197 transistor, to approximately 35 watts output (depending upon how hot the transistors are). The output power passes through a vswr/relative power indicator printed on the board similar to the units described in a previous article.¹ From there it passes through two switching diodes to the output jack. The switching diodes are part of an automatic TR

to the input jack of the amplifier. Since CR3 and CR4 are non-conducting they do not affect the passing signal. Since CR1 and CR2 are likewise non-conducting, the signal is thus prevented from entering the input stage of the amplifier.


In the transmit mode, all six diodes are in conduction. Diodes CR3 and CR4 present a near short circuit to ground at the junction point of the two quarter-wave lines. Since a shorted quarter-wave line on one end looks like an open circuit on the other end, the line presents a very high impedance to the incoming driving

power. Diodes CR1 and CR2 are now biased into conduction and pass the driving power to the amplifier input stage relatively unobstructed. CR5 and CR6 pass the amplified power from the output stage to the output jack. Again, CR3 and CR4 perform the same function as in the input circuit and short out the output quarter-wave line, blocking the output power signal.

Since the amplifier is zero biased and displays excellent immunity to spurious

vhf power transistors offer a good combination of reasonable cost and rugged construction while maintaining high performance in the power range of one watt in, 30 watts out.

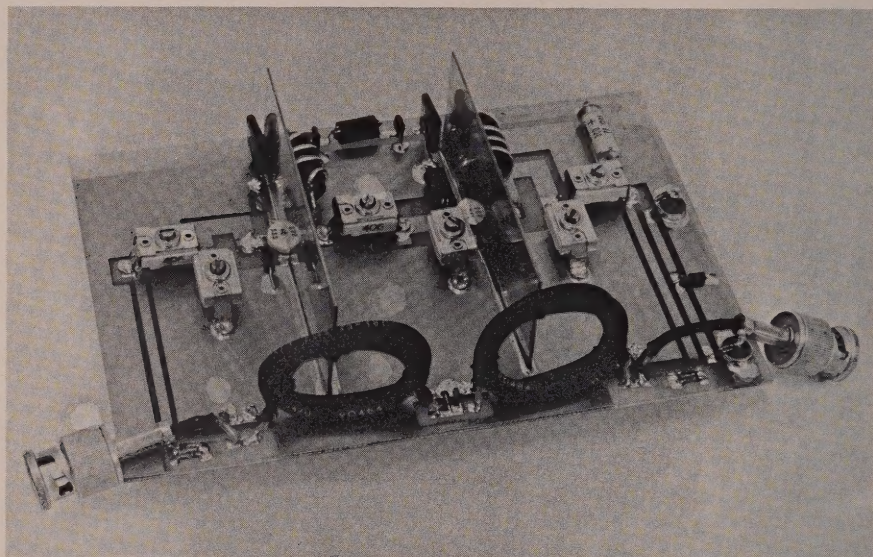After the determination has been made to use a certain type of transistor, the next step is to decide on what type of matching networks will work best. To do this, the designer must know the large-signal input and output impedances of the transistors he has chosen at the



Built-in transmit-receive switch uses diodes and quarter-wave coaxial lines (foreground). In this view the input stage is on the left, the output stage on the right. The built-in swr pickup line is etched on the right-hand side of the board.

oscillations, there is no need to switch the 13.6 Vdc supply voltage each time the driving transceiver is keyed. This fact, along with the solid-state switching network, yields an rf power amplifier free of any switching relays (often a source of trouble, particularly at these frequencies).

design considerations

Quite normally with any new design cost versus performance is one of the first considerations. It now appears that the Solid State Scientific Company's SD-1198 (\$8.45) and SD-1197 (\$12.30)

intended frequencies and operating power levels. Most manufacturers of high power rf transistors publish large-signal input and output matching information. Some companies omit the large-signal output real-part values that the transistor should be matched to. For these cases the designer may use the approximate equation:

$$R_{out} = \frac{(V_{cc})^2}{2P_o} \quad (1)$$

Where V_{cc} is the dc input voltage, P_o is the rf power delivered to the load and R_{out} is the parallel output impedance in

ohms. For reasons that will be explained later, this parallel value, along with the output capacitance of the transistor, may have to be mathematically transformed into an equivalent series value. This can be accomplished by the following equations:

$$R_s = \frac{R_p}{1 + (R_p/X_p)^2} \quad (2)$$

$$X_s = R_s \frac{R_p}{X_p} \quad (3)$$

Where R_s is the series resistance, X_s is the

matching networks

When the input and output impedances have been determined, the next step is to select the best type of matching network for the input, interstage and output. The two most commonly used networks are the pi and the tee. Theoretically, either network may be used, but the tee network will produce more reasonable values of inductance and capacitance when you're working with low values of transistor impedance. After

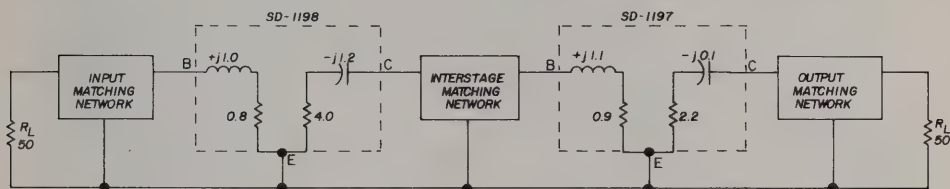


fig. 2. Series input and output impedances of the two transistors used in the two-meter power amplifier.

series reactance, R_p is the parallel resistance and X_p is the parallel reactance. Note that X_p is the transistor output capacitance in ohms at the frequency of operation.

Input matching information included on the manufacturer's specification sheet will include values for both resistance and reactance. Here again, if parallel values are given, it may be necessary, in some cases, to convert to equivalent series values.

Referring to the manufacturer's data sheets for the two transistors used in this amplifier, the input and output impedances at various power levels are given in series values:

SD-1198 input impedance at 1-watt input = $0.8 + j1.0$

SD-1198 output impedance at 10-watts out = $4.0 - j1.2$

SD-1197 input impedance at 10-watts input = $0.9 + j1.1$

SD-1197 output impedance at 35-watts out = $2.2 - j0.1$

selecting a value of circuit Q between 5 and 10, the L and C reactances for the tee network (see fig. 1) are calculated from the following formulas:

$$X_L = QR_1 - [X_1] \quad (4)$$

$$X_{C2} = AR_2 + [X_2]$$

$$X_{C1} = \frac{B}{Q - A}$$

Where:

$$A = \sqrt{\left[\frac{R_1(1+Q^2)}{R_2} \right] - 1}$$

$$B = R_1(1 + Q^2)$$

When you use these equations to

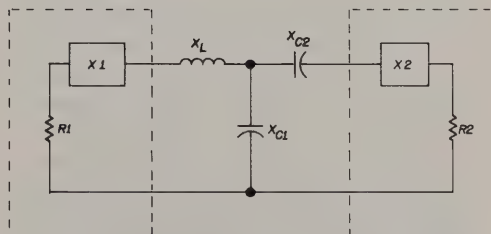



fig. 1. Tee matching network with series input and output impedances. Design formulas for this network are given in the text.

design a tee network, there are several rules which must be observed:

1. R_1 , X_1 , R_2 and X_2 must be expressed in series form. If they are given in parallel form on the data sheet, they must be converted to series equivalents using eqs. 2 and 3.

value except to stay within the 5 to 10 boundary. The designer arbitrarily picks the value he wants. It doesn't have to be calculated for this type of use. I picked a loaded Q of 10 for the input and output circuits, and a loaded Q of 7 for the interstage matching network.

The circuit for the input matching

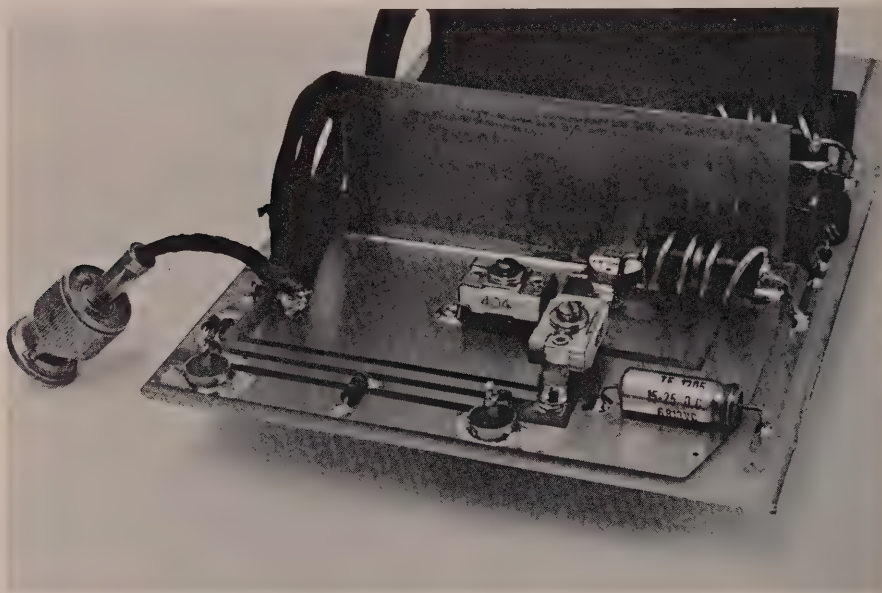

Output tank circuit and swr bridge pickup line.

2. R_1 must be lower in value than R_2 , and X_L must "look" into the lower of the two resistances. Arrange the tee circuit until this condition is met.
3. Enter X_1 and X_2 as a positive number if inductive; enter X_1 and X_2 as a negative number if capacitive.

At this point a word is in order about circuit Q . The Q in this case means the loaded Q , not unloaded. Experience has shown that a loaded Q between 5 and 10 works best in power amplifiers of this bandwidth (2 MHz at two meters). Too low Q will result in poor harmonic reduction and broad tuning. Too high Q will produce critical tuning, narrow bandwidth and poor transfer efficiency because of the high currents involved. Again, there is nothing magical about this

network is shown in fig. 3. Since R_1 , the real part of the SD-1198 transistor series input impedance, is smaller than R_2 , the 50-ohm input impedance, the configuration of fig. 3 must be used for this matching network. Reactance X_1 is the imaginary part of the transistor input impedance. Since there is no reactance at the input (see fig. 2) X_2 is zero.

Using the values of fig. 3 and the formulas of eq. 4, you will arrive at the

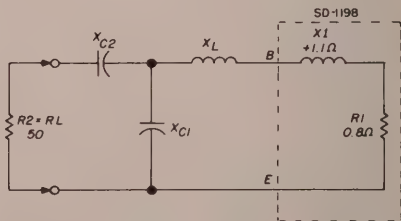


fig. 3. Input matching network.

following reactance values for the tee network components:

$$X_L = 7 \text{ ohms}$$

$$X_{C2} = 39.24 \text{ ohms}$$

$$X_{C1} = 8.76 \text{ ohms}$$

The design of the interstage matching network shown in fig. 4 follows the same procedure. Using the values of fig. 4 in eq. 4 will yield the following values for the interstage matching network:

$$X_L = 5.2 \text{ ohms}$$

$$X_{C2} = 11.6 \text{ ohms}$$

$$X_{C1} = 11.8 \text{ ohms}$$

The same technique is used to design the output matching network shown in fig. 5. The reactance of the matching network components, from eq. 4, are:

$$X_L = 22.1 \text{ ohms}$$

$$X_{C2} = 92.8 \text{ ohms}$$

$$X_{C1} = 27.3 \text{ ohms}$$

The only remaining calculation is to convert all of the inductive and capacitive reactance values into inductance (in nanohenries) and capacitance (in picofarads). This is accomplished with eqs. 5 and 6.

$$C = \frac{1}{2\pi f X_C} \quad (5)$$

$$L = \frac{X_L}{2\pi f} \quad (6)$$

where C is in microfarads, L is in microhenries, f is in megahertz and π is 3.1416. Remember that there are 10^6 picofarads in one microfarad, and 10^3 nanohenries in one microhenry.

The complete two-meter power ampli-

fier with matching networks is shown in fig. 6. Note, however, that the required inductance values are very small. Therefore, printed-circuit inductances are one of the most practical ways to obtain the required values. The graph in fig. 7 shows

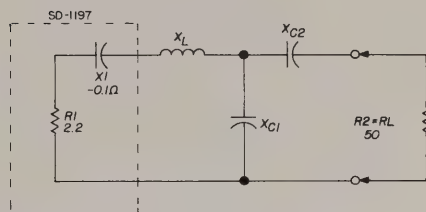


fig. 5. Output matching network.

the inductance of 0.1- and 0.2-inch copper strips on G-10 epoxy printed-circuit boards. The required length does not have to be laid out in a straight line, but can be etched in a loop as was done in the completed amplifier shown in fig. 8. When the printed inductances are etched as loops, the total length is measured on the center line of the copper strip.

Although the inductance and capacitance values shown in fig. 6 will be accurate in an ideal amplifier where all stray inductances and capacitances are eliminated, such will *not* be the case in a practical amplifier because, alas, we do not live in an ideal world. Because of the inherent strays, even in the best designs, the actual inductance and capacitance values will vary somewhat. That is why you must use variable capacitors in all three matching networks.

parasitics

When designing an rf power amplifier you must minimize the possibility of low- or high-frequency parasitic oscillations. Parasitic and spurious oscillations can be controlled by observing several important rules of thumb:

1. The impedance of the base-emitter choke should be no more than 50 times, and no less than 5 times the large-signal input impedance of the transistor.

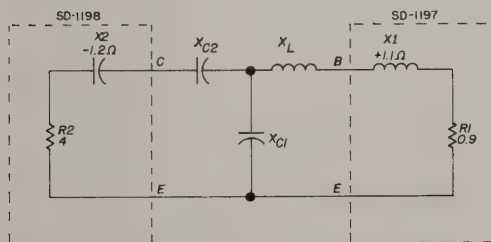


fig. 4. Interstage matching network.

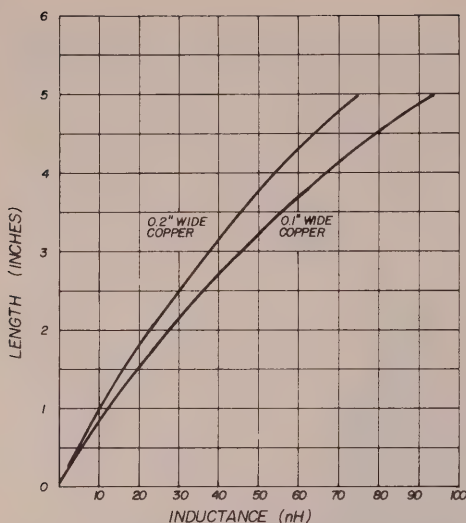


fig. 7. Inductance of 0.1- and 0.2-inch copper strips versus length. This graph may be used to determine the length of etched inductors on printed-circuit board (1-ounce copper).

2. The impedance of the rf choke in the collector circuit should be no greater than 10 times the large-signal output impedance of the transistor (10 times the load impedance seen by the transistor at the fundamental frequency or the lowest frequency of operation).

3. It is a good idea *not* to use a ferrite rf choke in the dc collector circuit due

The 0.1- μ F capacitor should be as small as possible with the shortest possible lead lengths.

If you are designing a two or more stage power amplifier, a husky ferrite rf choke should be installed between the stages in the power supply line with adequate bypassing to ground. In extremely tough cases of spurious oscillation, a carbon resistor from base to ground may help. Its value should be no more than 50 times, or no less than 5 times, the large-signal input impedance of the transistor.


The use of a metal shield which isolates the input and output circuits will sometimes increase power output by reducing degenerative feedback. Finally, when you are designing an rf power amplifier, try to use the newest transistor types available. They may cost a bit more, but the results will be well worth it.

heat sinks

A good, conservative rule of thumb for proper heat sinking is to use a heat sink capable of dissipating as much or more power than the amplifier produces. Silicon heat-sink grease should be used between the transistor header and the heat sink to insure maximum power transfer.

Use caution when tightening a transistor to its heat sink because the metal used

fig. 6. Basic design of the two-stage rf power amplifier.

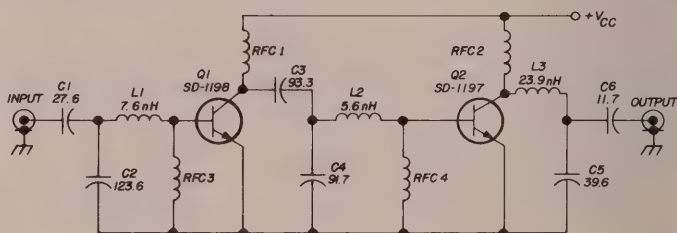


to the possibility of the ferrite saturating and turning the stage into a blocking oscillator.

4. Use three separate bypass capacitors on the B+ supply lead consisting of 10- μ F, 1- μ F and 0.1- μ F capacitors.

in the threaded studs of most rf power transistors is very soft and can be easily twisted off if you use too much torque.

construction

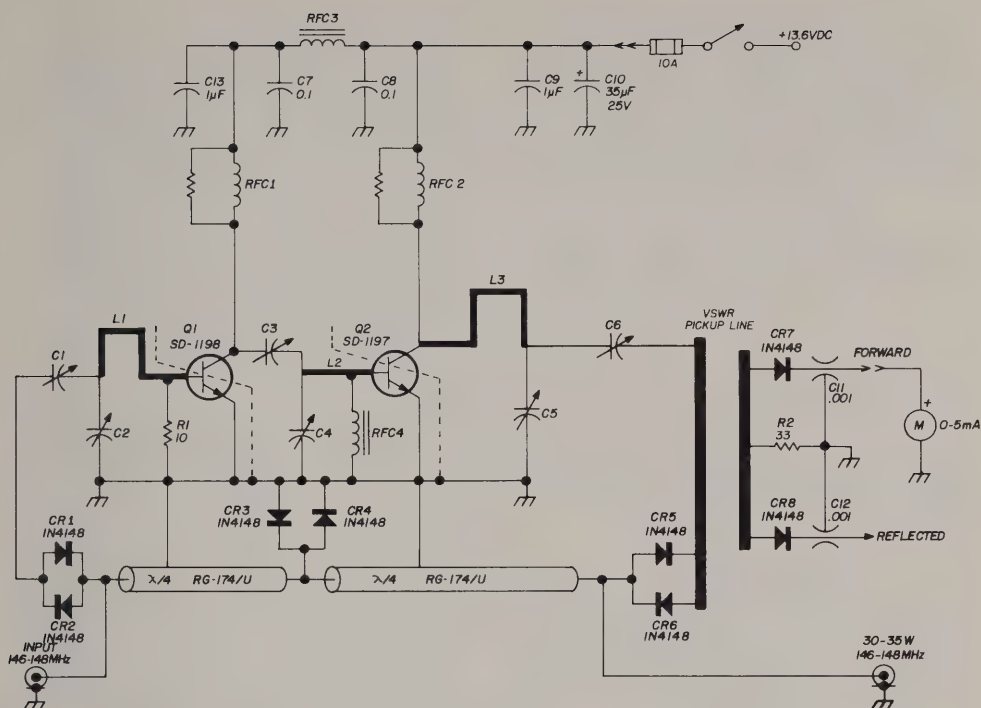The two-meter rf power amplifier shown in fig. 8 is built on a G-10 epoxy



C1,C3	15 to 115-pF trimmer (Arco 406)	CR1-CR8	1N4148 (Texas Instruments)
C4,C6		L1	7.6 nH printed inductor
C2,C5	4 to 60-pF trimmer (Arco 404)	L2	5.6 nH printed inductor
C7,C8	0.1 μ F, 50 V (Erie 8121-050-651-104M)	L3	23.9 nH printed inductor
C9,C13	1 μ F, 50 V (Erie 8131-050-651-105M)	Q1	SD-1198
C10	35 μ F, 25 V electrolytic (Sprague TE-1208)	Q2	SD-1197
C11,12	.001 μ F feedthrough (Allen-Bradley FA5C-102W)	R1	10 ohms, 1/4 watt, 5% carbon
		R2	33 ohms, 1/4 watt, 5% carbon
		RFC1,RFC2	4 turns no. 18 on 470-ohm, 2-watt, carbon resistor
		RFC3,RFC4	ferrite choke (Ferroxcube VK-200-10/3B)

fig. 8. Complete two-meter power amplifier with etched inductors, etched vswr/power indicator and solid-state TR switching. The two quarter-wave RG-174/U coaxial lines are each 14-3/16" long.

printed-circuit board with printed inductances and a printed vswr and relative power indicator.* The vswr and relative power indicator is similar to one previously described.¹ The use of a printed-circuit board allows the builder to produce a reliable power amplifier as close to the original design as possible with a minimum potential error.

The shield partition between the stages is made from 0.010-inch copper or brass, and is laid out as shown in fig. 9. The

*Completely etched and drilled printed-circuit boards for these amplifiers may be obtained from Artronics Company, Box 462, Merrifield, Virginia 22116. The board for the 1-watt input/35-watt output amplifier is priced at \$13.50; boards for the other two units are priced at \$11.50, each, postpaid.

The power transistors and other components for these amplifiers are available from Almo Electronics, Roosevelt Boulevard and Bluegrass Road, Philadelphia, Pennsylvania 19114. The price for the SD-1198, 10-watt power transistor is \$8.45; the SD-1197, 35-watt power transistor is priced at \$12.30.

heat sink is a 6-inch section of Wakefield 640 heat-sink extrusion, or equivalent.

Start construction by trimming all transistor leads to 3/16-inch long. Lightly tin the area of the PC board where the transistor leads and variable capacitors

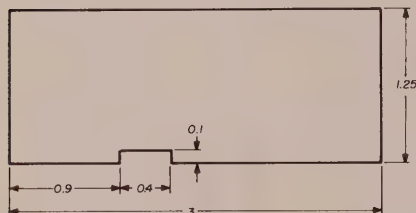


fig. 9. Layout of the copper or brass shield partitions used between stages (two required).

will be installed. Bend all variable-capacitor leads at the mid-point of the cutout slot. This will keep the adjustment screw from shorting out to ground after the capacitor is installed.

Install both transistors and solder them securely in place. Sweat solder the two shield partitions in place, and sweat solder the two .001- μ F feedthrough capacitors in place and cut off the protruding lug on the heat-sink side of the PC board.

Now install the rf chokes, base resistors, bypass capacitors and switching diodes, including the two used in the vswr indicator. Install the 33-ohm resistor in the vswr circuit. Install the six variable capacitors and adjust C1 and C6 to maximum capacitance. Install the two quarter-wave RG-174/U coaxial lines.

Attach the printed-circuit assembly to the heat sink using Dow silicon heat-sink grease (or similar). Use caution when you tighten up the transistor stud nuts, as mentioned previously.

tuneup


Temporarily connect two short coaxial cable leads (RG-174/U) to the input and output points of the amplifier. Connect the output lead to a good non-reactive 50-ohm dummy load such as a Bird Termaline®, or perhaps, a Heath Can-

tenna. Do not use a light bulb as it is too reactive at this frequency.

Connect the input to a suitable 146-148-MHz driver with 1 to 2 watts output. Connect the B+ lead through a 7-amp quick-blow fuse to preferably a variable power supply. Connect a volt-ohmmeter (5 mA range) between the vswr feedthrough capacitor nearest the output transistor and ground. Slowly raise the supply voltage to approximately 10 to 11 volts. If there is no indication on the meter, a more sensitive range may help.

During initial tuneup it may be easier to monitor the dc ammeter on the power supply and tune for maximum current, up to about 4 amperes. By that time there should be an indication on the rf power output meter. From this point on all adjustments should be for maximum indication on the rf output meter. A reading of approximately 4 mA will indicate maximum rf power output of 30 to 35 watts. This should pull 5 or 6 amperes from the dc power supply.

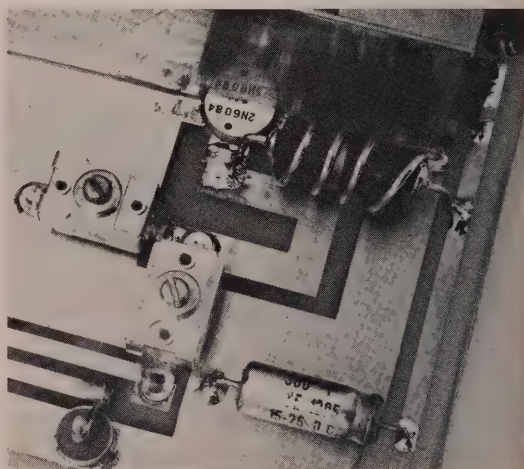The completed rf power amplifier can be installed in a Minibox or similar enclosure with the heat sink installed on the outside. Two test jacks may be brought out of the cabinet for monitoring vswr and output power. The 13.6-volt B+




Closeup of 35-watt output stage shows construction simplicity that results from using printed-circuit inductors.

lead should be in series with a switch and a 10-amp quick-blow fuse to your automobile battery or other power supply.

acknowledgements

I would like to thank Chris Galfo,

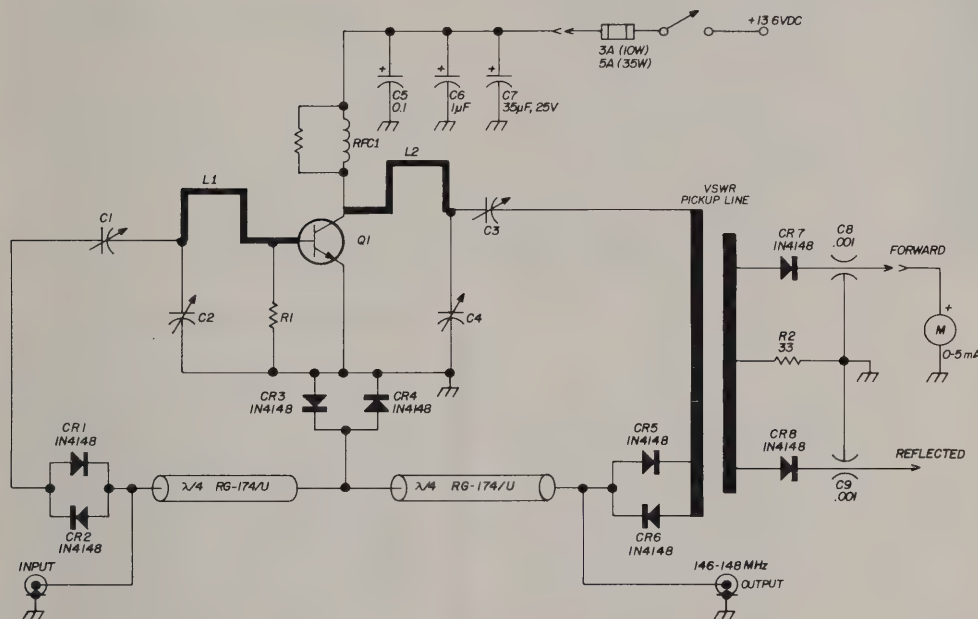WB4JMD, and Marc Dressman, WB4DRB, for permission to use their solid-state TR switching technique. I would also like to thank John Gregory, W3ATE, for providing the photo-copy work for the printed-circuit board.



C1,C3	15 to 115-pF trimmer (Arco 406)
C2,C4	4 to 60-pF trimmer (Arco 404)
C5	0.1 μ F, 50 V (Erie 8121-050-651-104M)
C6	1 μ F, 50 V (Erie 8131-050-651-105M)
C7	35 μ F, 25 V electrolytic (Sprague TE-1208)
C8,C9	.001 μ F feedthrough (Allen-Bradley FA5C-102W)
CR1-CR8	1N4148 (Texas Instruments)

L1	10-watts output, 7-nH printed inductor
	35-watts output, 8-nH printed inductor
L2	10-watts output, 28 nH printed inductor
	35-watts output, 15 nH printed inductor
Q1	SD-1198 for 10-watts output, SD-1197 for 35-watts output
R1	10 ohms, 5% carbon. 1/4-watt for 10-watts output, 1/2-watt for 35-watts output
R2	33 ohms, 1/4 watt, 5% carbon
RFC1	4 turns no. 18 on 470-ohm, 2-watt carbon resistor

fig. 10. Single-stage rf power amplifier for 1-watt input, 10-watts output or 10-watts input, 35 watts output. The two quarter-wave RG-174/U coaxial lines are each 14-3/16" long.

references

1. A. Hall, W4CGC, "Vhr/Uhf Microstrip Moni-match SWR Indicator," *ham radio*, December, 1972, page 22.
2. C. Galfo, WB4JMD, M. Pressman, WB4DRB, "A Two-Meter Amplifier for Transceiver Users," *QST*, August, 1972, page 48.
3. Frank Davis, "Matching Network Designs

with Computer Solutions," Motorola Application Note AN-267, Motorola Semiconductor Products, Inc., Phoenix, Arizona.

4. John Taylor, "Vhf/Uhf Power Transistor Amplifier Design," ITT Semiconductor Application Note An-1-1, ITT Semiconductors, West Palm Beach, Florida.

ham radio

the vertical radiator

A discussion of
the operating
characteristics
of simple
vertical antennas
for 40, 80 and 160

On the 40-, 80- and 160-meter amateur bands, a vertical radiator is superior to the horizontally-oriented dipole. It gives omni-directional coverage with extremely low radiation angles when anchored in the earth, which will provide excellent long-range communication and good signal strengths at short range.¹ Further, if properly constructed, it will provide full band, low vswr coverage over the three amateur bands.

balanced horizontal radiator

The balanced horizontal radiator system is one of the most common systems in use. If a half-wave dipole antenna is horizontally oriented in space, free of all other objects, the radiation pattern is like a doughnut at right angles to the axis of the dipole wire. However, if the dipole is situated near the earth (quarter wavelength or less), the ground reflected ray cancels most of the direct ray of radiation at lower vertical angles. Only the higher angles are propagated with appreciable amplitude under these circumstances.

If the dipole is oriented about a half wavelength above the earth, the radiation pattern has two fairly broad major lobes at right angles to the wire in the vicinity of 25-35° above the horizontal. To reduce the major lobe to 10-20° the dipole has to be elevated to approximately one wavelength above the ground. Dipoles have little radiation below 15° in any direction if less than one wavelength above poor earth.

A typical half-wave dipole for 80 meters would be about 125 feet long. If it were made of no. 10 wire (0.1-inch diameter) it would have an extremely high characteristic impedance (over 2000 ohms). This would make an efficient radiator at resonance; however, due to its high characteristic impedance, it would have a very narrow operating bandwidth

John R. True, W40Q, 10322 Georgetown Pike, Great Falls, Virginia 22066

If the two halves of the dipole could be made into a multiwire cage about one foot in diameter, the characteristic impedance would be approximately halved and the bandwidth increased proportionally.

unbalanced vertical radiator

If, instead of a balanced dipole, an unbalanced system fed by unbalanced coaxial cable were used, and further, if the outer conductors of the coaxial cable were unbraided into a plane at right

25° above the horizontal. When the length approaches 1/2 wave, the vertical pattern is concentrated between 30° and near 5°, with the peak of radiation near 15° above the horizontal. At 5/8-wave-length, the lobe is concentrated between zero and 20° with the peak radiation about 8° above the horizontal. Additionally, at this height there is a small high-angle lobe near 60°.

At lengths in excess of 5/8 wavelength the low-angle lobe diminishes in amplitude and the high-angle lobe increases

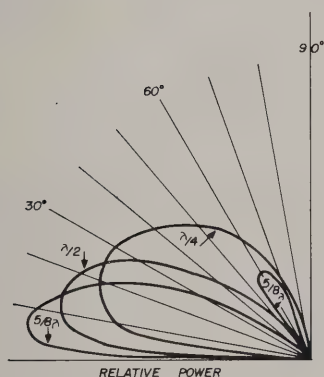


fig. 1. Radiation pattern of the vertical monopole antenna. The pattern is omnidirectional for heights of 1/4, 1/2 and 5/8 wavelength when an adequate ground plane is used.

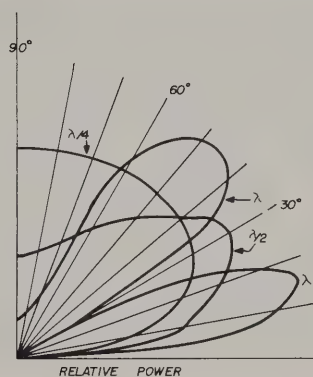


fig. 2. Radiation pattern of the horizontal dipole antenna. Pattern at right angles to the wire for heights of 1/4, 1/2 and 1 wavelength over a good ground.

angles to the center conductor, an unbalanced radiator would result. This form of radiator is known as a monopole or unipole. If the center conductor is vertically anchored in the earth it becomes known as a vertical monopole, for obvious reasons. If the length of the center conductor is made an electrical quarter-wavelength long and the plane of outer conductors is also made one-quarter wavelength, it becomes a very efficient omnidirectional radiator at low vertical angles.

When the center conductor is about one-quarter wavelength, the vertical pattern is quite broad and extends from near 10° to about 50° at the half power points with the peak radiation at about


until, at a height of one wavelength, the low-angle lobe disappears altogether and the high-angle lobe is at a maximum. See figs. 1 and 2 for a comparison of the vertical pattern of a typical vertical radiator and a horizontal dipole.

If the vertical (center) conductor is small in diameter with respect to its length, its characteristic impedance would be a high value. Typically, a quarter-wave vertical conductor at 80 meters, made of 63 feet of no. 10 wire, would exhibit a characteristic impedance of over 1000 ohms. On the other hand, if the vertical conductor were to be made of a metal pole, 1 foot in diameter (30-inch diameter triangular tubing tower is the equivalent), it would have a characteristic

impedance near 500 ohms. (This is about one-fourth the characteristic impedance of a thin dipole.) This would result in a much broader bandwidth characteristic and allow the use of the radiator throughout an amateur band without appreciable variation in its electrical characteristics. The bandwidth available for efficient operation is proportional to the radiating conductor's diameter to length ratio.

ground plane

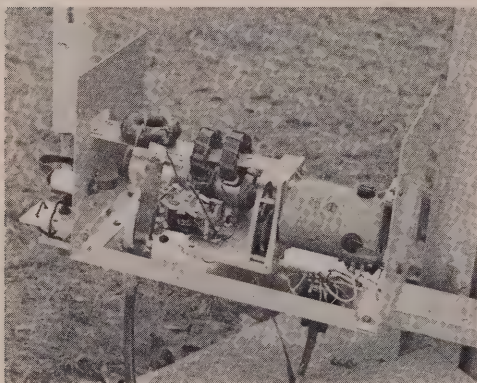Other factors which affect the efficient operation of a radiator are the



Control box located at bottom of the tower. The geared motor on the right drives the voltage-variable capacitor which is nearly hidden by the two toroid inductors. The circuit for the control box is shown in fig. 3.

ohmic (rf) resistance of the system and dielectric losses induced by material of lossy characteristics between the two halves of the radiator. No one in his right mind would erect a dipole and then surround one of the two elements with several inches of lossy material such as grass, soil or clay! Ridiculous? Not at all! For years the designers of vertical radiators have been burying the outer conductor extension of the unbalanced vertical system in the earth "to get a good ground."

A good *ground* we do not want. A large plane of highly conductive material that the vertical radiating member can see without intervening lossy dielectric is what is needed! The current must flow

between the two halves of the system without lossy material in the intervening space, and charge the medium that will carry the signal outward. The *ideal* outer conductor extension would be a continuous plane, at least one-quarter wave long of metal of high conductivity that would completely hide the earth in the near field (most model studies are made this way). Since this approach results in rather poor economics at the lower amateur frequencies a mat of mesh wire and/or a radial wire system, extending outward one-quarter wavelength in as many directions as the budget and available space will allow, will provide an adequate outer conductor extension of the unbalanced system. However, the mesh/wire should *not* be buried deeply.

Since the typical amateur's backyard location of an antenna system must be available for other purposes, as a compromise the radials may be placed into the sod of the grass, as shallow as is possible. They should not present an obstacle course, nor should they be buried so deeply that part of that expensive antenna power is used in warming the backyard.

How extensive should the outer-conductor extension plane be made? First, let's review the things not to do. It should *not* be made by merely connecting the bottom of the vertical member to several rods driven into the earth to get a good ground. Five ground rods 6-foot long (or three ground rods 10-foot long) connected to the tower base is good lightning insurance, however.

The extension plane need not be made one-quarter wavelength long in all 360° directions of the radial system. If an omnidirectional pattern is a requirement it should be about $\lambda/4$ in all directions but this is not mandatory if some pattern distortion is permissible or desirable. The individual wires need not be of large diameter if there are enough of them to satisfy the area and conductivity requirements indicated below.

Now, let's think of some of the things that should be done. The outer conductor extension plane of the unbalanced vertical

radiator should be made of material that has high conductivity. Also, between the base of the vertical and the extension plane the connecting conductors should be made of many large cross-section wires to reduce the chance of losses in this high-current part of the system.

The extension plane should have an

near the tower base (10 to 15 feet out) to augment the radial wires.

If the radial wires are spaced not more than 0.1 wavelength at a distance of $\lambda/4$, they will intercept about 95% of the energy (16 radials meets this requirement). This is not a perfect design but will provide a good extension plane for

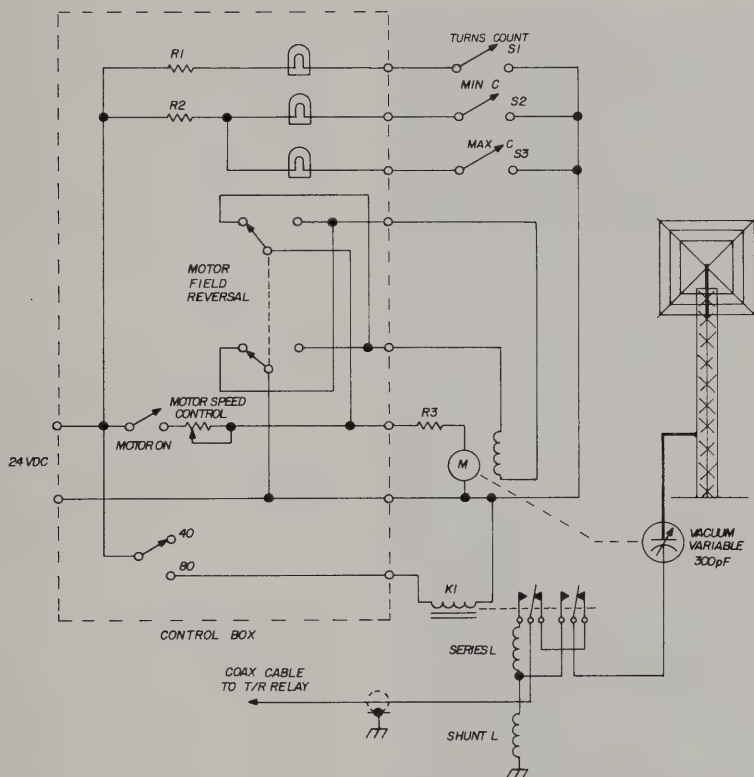


fig. 3. Electrical control system for the 40- and 80-meter vertical antenna. Microswitches S1, S2 and S3 are limit switches actuated by the motor system, which control the pilot lamps. R1 and R2 are pilot-lamp current-limiting resistors. R3 controls maximum motor speed. The motor is a 24-volt unit geared down to drive the vacuum variable capacitor.

area (total) approximately equal to the area of the vertical member. To build a capacitor with several square units of area on one plate and a single square unit of area on the other would not be good practice. A radiator is an L-C circuit; the length of its elements provide the inductance and the area of its members provide the capacity. Therefore, they should be roughly equal in area and length. If necessary, use wire matting (fence wire)

the outer conductor. If the mesh mat is made of fence wire of the type that has each crosswire welded to the longitudinal wires it will provide a high capacitance at the base of the vertical radiator.

If some directivity is desired it may be concentrated in one direction both in length and spacing. Do not overdo the length, however. There is a point of diminishing returns beyond $3/8$ -wavelengths long.¹

Excellent results can be obtained by using multielement, multiband, rotatable beams on 20 meters and above, especially if they are mounted on top of a tower that gets them far enough above the earth for low angle radiation (50 to 60 feet). They can be purchased or constructed at a nominal price. Also, they can be made

radiator on 40 meters and lower. Further, the use of a beam supporting tower for the vertical member of the radiator is recommended as a bonus with minimum additional expenditure.


base impedance

There are many charts which show the characteristic impedance, as well as the resistive and reactive components, for the *ungrounded* vertical radiator when fed at the base. However, there are several reasons why the ungrounded vertical radiator is impractical for use by the radio amateur. For one thing, any static level and/or lightning strokes in the vicinity would channel this collected energy directly to the equipment to which it is connected. Also, any use of the tower for other purposes, such as for mounting hf or vhf beams, would require all the cables to be routed through a decoupling device at the base so that these cables would not short out the base insulators. The tower would almost certainly have to be guyed in order that too much stress will not be placed on the base insulators.

Whether the tower is ungrounded or grounded, towers that require guys should be insulated from metallic guys. These guys must be broken up with egg insulators into non-resonant lengths to reduce pattern distortion. Non-conductive guys of polypropylene are relatively invisible to rf at high frequencies and are reputed to be quite strong and inexpensive. Nylon stretches too much to be considered for use in tower guying.

Also, whether the tower is guyed or unguyed, any rf and control cables from the beams down to the base, should be routed inside the tower structure all the way to the bottom to reduce pattern distortion. Additionally, they should be routed underground a few inches from the tower base to the operating position. Here is a good place to use that lossy earth. It will attenuate any rf on the outside of the cables. This will also assist in TVI reduction.

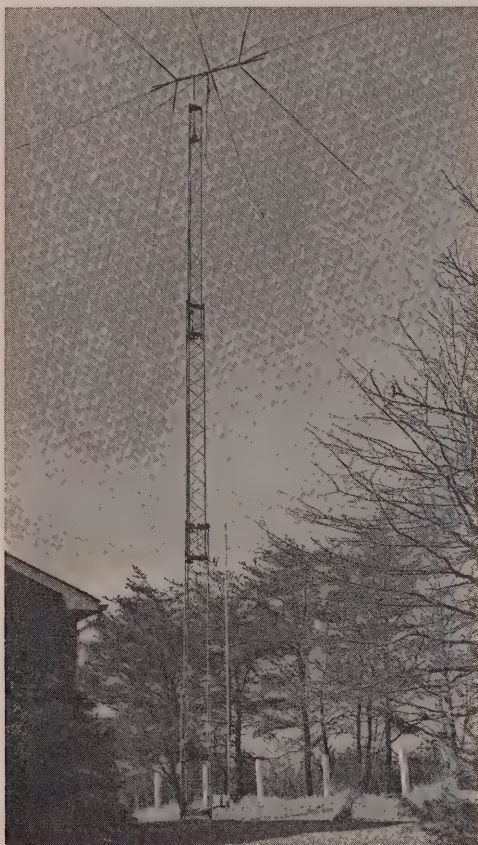There are few charts available for feed impedance versus tower heights for the grounded tower vertical radiator. Al-



The W40Q vertical-tower antenna system that covers all bands, 80 through 10 meters.

rugged enough to withstand rather heavy weather.

For the lower frequencies it is nearly impossible to get a large enough beam, with rugged characteristics, up a full wavelength in height for low-angle radiation, without excessive expenditure of funds and effort.

These are the reasons that this article is directed toward the use of the vertical

though there are too many variables in such a system to make an accurate prediction of the feed impedance some generalities can be stated.

A grounded-base tower can be easily shunt fed by the use of either the delta-or the gamma-type feed system. The delta system will radiate a little and distort the radiation pattern. Therefore, it is not considered practical. The gamma system is an excellent choice for shunt feeding the grounded radiator. Its feed impedance can be adjusted by changing the length of the vertical member. It can also be

the two higher frequencies be used with one gamma rod, and that a second gamma system be provided on the opposite (physical) side of the tower to reduce reaction between them. This second gamma system can be made physically longer on the tower than the other one which will increase the resistive component.

measurements and matching

After the gamma matching system has been installed the measurement of feed point reactance and resistive components can be accomplished by use of a commercial or home-made rf impedance bridge.² Once the electrical characteristics on each amateur band have been determined, the design of the reactance cancellation and resistance matching transformation to the coaxial feed impedance can be solved by the use of a graphical technique.³ This technique requires no more exotic tools than a straight edge, a compass and graph paper. The mathematics required will not exceed simple arithmetic. Every amateur interested in antenna work should add this valuable set of tools to his experience and knowledge.

Next month I will present some practical solutions to the construction of the vertical radiator and its ground plane. The use of the rf impedance bridge and solution of impedance matching by use of the graphical method will also be shown. A practical control system using a motor-driven vacuum-variable capacitor to cancel the reactance will be explained. Additionally, a switching system that will allow complete remote control of one vertical radiator over the 40- and 80-meter amateur bands will be illustrated.

references

1. H. Jasik, "Antenna Engineering Handbook," McGraw-Hill, New York, 1961.
2. J. 'Hall, K1PLP, J. Kaufmann, WA1VQW, "The Macromatcher," QST, January, 1972, page 14.
3. I.L. McNally, W1NCK, H.S. Keen, W2CTK, "Graphical Solution of Impedance-Matching Problems," ham radio, December, 1969, page 26.

ham radio

Table 1. Typical resistance and reactance values for various lengths of gamma rods and vertical antennas.

tower height (wavelengths)	gamma length (wavelengths)	resistance (ohms)	reactance (+j ohms)
0.25	0.1	5-10	200-300
0.5	0.2	40-80	700-1000
0.5	0.25	over 500	over 1000'

Note: The above readings were made with a fence-wire ground mat (two lengths, 100-feet long by 3-feet wide). The tower height was varied from 22 to 54 feet (a 3-element tri-band quad mounted on top). Another tower, ground plane or beam setup will have a different feed-point impedance but it should be near those figures listed above.

adjusted a small amount by changing the diameter and spacing of the gamma rod. In all cases where the gamma rod is less than one-quarter wavelength long, it will show inductive reactance. This reactance can be cancelled by a series variable capacitor. Typical $R \pm jX$ readings for various lengths of gamma rod and vertical antenna heights are given in table 1.

From table 1 it becomes obvious that a gamma length too near one-quarter wavelength is to be avoided, especially if the vertical radiator is near one-half wave. At the other extreme, if the gamma rod is much shorter than 0.1 wavelength and the tower is well below one-quarter wave high, the feed-point resistive component may be so low that transformation to the coaxial-line impedance may be difficult.

If all three lower frequencies available to the amateur are to be used on one vertical antenna, it is recommended that

phasing-type ssb generator

Complete
construction information
on a simple,
all-passive
phasing-type
single-sideband generator

Phasing-type single-sideband generators described in the literature use active devices, either to isolate the phase-shift networks from the modulators or as the modulators themselves. A few years ago it occurred to me that it should be possible to build a phasing-type sideband generator using only resistors, capacitors, inductors and diodes and using no dc power. This article describes a recent version of such a unit.

Its input requirements are about 3 volts peak rf across 50 ohms (0.1 watt) and a few tenths of a volt of audio across about 15 ohms. Output is from an rf transformer whose tuned winding can drive a vacuum tube or fet directly, while a transistor can be driven from an added low-impedance winding or a capacitive tap on the tuned winding. An attractive aspect of the circuit is that it could be fabricated as a compact, general purpose, sideband generator three-port, since only the two rf phase-shift reactors and the output transformer depend upon carrier frequency.

Usually, both phase-shift networks are designed for infinite impedance loads, automatically requiring that tubes or fets

follow. On one memorable occasion however, a design appeared for a relatively low-impedance network where the input impedances of the transistor load were included in the resistive output branches of the audio phase shift network.¹ My unit carries this idea to the logical conclusion of dispensing with the drivers and simply including the impedances of the diode modulators in the design and adjustment of the output branch of the audio phase-shift network. The rf phase-shift network design also allows for the modulator impedance. Finally, since the diode modulator impedances vary somewhat with rf drive level some swamping is used to simplify design and adjustment.

The result appears in fig. 1. The version shown operates at 10.5 MHz. Other versions have run at 12 and 7.25 MHz. The values shown for the audio phase-shift network components are those suggested by van Heddegem. The values actually used were scaled up a few percent in impedance to accommodate a couple of odd precision resistors in my own junk box. The test equipment used to build and adjust this circuit consisted of a diode rf probe connected to an ordinary vom, a low-frequency R-C bridge² and a receiver with a mechanical filter to verify sideband suppression.

The method of sideband switching is one I have not seen mentioned in print. It has the advantage that one side of every modulator input may remain permanently grounded. The only audio transformer required is the one driving the phase-shift network.

circuit description

The circuit consists of three sections: the audio and rf phase-shift networks and

Worthie Doyle, W7CMJ, 1120 Bethel Avenue, Port Orchard, Washington 98366

the two balanced modulators. The rf phase-shift network values are those I used, but other builders should be guided by what identical precision resistors are available. The diode balanced modulators are so arranged that both rf and audio inputs are single-ended with one side grounded. The audio and rf inputs are effectively in series, as usual.

The rf phase-shift network is an ordinary arrangement of plus and minus 45-degree sections, except that an estimate of the resistance looking into each modulator is made part of the resistive branches. To estimate this resistance, note that each diode conducts half the

formance of the audio phase shift network. They have about 100 ohms reactance at 10.5 Mhz but do not significantly affect the rf phase shift, since they are in series with a few thousand ohms as well as combining in quadrature. Furthermore, any effects they have are identical for the two modulators, shifting phase slightly without changing the 90-degree relationship.

If 51 ohm resistors are used in the phase-shift networks, the modulator resistance is swamped by a factor of about 28, so a 28% error in the estimate of the modulator resistance is equivalent to a 1% error in the rf phase shift resistor. For

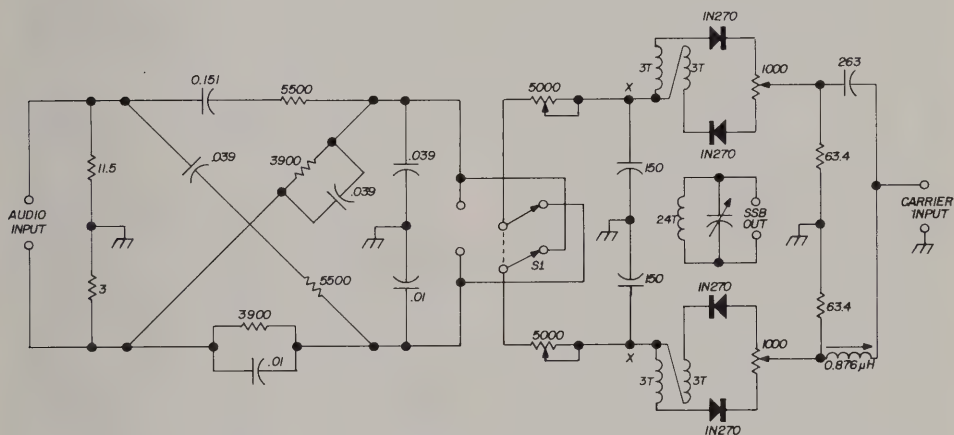


fig. 1. Circuit of a passive phasing-type ssb generator which uses no active devices.

time. With one diode conducting, the rf input resistance for each modulator is half the balancing pot, 500 ohms, plus a few hundred more ohms for the diode (varying somewhat with rf drive level) plus another 500 to 1000 ohms for the load seen at the output winding feeding the rf transformer. This load will depend on the Q of the rf transformer and on the load presented by the other balanced modulator. You can only guess at these values, but a reasonable guess is that they will nearly match the roughly 700 ohms of diode plus balancing pot, giving an estimate of about 1400 ohms.

The 150-pF bypass capacitors were made small to avoid affecting the per-

this combination the effective resistances of the rf phase shifter output branches are about 49.2 ohms; the rf phase shifter L and C should have this reactance at the operating frequency.

My network was built by making the C from a precision unit a little above the calculated value in series with a larger low-precision unit. The L, a slug-tuned coil, was then adjusted so the rf voltages across the two phase shifter outputs were equal. As a check, note also that each of these outputs is about 70.7 percent of the whole rf input voltage. There is no reason why both L and C should not be variable. In that case you can forget about the exact modulator impedances as long as

the two are built identically, but the rf phase-shift adjustment becomes more complicated.

audio phase-shift network

The audio phase-shift network was made of junk-box items. Resistors were precision types or a precision type shunted by a much larger ordinary resistor. Capacitors were paralleled from whatever was on hand. All R and C values were checked on the bridge before being wired in. I've built three audio phase-shift networks by this *dead-reckoning* method (no adjustments) and they all seemed to work fine as judged by listening to speech while switching sidebands.

The resistances at the input of the audio phase shift network should have a ratio of 3.83 with 1% accuracy, but actual values don't matter. I used 5.24 and 20 ohms because my junk box supplied them. Note that the sum of these two resistances should be matched to the audio driver. A junk output transformer from a midget broadcast set is ideal, since it has about the right turns ratio to match a medium-mu triode to 15 or 30 ohms and operating it at this higher impedance level will reduce low-frequency response below 300 or 400 Hz. Be sure neither old vc lead is grounded when using such a transformer.

The important adjustment in this unit is to make each output resistive branch look like the desired 3900 ohms. Each of these resistances is the sum of the trimpot resistance and the modulator audio input resistance. The modulator resistances will be about 700 ohms since the modulator rf transformer windings have negligible audio impedance. This shows that there is a swamping factor of about 5 for variations in the audio impedance of a modulator.

To insure that the resistance of this branch is correct under operating conditions, disconnect the input end (end at the dpdt switch) of each trimpot from the audio phase-shift network and connect this end of the trimpot and ground to the R-C measuring bridge. Set the bridge dial to 3900 ohms (or whatever

the design resistance is for your own audio phase-shift network). Turn on the rf carrier oscillator to be used with this unit. It should be operating at the intended voltage, preferably regulated (I'm using a 6C4 fed from a VR150). Now adjust the trimpot for a bridge null. Repeat for the other trimpot and both output branches will have the desired effective resistance.

To insure proper combination of the two modulator outputs, all coils of the output transformer should be closely coupled and both sets of modulator windings should be identical bifilar windings. The easy way to do this, used in the unit described, is to wind the output rf transformer on a high-permeability toroid. The bifilar modulator windings are made from a slightly twisted pair of a few inches of thin magnet wire (cotton or silk covering increases your confidence in the absence of shorts) closely wound around the core.

The two modulator windings and the tuned output winding are all slightly spaced from one another so coupling will be mainly from flux through the core. The numbers of turns indicated in **fig. 1** worked at 10.5 MHz for a nice mystery core from the junk box. For your own core an easy solution is to use a grid-dip meter and the expected tuning capacitance (add 10 pF or so for strays) to discover how many turns are needed on the tuned winding. The modulator windings are then chosen for the indicated turns ratio.

Another arrangement I have used successfully is a solenoidal tuned winding with the two modulators connected to a quadrifilar winding made from four wires slightly twisted together and wound over the solenoid near the middle. A slug-tuned form is convenient in this case. The turns ratios are not critical. Cup cores are nice if you have small, steady fingers.

Balance pot adjustment also deserves some comment. Originally the usual 1000-ohm pots shown in the diagram were used. Later these were replaced by 100-ohm pots at the centers of pairs of 470-ohm resistors to ease carrier nulling.

This required some diode selection, unnecessary with the 1000-ohm pots. The diodes are 1N270s removed from computer boards, but any rf germanium diode is suitable.

In this diode balanced-modulator circuit an rf bypass is often shown across each 1000-ohm balance pot. Such bypasses will cause balance to occur far from pot center unless the diode back resistances are matched or swamped by about 50k across each diode. The reason is that this rf bypass assumes a steady voltage that applies reverse bias to the diodes. Since the diodes are in series for this bias, they divide it in proportion to their back resistances. Unless they are well balanced or swamped to equality the result is to require an eccentric setting of the carrier balance pots. The rf portions of the unit should be shielded so that balance is unaffected by hand capacitance.

sideband selection

The usual method of switching sidebands in a phasing-type sideband generator is to reverse the phase of one of the audio signals or one of the rf carrier inputs. This is not practical when all modulator inputs are to be single-ended with one side at ground. A dpdt switch could be used to reverse the connections of one pair of diodes to the corresponding modulator output winding, but this destroys the symmetry of the circuit and might degrade sideband suppression. At this point in thought I noticed that interchanging either the two audio signals or the two rf signals would also switch sidebands. Obviously, the audio signals are the ones to switch. I have never seen this method of sideband switching in print but assume the experts are aware of it.

results and afterthoughts

When I built the present unit, the rf phase shift C was computed and a fixed capacitor wired in; the coil was then adjusted to make the two modulator rf input voltages equal. The audio phase-shift network trimpots were then adjust-

ed as described earlier and a voice-modulated signal tuned in on a receiver with a 3-kHz wide mechanical filter. The signal sounded normal. When the sideband switch was flipped only a few faint glitches were audible, indicating satisfactory sideband suppression. As noted, the test equipment used on this project is too rudimentary to permit any fancier assessment of unwanted sideband suppression. Suppression was audibly the same on either sideband position.

Having finished the unit and gotten it working, I noticed that I'd forgotten to include an audio balance adjustment to equalize the contributions from the two balanced modulators. In general such an adjustment should be included. Don't try to do it by twiddling the trim pots in the audio phase shift network. A suggested method is about 10k from one of the points X to ground and 5k pot plus 7.5k resistor from the other point X to ground. These resistors should be in the circuit with the variable branch set at 10k when the trim pots are adjusted.

The very small adjustment that is made to reach exact audio balance will not significantly affect the operation of the audio phase-shift network. If audio balance can't be reached (poor unwanted sideband suppression) look elsewhere for the trouble. A test of the audio phase-shift network can be made by checking that the output voltage at each trimpot (end away from modulator) is exactly half the voltage across the 3-ohm input resistor.

This unit has been on the air with conversion to the 75-meter band, where it was reported as sounding like a good, normal ssb signal. Of course, it also sounded normal, as monitored on my own receiver, before it was put on the air.

references

1. Wilfried van Heddegem, ON4HW, "Audio Phase-Shift Network for Transistorized SSB Transmitters and Receivers," *QST*, December, 1964, page 27.
2. Beverly Dudley, "An Impedance Bridge for Less Than Ten Dollars," *QST*, June, 1950, page 19.

ham radio




the **REPEATER** 2 Meter Fixed Station

Designed for the man who demands professional standards in 2 meter equipment. *REPEATER LINE* fixed station antennas are the 2 meter HAM's dream come true. With everything you need for top fixed station performance...toughness, efficiency and the gain to gain access to distant repeaters with ease. Work many stations, fixed or mobile, without access to a repeater.

The right antennas for the new FM transceivers...or any 2 meter fixed station.

REPEATER LINE Fixed Station Antennas

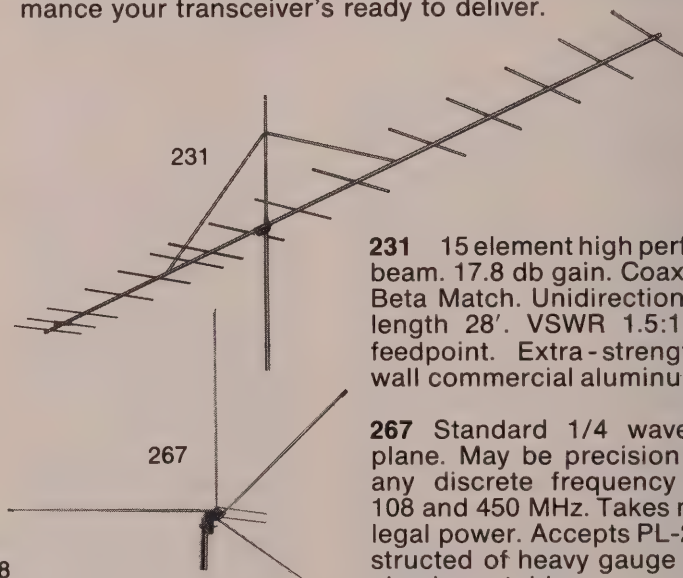Tough, high efficiency antennas with a long, low radiation. For the top signal and reception you want...and the top performance your transceiver's ready to deliver.



231 15 element high performance beam. 17.8 db gain. Coaxial balun. Beta Match. Unidirectional. Boom length 28'. VSWR 1.5:1 52 ohm feedpoint. Extra-strength heavy wall commercial aluminum tubing.


267 Standard 1/4 wave ground plane. May be precision tuned to any discrete frequency between 108 and 450 MHz. Takes maximum legal power. Accepts PL-259. Constructed of heavy gauge seamless aluminum tubing.

268 For repeater use. Special stacked 4 dipole configuration. 9.5 db offset gain. 6.1 db omnidirectional gain. Heavy wall commercial type construction. 144 thru 174 MHz. 1.5:1 VSWR over 15 MHz bandwidth eliminates field tuning. Extreme bandwidth great for repeater use. Center fed for best low angle radiation. DC ground. Complete with plated steel mounting clamps.

LINE from **hy-gain**


Antennas with real PUNCH!

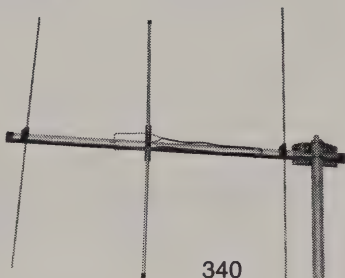340 3 element high performance beam. 9 db gain. Coaxial balun. Special VHF Beta Match configuration. Unidirectional pattern. VSWR 1.5:1. 52 ohm impedance. Heavy gauge aluminum tubing and tough aluminum rod construction.




340

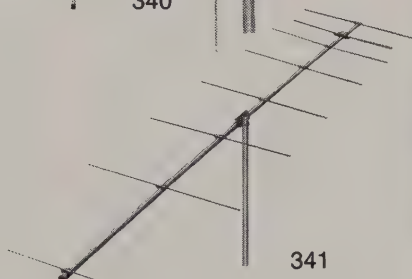341 8 element high performance beam. 14.5 db gain. Coaxial balun. VHF Beta Match. Unidirectional. Boom length 14'. VSWR 1.5:1. 52 ohm feedpoint. Heavy gauge commercial type aluminum construction.



341

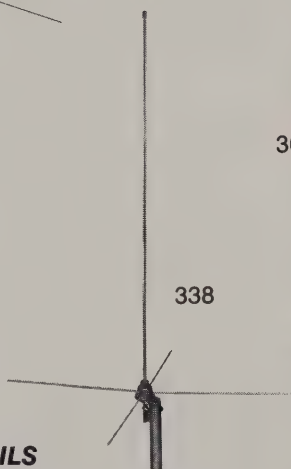338 Colinear ground plane. 3.4 db gain omnidirectionally. Vertically polarized. 52 ohm match. Radiator of seamless aluminum tubing; radials of solid aluminum rod. VSWR less than 1.5:1. All steel parts iridite treated. Accepts PL-259.



338

362 SJ2S4 high performance all-driven stacked array. 4 vertically polarized dipoles. 6.2 omnidirectional gain. 52 ohm. May be mounted on mast or roof saddle. Unique phasing and matching harness for perfect parallel phase relationship. Center fed. Broad band response. DC ground.



362

WRITE FOR DETAILS

For top fixed station performance on 2 meters...
THE REPEATER LINE

From
HY-GAIN ELECTRONICS CORPORATION

P. O. Box 5407-WD Lincoln, Nebraska 68505

rf phase meter

An instrument
for measuring
the phase angle
between elements
of vertical
antenna arrays

Vertically polarized directional antennas are popular for use in the 40- and 80-meter amateur bands.¹ Successful operation of these antennas depends on the phase relationship between antenna elements. Described here is an instrument that permits phase-angle measurements within acceptable limits for aligning such antenna systems.

R. G. A. Brearley, VE2AYU, and Werner H. Korth, 805 Wake Street, Arvida, Quebec

Computer studies² have shown that satisfactory antenna performance can be obtained if the lead-lag phase angles are within ± 5 degrees of the target (design) figure and the current ratios are within ± 5 percent of the target ratios. The phase meter described will perform within these limits to 7 MHz. The circuit uses standard components and is easily calibrated with a vtvm and oscilloscope. The circuit also has inherent lead-lag discrimination.³

The phase angle, θ , by which waveform A leads B (fig. 1) can also be expressed as a time differential, Δt . The phase meter measures Δt , which can be read in terms of an average dc voltage at the output.

functional description

As an aid to understanding circuit functions, the truth tables and timing diagram of figs. 3 and 4 should be used in conjunction with the block diagram, fig. 2.

Channels 1 and 2 are identical up to the Exclusive-OR gate. The input to the Schmitt trigger is provided by the pickup loops, which are not part of the circuit but are placed near the applicable antenna element. The Schmitt trigger squares the positive half of the incoming sine wave, and its output is fed to flip-flop 1.

A flip-flop is essentially an electronic

switch. The devices each have two output terminals, one of which is on while the other is off. Every negative-going input pulse will cause the flip-flops to switch state. If, for instance, output A is on, then the next negative-going input pulse will switch A off and B on. The next negative-going input pulse will then switch the device to its original state; i. e. A to on and B to off. Thus, if A is the output terminal, it will be on for every second input pulse, and the input frequency will have been divided by two in the output. Two flip-flops are used in series to divide the signal frequency by four. The first flip-flop in Channel 1 is used to provide gating pulses for each NAND gate.

The Exclusive-OR gate provides an output if either A' or B' is present, but not if both are present or both are absent. Therefore its output consists of pulses exactly as wide as interval Δt , or the lead-lag angle, \emptyset .

A NAND gate will always have an output except when both inputs are present. The timing diagram shows that for a Channel 1 input leading that of Channel 2, NAND gate 1 output will be at a constant value, which is that of the logic on value. This average dc level will be directly proportional to the lead angle of Channel 1; it will decrease with increasing lead angle. If, on the other hand, Channel 2 input leads that of Channel 1 NAND gate 2 output will be increasing lead angle. If, on the other hand, Channel 2 input leads that of Channel 1

continuously on, while the average dc level of NAND gate 1 will vary with lead angle. Thus, the circuit provides a linear measurement of the lead-lag angle between two waveforms and also allows an unambiguous determination of which waveform leads or lags in relation to the other.

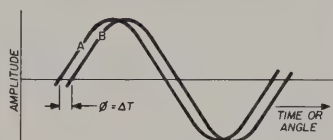


fig. 1. Relationship between two sine waves in terms of phase angle, \emptyset , and time, Δt .

circuit details

The phase-meter schematic is shown in fig. 5. A single pickup loop (for simplicity) is shown connected to the system. The pickup loop acts as a current transformer looking into coaxial lines terminated in their characteristic impedance, Z_0 (R1-R6). Potentiometers R20, R21 are used to reduce and equalize input voltages to the logic circuits. The MC1550G and the 2N2369 operate as a combined Schmitt trigger (wave squarer) and interface to drive the following TTL stages.

The circuit was originally developed for use up to 5 MHz.⁴ As modified here it's not a true Schmitt trigger but will produce reasonably square waves to 10 MHz. Calibration potentiometers R11, R12 are used to compensate for unequal phase shifts through each channel.

The frequency dividers and subsequent logic circuits must be connected as shown, otherwise errors and confusion in the phase lead-lag determination will result. The output metering points have RC filters that respond to the average value of the square waves. Various RC combinations were tried and did not seem critical. The circuit will work without the filters, but as a matter of principle it's not good practice to have rf hash floating around the chassis. Test switch S4 is used to check the operation of the Ex-



Top view of the assembled phase meter.

clusive-OR circuit, and reset switch S5 is used to synchronize the channels.

power supply

The power supply is important because the calibration limits of the phase

inductive. We used the meter described in reference 5 to check a couple dozen carbon ¼-watt resistors to find six suitable 52-54 ohm components.

The meter has six inputs rather than three so that phase angles in the antenna

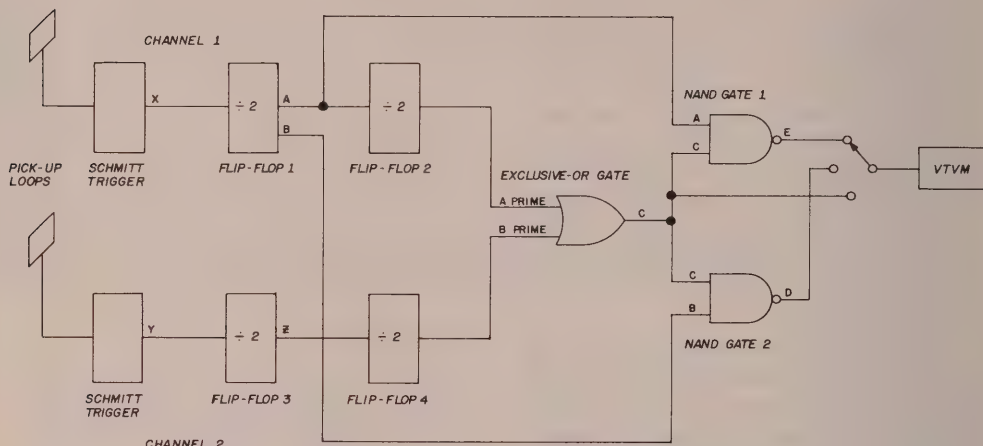


fig. 2. Functional block diagram.

detector (Exclusive-OR) circuit output are 0.09 and 3.8 volts. Originally an unregulated supply was used. During the calibration of the meter these limits changed with variation in the house-current supply.

Since the power supply is mounted externally, the protective diodes are needed in case of wiring errors. The various voltage-dropping resistors ensure equal positive and negative voltages on each of the triggers and give the approximate 3 volts needed for the HI inputs of the flip-flops and gates. If you wish to use a built-in ± 5 volt regulated supply, then only R26 and R27 will be needed.

component notes and layout

Details of the pickup coils are shown in fig. 6. With the transmitter running at 40 watts input, sufficient voltage was available to drive the meter. Although the length of the cables between coils and meter is not important, *all* cables must be the same length.

It is absolutely essential that the terminating resistors, R1-R6, are non-

power divider could be measured as well as those between the antenna elements. The meter has two types of input connectors, which further enhances its versatility.

Wiring to the input selector switches must be as shown to avoid phase-shift errors (see the schematic and the bottom view of the chassis). Diode probe circuits C1, CR1, R7 (channel 1) and C2, CR2, R8 (channel 2) must have leads as short as possible. However, the wiring between R7, R8 to switch S3 can be 4 inches long, unshielded.

As can be seen in the photos and the component layout sketch, fig. 7, most of the circuit is on a PC board fitted with twelve 8-pin, dual in-line sockets. The

Input	output	Input	output	
A C	E	A' B'	C	A' B' C A B D E
0 0	1	0 0	0	0 0 0 1 0 1 1
0 1	1	0 0	1	0 0 0 0 0 0 0
1 0	1	1 0	1	1 0 1 1 0 1 0
1 1	0	1 1	0	1 1 0 0 1 1 1

NAND gate 1 exclusive-OR combined logic

fig. 3. truth table.

board happened to be on hand and permitted about a dozen different variations in circuit layout, which accounts for the general disorder shown. If the project were to be started again, stick-on "Circuit Zaps" and a perforated board would be used. Note that wiring must be as direct as possible for the rf circuits. For example, switch S4 must be mounted near the flip-flop to which it's connected.

Voltage-dropping pots and isolating chokes are on a separate board and its location isn't critical. Number 26 hook-up wire was used throughout, and coax was used only at the switches and Schmitt trigger inputs.


Carbon resistors rated $\frac{1}{4}$ watt should be used, because they perform well at high frequency. Pots R11, R12, R20, and R21 should be carbon. Chokes L1, L2 aren't critical but are needed to isolate the Schmitt triggers.

initial adjustments

The only test instruments needed to align the phase meter circuits are a scope with a 5-MHz bandwidth, an rf probe, a Heath vtvm, and an rf signal generator.

The following procedures should be followed for initial adjustments.

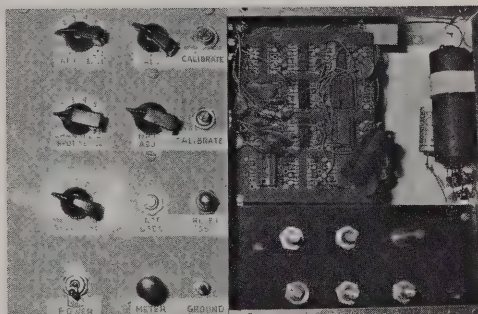Before plugging in any devices, turn on the power and ensure that the correct polarities appear at the various device terminals. The power supply used here



Top view with cover removed.

provided ± 5.8 volts at the input to the phase meter circuits. When all devices were installed, the voltage appearing after the protective diodes was about ± 4.9 volts.

After checking voltages, turn off the power, connect the vtvm to the meter terminal of S3, and plug in the 7473s and the EX-OR gate devices. Adjust R26 for 3.0 volts at the EX-OR gate HI outputs. With S3 at position C and S4 in the normal position, the vtvm will indicate either 0.09 volt or 3.8 volts, which are the LO and HI outputs of the EX-OR gates. Pressing reset switch S5 will cause the 3.8 volts to decrease to 0.09 volt; or, if the reading is already 0.09 volt, pressing S5 will make no difference. Very often when the power is switched on, the reading will be 0.09 volt and no amount of pressing the reset switch will produce 3.8 volts; this is normal. With switch S3 still at position C and switch S4 in the opposite position, the meter will read 3.8 volts, and pressing the reset switch will have no effect.

Return S4 to normal and turn S3 to D and E, which are the NAND gate outputs. Normally 3.8 to 3.9 volts (HI) will be found, and no amount of pressing the

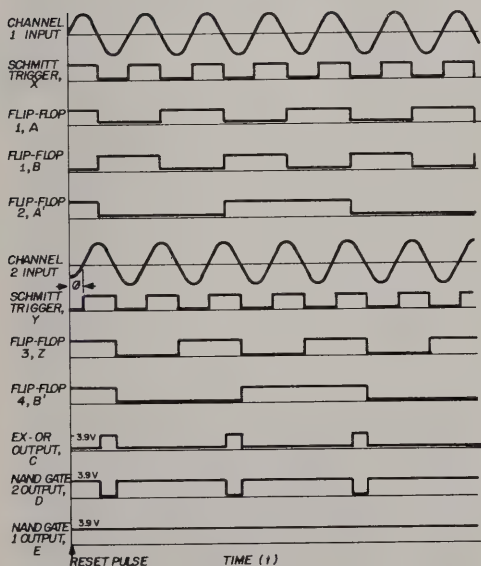


fig. 4. Timing diagram. In this example channel 2 lags channel 1 by $\phi = 90$ degrees. Note that the average values of C, D, E correspond to those in the calibration curve, fig. 8.

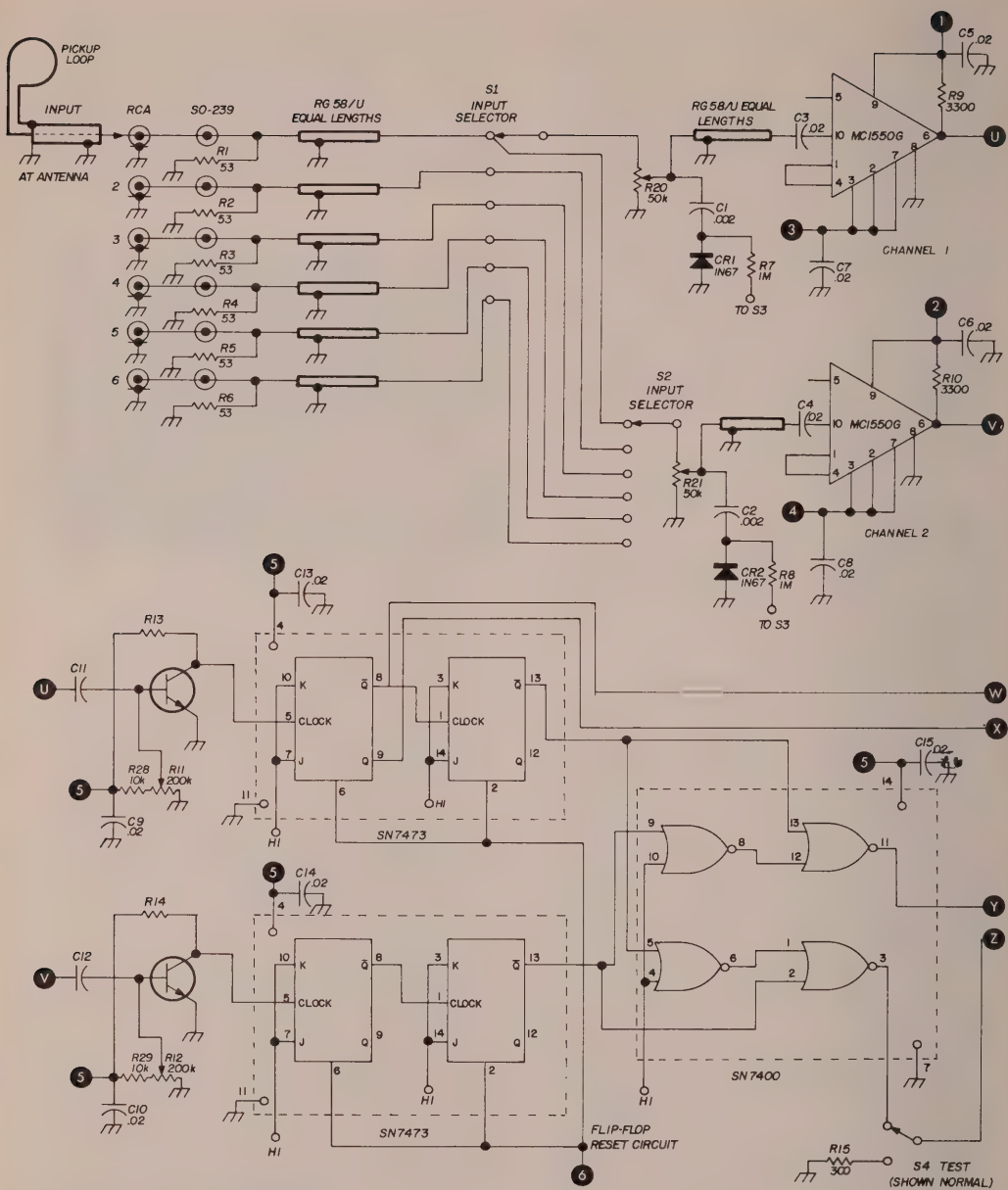


fig. 5. Phase meter schematic.

reset button should change this. With S3 at the opposite position, the meter will read the LO of the NAND gate. Note that the values of HI and LO depend on IC construction and the values mentioned here just happen to be what were found with these particular devices. If you don't get the above sequence of voltages you've

made a mistake somewhere, and any further steps will be just a waste of time. Plug in the MC 1550s and 2N2369s and adjust the supply voltages by means of R22, 23, 24, 25 so that positive and negative voltages are equal at the IC terminals.

It's possible to adjust the instrument

values of R28 and R29 slightly.

Repeat the procedure for Channel 2 with a signal at input 2 and S2 at Input 2. Next, put the two channels in parallel via S1 and S2, and feed in a signal at 1 MHz

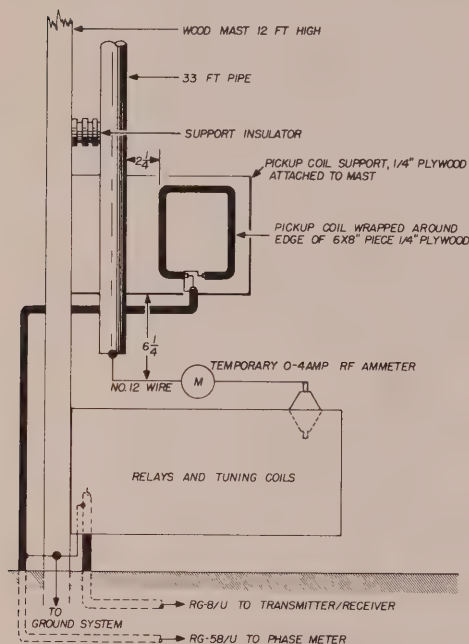


fig. 6. Antenna pickup loop details. The pickup coil must be in the plane formed by the L of the support pipe and the no. 12 wire.

(the pot setting for 7.5 MHz will also be good down to 1 MHz). Adjust R20 and R21 for equal voltages with switch S3 in positions 1 and 2 and switch S3 to C. The reading here will likely be anything up to 3.8 volts, and the object is to get it as close to 0.09 volt as possible. Press and release the reset button to ensure that 0.09 volt is possible. By carefully readjusting R11 and R12 the reading can be brought down to 0.09 volt. Then, when frequency is increased to 7.5 MHz, this reading will rise to about 0.18 volt. Further adjustment of R11 and R12 will bring this down to about 0.12 volt, which is at zero degrees of the calibration chart, fig. 8. Values of 3.7 and 3.9 volts should appear at positions D and E and these are also on the chart. If you can't get C down

to 0.12 or 0.11 volt, then something may be wrong with metering circuits R20, C1, R7.

The meter is working in every respect when the above readings are obtained. Input signals as low as 0.05 volt and as high as 0.6 volt gave equal phase angle readings for a given length of test cable. A somewhat annoying feature of the basic circuit is that it covers 720 degrees, as shown on the timing diagram. This means that a phase angle of, say, 30 degrees gives a reading of 0.25 volt and also a reading of 390 degrees at about 2.05 volts. Hence, when the zero adjustment is made, the meter will occasionally pop up to 1.8 volts, and the reset switch must be pressed to bring it back to the proper value. This causes no ambiguity because the D and E readings change accordingly and, as will be explained in the next section, the sum of any two valid C readings must be around 1.88 volts.

calibration

The secret is to find six readings that correspond to a known lag or lead condition and plot the data. For example, with a signal frequency of 3.8 MHz fed to Channel 2 and a cable length of 45 ft. 9 in. connected between Channel 1 and Channel 2, Channel 2 will lead Channel 1 by 96.5 degrees, assuming a cable velocity factor of 0.66.

table 1. Channel 1 and 2 phase angle as a function of calibration voltage.


test	switch 3 position	meter reading (volts dc)
1	C	0.55
	D	3.34 Channel 2 leads Channel 1 by 96.5 degrees
	E	3.39
2		1.33
		1.88*
	D	2.28 Channel 2 lags Channel 1 by 263.5 degrees
	E	4.03

*Sum of any two C readings (validity check)

After adjusting the Schmitt trigger inputs to equal values (0.26 volt) and momentarily pressing the reset switch, the readings in test 1, **table 1**, were noted. Pressing the reset switch four or five

4, 11 and 23 feet were on hand and were combined in various ways to obtain the complete calibration curve. From here on, all antenna measurements are in terms of Channel 2 as reference. Separate cali-

fig. 7. Component layout. Note that the MC1550G and 2N2369 devices are mounted in sockets, which in turn are soldered to the PC-board-mounted dual in-line sockets. (Other ICs are for experiments presently in progress.)

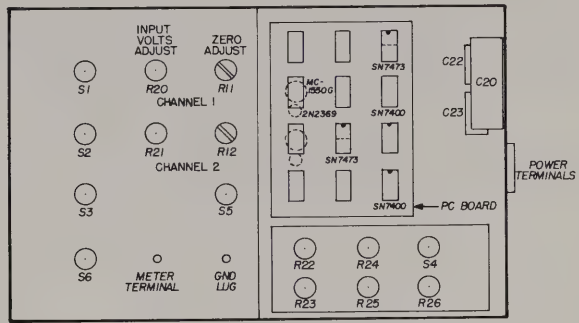

times changed the values to those shown at test 2, **table 1**.

From the timing diagram and the magnitude of the HI and LO voltages of the EX-OR gate, it is known that a 90-degree lead will correspond roughly to 0.5 volt at C, 3.3 volts at D, and about 3.9 volts at E. The discrepancy at E in test 1 (**table 1**) is annoying but poses no difficulty. The values found during test 2 were about the expected complementary values. Note that the sum of the C readings is always about 1.88, and this fact is used as a validity check at all times.

The six values are plotted on the calibration chart, **fig. 8**. Pieces of coax of

bration curves are needed for 3.8 and 7.1 MHz. It is important that straight lines connect plotted points. Any attempt to draw a smooth curve will lead to frustration and inaccuracies. Note that curves D and E do not give much discrimination between lead and lag in the region of ± 30 degrees. However, the readings of the complementary angles will reveal the answer. Sometimes when measuring very small angles (± 5 degrees) the complementary angle couldn't be obtained. This problem was resolved by installing coax of known electrical length in series with one input, then repeating the measurement.

experimental notes

By feeding power to one antenna at a time, with the other antenna detuned, the pickup coils were positioned so that the voltage measured on the phase meter was identical for a given current flowing in the antenna. The results of typical calibration runs are shown in **fig. 9**.

To prove out the position of the pickup coils, the antenna elements were fed in parallel pairs, and nearly equal currents and small phase angles were noted. The coax cables to the antenna were of equal length but were only 0.9 wavelength electrically at 7.1 MHz. By increasing the coax lengths to 1.0 wavelength, unwanted

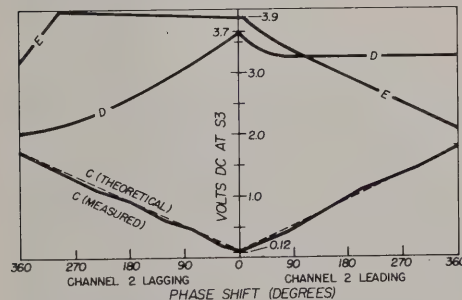


fig. 8. Calibration data for 3.8 MHz. Differences between theoretical and measured values of C are exaggerated to illustrate the need to connect points with straight lines. At 7.1 MHz the lines for C are similar, while those for D and E have the same shape but different values.

phase shift due to high swr was eliminated. With the three antenna elements active and the phase shifters and power dividers correctly adjusted, the f/b ratio (on the air) was 25 dB, which confirmed our design objective. Theoretical antenna patterns are shown in **fig. 10**.

acknowledgements and conclusions

This project was a team effort that included contributors over a wide area. John Ravenscroft, VE2NV, Montreal, provided many ideas and encouragement. Mr. Sam Tilden, also of Montreal, provided the data for the pickup coil design. Norman Tweit and Wes Vincent, Scottsdale, Arizona, contributed the basic Schmitt trigger circuit. George Oshiro provided the basic gating idea. Our colleagues at work provided many suggestions and our employer, the Aluminum Company of Canada, made test equipment available.

Preliminary tests have indicated that this instrument will work at frequencies to 10 MHz, and the limitation is probably due to the Schmitt trigger. The circuit was examined with the aid of a Tektronix scope, and it looks as if the flip-flops are another limiting factor. Operation

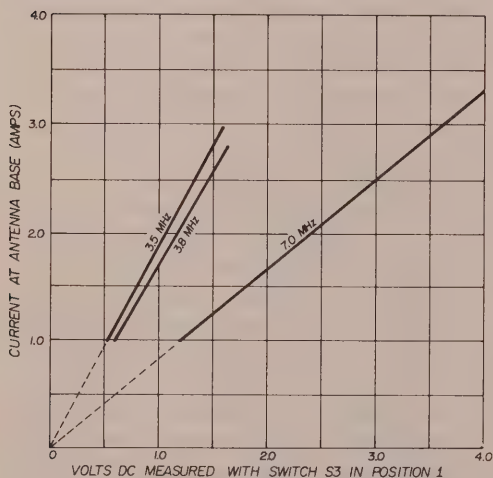


fig. 9. Pickup-coil calibration curves. The rf ammeter available was rated 0-4 A, and the meter scale was not calibrated in the 0-1 A range. Therefore the high-current points shown were used to prove system linearity and to correctly position the pickup coils.

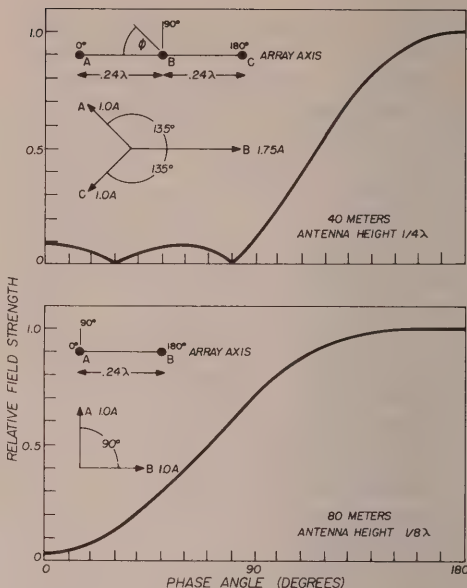


fig. 10. Antenna patterns. Data are shown in Cartesian rather than polar coordinates because null points are more easily identified. Data were plotted with the aid of a computer program (reference 2).

beyond 10 MHz would probably mean using a different family of ICs, such as the EECL. A PC board would be essential.

If one were to substitute the higher-speed TTL devices, the result would probably be a more linear calibration curve, which would permit the output meter to be calibrated in terms of phase angle.

references

1. R. Myers, W1FBY and J. Hall, K1PLP, "Phased Verticals in a 40-Meter Beam-Switching Array," *QST*, August, 1972, pp. 36-43.
2. Alton & Groe, "Computer Calculation of the Far-Field Radiation Pattern of an Antenna Array," *IEEE Transactions of Broadcasting*, Vol. BC-16, No. 1, March, 1970.
3. George S. Oshiro, "Exclusive-OR ICs Serve for Phase-Locking Tasks," *Electronics*, June 22, 1970.
4. Norman Tweit and Wes Vincent, "RF Linear IC Squares High-Frequency Sine Waves," *Electronics*, October 12, 1970.
5. Doyle Strandlund, W8CGD, "Amateur Measurement of R-jX," *QST*, June, 1965, p. 24.

ham radio

(PHOTO COURTESY OF THE SAN DIEGO EVENING TRIBUNE)

How to stay on the air WHEN AN EMERGENCY STRIKES...

...with a fully solid-state transceiver from SWAN.

That's right! Even if your area is struck with a massive electric power failure you can have full amateur band coverage, with up to 200 watts P.E.P. available, to relay emergency information or to call for help. A 12 volt battery, just like the one in your car, is all you need to operate a Swan solid-state transceiver.


Here's all you do to set up a home emergency station. Simply purchase a 12 volt automobile battery. Connect a Swan solid-state transceiver to the battery and your antenna. That's it! The station is ready to go on the air at any time — able to operate for several days — if necessary. Prepare now, to communicate in any emergency situation!

HINT:— Add a battery charger to a battery-powered solid-state home installation and you can regularly operate more efficiently. It'll cost less than most A.C. power supplies. Even Swan's big SS-200 transceiver takes very little power drain from a battery — less than 500 ma on receive and averages about 6 amps when transmitting on single sideband (as low as 0.8 amps average, to transmit SSB on the SS-15).

Another thought — a solid-state mobile installation can mean a savings of up to \$140.00 when compared to the special A.C. power supplies that must be purchased for mobile use of conventional tube-type transceivers.

Now is the time to join the new age of

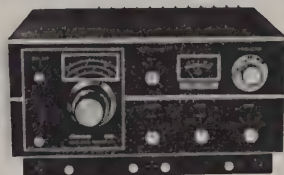amateur radio electronics by selecting a new fully solid-state Swan transceiver. Every model of the "SS" series features: NO TRANSMITTER TUNING, INFINITE VSWR PROTECTION, CONTROLLED NOISE BLANKING, BUILT-IN VOX, and more. Just 10% down will put an all-solid-state rig in your ham shack, when you use your Swan Revolving Credit Service account. Why wait? Order yours now!!



SWAN
SS-100

Gentlemen:

Please send me a

- ☐ SWAN SS-15 (15 watt P.E.P.)
@ \$579.00
- ☐ SWAN SS-100 (100 watt P.E.P.)
@ \$699.00
- ☐ SWAN SS-200 (200 watt P.E.P.)
@ \$779.00
- ☐ Full payment enclosed. (Calif. residents add 5% sales tax.) I will pay shipping C.O.D.

- ☐ 10% down payment enclosed. Charge balance to my Swan Revolving Credit Service Account

- ☐ Send order C.O.D.
- ☐ Send latest catalog.
- ☐ Please send a Swan Revolving Credit Service account application form.

Mail to:



SWAN
ELECTRONICS


A subsidiary of Cubic Corporation

305 Airport Road • Oceanside, CA 92054

Name _____ Call _____

Address _____

City _____ State _____ Zip _____

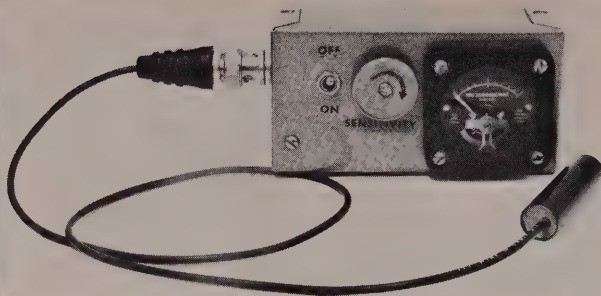

sensitive rf indicator

This high-gain
amplifier circuit,
when used with
a DyComm Sniff-It,
provides a sensitive
rf indicator —
the Snuff Box

D.L. Sprague, WB9DNI, 78 Paddock Street, Aurora, Illinois 60538

For some time now DyComm has offered an rf probe called the Sniff-It. This small black cylinder with a coax tail has proven to be quite useful in providing a dc current relative to an rf field. The manufacturer's instructions provided with the unit describe specific results of various applications, but do not provide general specifications such as frequency and power response. DyComm also has a very tight security rein on the contents of this midget marvel. So we approach the device as the classical black box. . . cylinder.

Art Householder, K9TRG, of Spectronics asked me to design an inexpensive relative rf indicator to be used with the Sniff-It, and the Snuff Box described here is the result of that request.

The Snuff-Box/Sniff-It combination is a portable rf level indicator useful in tracing problems in transmitters or receiver oscillator chains. By making the coax guide, also described in this article, leakage points in coax can be detected.

circuit description

The Snuff Box consists of a continuously variable gain dc amplifier feeding a five-volt meter. The gain can be varied from 1 to slightly more than 100. A μ A741 frequency compensated operational amplifier comprises the active element. This device is both reliable and inexpensive. Because the 741 is internally compensated, an external frequency com-

pensation network is not required. The dual inline package (DIP) was selected for the prototype. If desired, the metal can package can be substituted. However, the pin configuration given in **fig. 1** is for the DIP only.

The 741 IC is operated in the non-inverting mode to provide a relatively high input impedance. The input is protected by CR1, is a 5.6 V zener diode. R1 and R2 form a load for the Sniff-It with R1 acting to limit the input current when CR1 conducts. R2 was chosen by experiment as the approximate resistance for the desired power transfer. R3 and R4 form the negative feedback network which determines the gain of the op amp. Gain is represented by A

$$A = \frac{R3 + R4}{R3}$$

R5 and the 1-mA meter constitute a zero to 5 volt meter. The value of R5 is selected so that its resistance, along with the meter's resistance, will equal 5000 ohms. There are numerous articles available which explain how to determine a meter's internal resistance. The 741 requires a bipolar power supply. I found the simplest to be two matched batteries.

construction

In this project, the meter is the prime consideration. Small 1-mA meters are very common junk box items, as this style was a favorite with military designers for many years. I recommend that the meter selected be of the ruggedized style. Many portable devices with non-ruggedized meters get quickly returned to the junk box!

Select the box for the meter. The prototype was built in a 2 x 4-inch Minibox. Layout is not critical. It's a good idea to use a socket for the $\mu A741$, as unsoldering 14 pins is a pain.

As purchased, the Sniff-It is not equipped with a connector. I suggest either a phone plug or a BNC type. Both are quick disconnect, and provide adequate shielding for low levels of dc current. However, the BNC is superior for high rf fields.

coax guide

Take two 3/8-inch cable clamps and cut as shown in the photograph. Pop rivet or bolt the two clamps together back to back, keeping them at right angles to one another. The Sniff-It will fit into one, leaving the second open to guide along RG-58/U coaxial cable.

operation

Let's examine the sensitivity of the Snuff Box. With R4 fully shorted, the

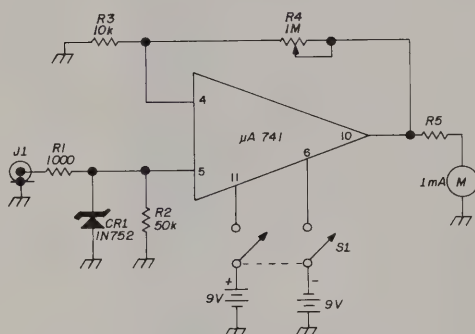


fig. 1. Circuit for the Snuff Box. DyComm Sniff-It is plugged into J1.

$\mu A741$ produces unity gain. Therefore, 5 volts across R2 will cause a full-scale deflection of the meter. This means that a current of 100 μA is being produced by the Sniff-It. Now, with a gain of 100, it will take only 1 μA for the highest setting of R4 to produce a full-scale reading. This sensitivity was sufficient for me to find the oscillating receiver crystal in my Regency HR-2.

DyComm's instruction sheet has many suggestions for the applications of the Sniff-It. The Snuff Box is ideal for most of these applications.

This unit is an invaluable aid in checking for rf on power supply leads, leaks in transmitter and antenna tuner cabinets, or for neutralizing detection. When peak-ing tuned circuits in a unit, the Sniff-It/Snuff Box is much handier than a grid dipper if you are just looking for maximum indications, since no tuning is necessary.

ham radio

The BEST CW in the world!

comes from Keyers by



MEMORY-MATIC 8000 Deluxe Keyer

The unquestioned leader in the keyer field. Up to 8000 bit easy-to-use memory capacity allows storage of up to eight complete message sequences. More features than you've ever imagined. The contesters and traffic handler's dream keyer.

Complete details in our exciting free catalog.

MEMORY-MATIC 500B Keyer

Easy-to-use 500 or 800 bit read/write memory offers complete flexibility to automate your CW station the modern Data Eng. way. Keep up with the winners with this exciting keyer. Send for full details.

Sh. wt. 4 lbs. with 500 bit memory \$198.50
with 800 bit memory \$219.50

SPACE-MATIC 21-B

The Switchable Keyer. It's up to eight-keyers-in-one. Use the switches to make this your very own personal keyer, both today and tomorrow. Add such features as dot dash memory or adjust spacing with the turn of a switch. Completely versatile, completely perfect with everything you will ever want. Full details in our catalog.

Sh. wt. 4 lbs. \$89.50

CRICKET 1

At last — a popularly priced IC keyer with more features for your dollar than all others in its price range. Fatigue-free sending with clean, crisp CW at all speeds.

Sh. wt. 3 lbs. \$49.95

FEATHER TOUCH KEY

Replace that mechanical key with our new electronic key. Go modern with Feather Touch the electronic key that detects the mere touch of your finger. Develop a truly professional fist.

Sh. wt. 2 lbs. \$22.95

adapted to MM-8000 & MM-500B \$27.95

MST-60


Synchronize your Meteor, Tropo, or Moon Bounce communications with WWV for transmission at 15, 20, 30 and 60 second intervals with this precision Meteoric Scatter Timer.

Sh. wt. 2 lbs. \$49.50

Send for FREE Catalog ● 5 Year Guarantees

Send today or use "Check-Off" to get our exciting new catalog describing the most complete line of electronic keying equipment available plus many other exciting accessories for your station.


DATA ENGINEERING INC.

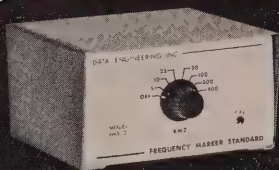

FMS-3

The frequency marker that gives you more. Just right for band edge markers for 160 to 10 meter bands.

Sh. wt. 2 lbs. \$32.95
(less batteries)

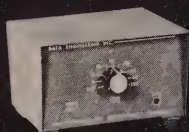

FMS-5

Designed specifically for the FMer. This deluxe frequency standard allows precise calibration of all receive and transmit crystals in the 10, 6, 2 and 1 1/4 meter FM bands. No more off frequency operation with the FMS-5.

Sh. wt. 2 lbs. \$44.50
(less batteries)

Exciting NEW FM Products



TOUCH-TONE PAD

In less than 15 minutes you can convert your portable transceiver to Touch-Tone operation.

TTP-1K Complete Kit \$34.50
TTP-1 Touch-Tone Pad \$44.50

Assembled in attractive case for home or mobile use. Complete PTT operation with one second transmitter hold. Built-in monitor.

TTD-2K Complete Kit \$34.50
TTP-2 Assembled \$44.50

MINI-PAD One half standard size Assembled \$44.50
Kit \$34.50

TOUCH-TONE DIALER

The electronic Touch-Tone dialer for home and car. It's safer and more accurate to use than a pad. Memory includes Access Code plus five phone numbers. Numbers easily updated. Built-in monitor. Complete PPT operation with transmitter hold.

TTD-4K Complete Kit \$49.00 TTD-4 Assembled \$59.00

REPEATER ID

Highly stable oscillator for automatic timing. AC or DC operation. ROS provides for more than 25 characters, more than necessary for DE "any call" RPT. AUX is automatically added to ID if desired when main power is lost. Tone Burst operation available.

ID-101K P.C. Board Kit \$49.95
ID-101 P.C. Board, Wired and Tested \$69.95
ID-101R Assembled in 1½" rack cabinet \$109.00

TONE ENCODER

Eight pre-adjusted tones. Duration and Output adjustable. PLL circuitry for extreme stability. Choice of continuous or Tone burst operation. Tone burst operation requires no batteries. Easy to install. Includes three special single or dual tones.

TEB-K Complete Kit \$31.95
TE-8 Tone Burst Encoder (1800, 1950, 2100, 2250, 2400, plus any 3 single or dual tones above 1200 Hz.) \$39.95

AUTO-PATCH CONSOLE




This mobile or home console includes all the features you need for complete auto-patch operation. A Touch-Tone Pad; an automatic dialer for sending one access code plus five Touch-Tone phone numbers; a single/dual tone burst encoder adjusted to your choice of frequency above 1200 Hz, and a built-in monitor. Complete PTT operation with one second transmitter hold.

APC-4K Complete Kit \$84.50 APC-4 Assembled \$98.50

TONE DECODER

Versatile single/dual tone decoder. PLL circuitry for extreme stability. 1 amp output relay can be reset automatically or manually. Monitor position. Adjustable sensitivity. Internal strap selects single or dual tone operation.

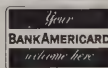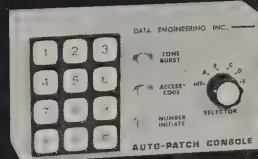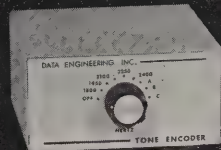TD-2K Complete Kit \$31.95
TD-2 Single/Dual Tone Decoder \$39.95
(Specify any freq. above 1200 Hz)



Ravensthorpe Industrial Park, Springfield, Va. 22151

5554 Port Royal Road • 703-321-7171

2-METER PREAMP

Specially made for both OLD and NEW receivers. The smallest and most powerful preamp available. Provides 20dB gain to bring in the weakest signals.

Sh. wt. 4 oz. \$9.50 kit
\$12.50 wired

PAD-PULSER


Now you can also obtain pulsing operation from your Touch-Tone Pad. Convert Touch-Tone frequencies to decimal pulses at 2805 Hertz with just a flip of a switch. Option can be added to TTP-2/K, TTD-4/K and APC-4/K.

PP-12K P.C. Board Kit \$22.95
PP-12 Assembled \$29.95

TOUCH-TONE DECODER

A highly reliable twelve digit decoder with input protection, and PLL circuitry for extremely stable operation. Heavy duty output relays, small size, plug-in circuit board. All these major features at an UNBEATABLE price.

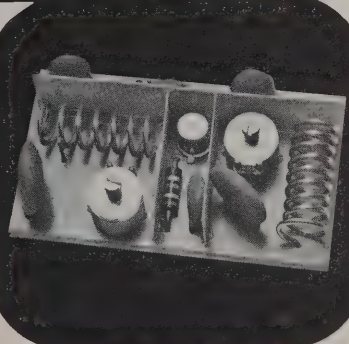TTD-12K P.C. Board Kit \$89.50
TTD-12 Touch-Tone Decoder \$129.50





simple regenerative WWV receiver

This low-voltage
WWV receiver
tunes from
4.7 to 15.5 MHz,
and is powered by
one 1.5-volt
flashlight battery

Courtney Hall, WA5SNZ, 7716 La Verdura, Dallas, Texas 75240

The receiver described here has a frequency range of approximately 4.7 to 15.5 MHz; this covers three of the WWV frequencies as well as the 20- and 40-meter amateur bands and several foreign broadcast bands. Its simplicity and economy are enhanced by the fact that it operates from a single flashlight battery.

I chose a regenerative detector because it will perform well with a-m, CW, or ssb. Regenerative detectors use positive feedback to obtain large amounts of amplification and very high Q in the input tuned circuit. As feedback is increased, Q and gain increase until a point is reached where the detector goes into oscillation. When oscillating, the detector provides its own bfo signal. All of the selectivity is obtained in the single front end tuned circuit, thus cross modulation and/or intermodulation interference is very low because unwanted signals don't reach the first transistor.

battery power supply

By designing the receiver to operate from a single flashlight cell, a consider-

able saving in battery expense has been achieved; also, battery changes are required much less frequently than if the popular 9-volt transistor radio battery is used.

Table 1 shows data extracted from battery performance curves in the Burgess Engineering Manual, 1967 edition. Only ordinary carbon-zinc batteries are shown. End-of-life voltage in each case was arbitrarily chosen to be 1.2 volts-per-cell, and all data is for continuous discharge at 70° F.

In comparing batteries, the important parameter is capacity in milliampere-hours; the 9-volt battery will supply 1 mA for 400 hours, but the D cell will supply 1 mA for 3200 hours, eight times as long as the 9-volt battery.

table 1. Carbon-zinc battery performance.

battery type	load current (mA)	life (hours)	capacity (mA-hours)
9 volt	1	400	400
AA	5	180	900
C	5	330	1650
D	20	160	3200

When you consider that the 9-volt battery may cost twice as much as the D cell, the cost-of-operation factor is about 16 to 1 in favor of the D cell. The above rational assumes the 9-volt circuit would draw the same current as the 1.5-volt circuit. If, however, the two circuits were designed to have the same output impedances, the 9-volt circuit could draw about six times as much current, making the cost-of-operation factor 96 to 1 in favor of the D cell.

headphone power

I used a subjective listening test to determine whether a 1.5-volt circuit could drive a pair of 2000-ohm headphones. The phones were connected to a 1-kHz audio oscillator, and an ac voltmeter used to measure the voltage across the phones. **Table 2** shows the results. Since 300 mV rms is about 0.85-volt peak-to-peak, and since an amplifier hav-

ing a 1.5-volt supply should be able to have an output swing of 0.85-volt peak-to-peak, there should be more than enough power available to drive the phones.


table 2. Headphone loudness vs supply voltage.

headphone voltage (mV rms)	power to headphones (microwatts)	observed loudness effect
2	0.002	detectable
30	0.45	comfortable
100	5.0	desirable
300	45.0	excessive

threshold howl

A common trouble in designing regenerative detectors is threshold howl. This is a loud audio-frequency oscillation heard when the regeneration control is advanced to the point of rf oscillation. It is caused by the circuit squegging or going in and out of rf oscillation at an audio rate. This is similar to the action of a superregenerative vhf detector which starts and stops its rf oscillations at a rate somewhere around 100 kHz.

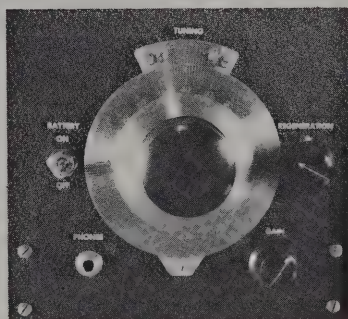According to Terman,¹ the tendency to have intermittent oscillations is reduced by decreasing the R-C time constants associated with the bias network. I had no trouble with threshold howl after I reduced the collector and base resistors of Q1 to the values shown in **fig. 1**. The



WWV receiver is built into an old Bud enclosure that was picked up at a swap-fest.

22-pF base coupling capacitor of Q1 should not be increased.

circuit

Fig. 1 is a schematic of the complete receiver. Battery drain is less than 1.5 mA.

Measure the dc voltage between the collector of Q4 and ground with a 20,000 ohm-per-volt vom or a vtm. The audio gain should be set at minimum for this test, and 10 seconds allowed for the amplifier to stabilize after it is turned on.

electrical stability is improved by mechanical rigidity, and short leads should be used in the detector circuit. The Bud C-973 cabinet, with chassis, and the National type N-2 dial were salvaged from an old vacuum-tube vhf converter I bought at a swapfest for a dollar. The photographs show how the tuning capacitor is mounted to a 1.5-inch aluminum angle and coupled through a flexible coupling to the dial. Not shown is the rf choke and audio amplifier which are mounted below chassis. All detector com-

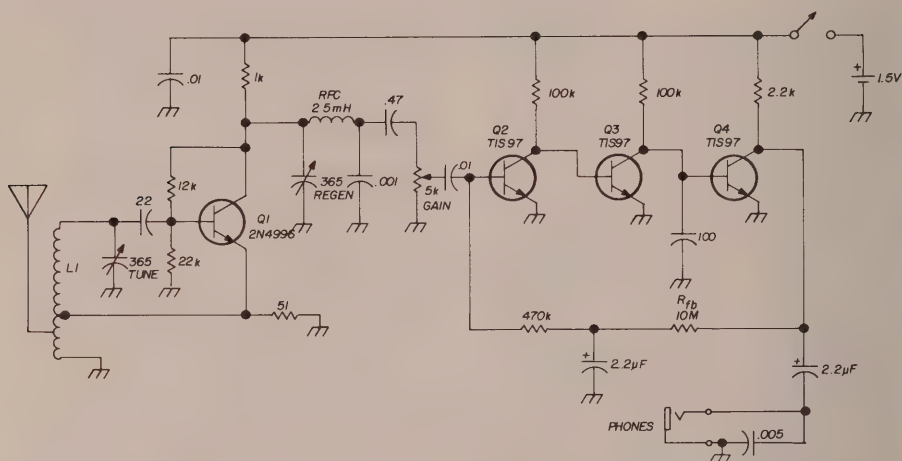


fig. 1. circuit diagram of the low-voltage WWV receiver which tunes from approximately 4.7 to 15.5 MHz. L1 is 3.8 μ H (12 turns, 1½" diameter, 6 turns-per-inch coil stock).

If the voltage is not in the range of 0.75 to 0.85 volt, substitute different size resistors for R_{fb} until the voltage is about 0.8; larger value resistors will raise the voltage, and smaller ones will lower it.

The large coil stock was used to make it easy to experiment with tap positions. Antenna coupling is varied by means of a minigator clip from the antenna terminal which can be clipped to the coil at any point. The emitter tap is one turn from ground. A 51-ohm resistor from emitter to ground was necessary to ensure that oscillation could be stopped at all frequencies; it also stabilizes the circuit against antenna impedance variations.

There is nothing critical in the construction of the receiver, but, as usual,

ponents are mounted to solder terminal strips, and the audio amplifier is assembled on a piece of Vectorbord.

Important considerations are the need for a speed-reducing dial because of the high selectivity and wide tuning range, and the desirability of a smooth action ballbearing capacitor for the regeneration control. The regeneration setting is rather critical, and anything you can do to make it easier is quite worthwhile. I used Calctro A1-227 variable capacitors for both tuning and regeneration.

operation

Use a fresh flashlight battery; old ones may have developed enough internal resistance to provide coupling between

circuits which results in undesired oscillations.

There will be about a 10-second delay after the battery switch is turned on before anything will be heard in the phones; this is because of the long time constant of the 10-megohm resistor and 2.2- μ F capacitor in the audio amplifier feedback network.

The antenna tap should be set for the best compromise between sensitivity and selectivity. One or two turns from ground is about right for long antennas, but three or four turns can be used with short antennas. If selectivity is poor, move the tap toward ground.

Use only headphones having 2000 ohms, or more, impedance. Advance the regeneration control toward oscillation by increasing its capacitance (this turned out to be counter-clockwise with the variable capacitor I used). When the point of oscillation is reached, a sudden increase in the background hissing noise will be heard; if a signal is within a few kHz of the detector's frequency, a beat note will be heard.

To tune in an a-m station, adjust the tuning dial and regeneration control simultaneously, keeping the regeneration just below the point of oscillation, until the station is clearly heard. There is interaction between the two controls, and some practice will be required to become proficient at tuning. Once the station is tuned in, it may be necessary to back off on the regeneration to eliminate distortion; the selectivity is so narrow at maximum circuit Q that sidebands can be clipped. CW signals should be tuned with the regeneration control set just above the point of oscillation.


With a tuning range of more than 10 MHz on 180 degrees of dial, it is a test of skill to tune in a ssb signal, but it can be done. The regeneration control should be set somewhat higher than for CW, and both tuning and regeneration carefully adjusted until the signal is clear.

High-powered amateur stations nearby can cause overload problems and be heard all across the dial, but this is not unusual,

even with receivers of more sophisticated design. Moving the antenna tap toward ground will help.

conclusion

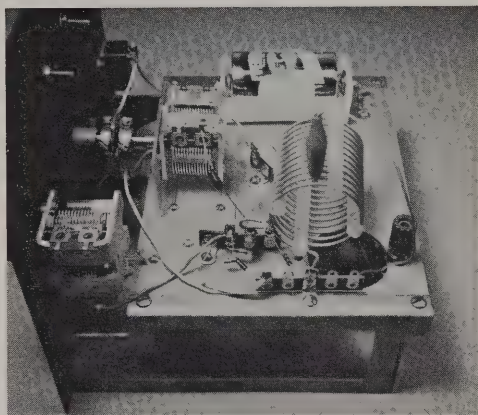I hope the information above will help those who wish to build a simple general coverage receiver which is capable of good a-m performance. My reason for building it was to avail myself of WWV's accurate frequencies, time signals and propagation forecasts. I am well satisfied. Some will consider the critical two-



Construction of the WWV receiver. Audio amplifier is built on perforated board mounted underneath the chassis.

handed tuning procedure a serious disadvantage, but I don't; things that require skill are more fun to do.


To my knowledge, this receiver is unique in that it can give good shortwave performance using a single flashlight battery power supply. Field Day enthusiasts and campers might consider adding a bandspread control for portable hamming. Regenerative receivers aren't as good as direct-conversion for CW and ssb, but they work.

reference

1. F.E. Terman, *Electronic and Radio Engineering*, 4th edition, McGraw-Hill, New York, pp 491-492.

ham radio

Heathkit® 2-Meter FM gear is here!

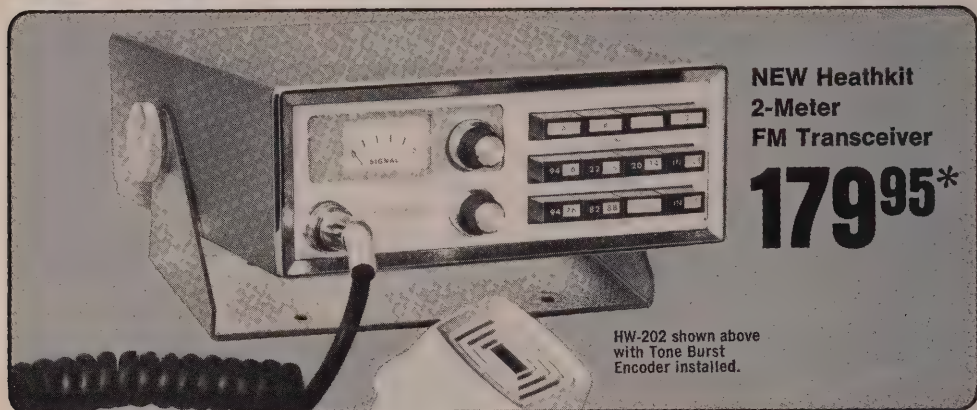

• **All solid-state design** • **Can be completely aligned without instruments** • **36-channel capability** — independent push-button selection of 6 transmit and 6 receive crystals • **10-Watts Minimum Output** — designed to operate into even an infinite VSWR without failure • **Optional Tone Burst Encoder** — mounts inside, gives front-panel selection of four presettable tones

The Heathkit HW-202 compares with the best wired amateur 2M/FM rigs. Plus it has: 36-channel capability via independent selection of 6 transmit and 6 receive crystals. Solid-state circuitry with complete built-in alignment procedures using only the manual and the front-panel meter allow operation over a 1 MHz segment from 143.9 to 148.3 MHz. Removable front-panel bezel permits installation of the new Heathkit HWA-202-2 Tone Burst Encoder.

10-15 watts transmission into an infinite VSWR — indefinitely, with no failure! The HW-202 needs no automatic shut-down — it continues to generate a signal regardless of antenna condition. Transmitter deviation is fully adjustable from 0 to 7.5 kHz, with instantaneous deviation limiting. Harmonic output is greater than —45 dB from carrier. The push-to-talk ceramic microphone supplied has an audio response tailored to the HW-202.

Excellent reception — 0.5 uV or less produces 12 dB Sinad, or 15 dB quieting. Output at the built-in speaker is typically 2 watts at less than 3% total harmonic distortion. The receiver circuitry utilizes diode-protected dual-gate MOSFETS in the front end; an IC IF that completely limits with less than a 10 uV signal; dual conversion, 10.7 MHz and 455 kHz via a 4-pole monolithic 10.7 MHz crystal filter. Image response is —55 dB or better. Spurious response is —75 dB or better.

The Heathkit HW-202 comes with two crystals used in initial set-up and alignment, give you simplex operation on 146.94. Kit includes microphone, quick-connecting cable for 12-volt hook-up, heavy duty alligator clips for use with a temporary battery, antenna coax jack, gimbal bracket, and mobile mount that lets you remove the radio from the car by unscrewing two thumbscrews. The HWA-202-2 Tone Burst Encoder provides four presettable pushbuttons for instant repeater access. Fixed station operation is as easy as adding the HWA-202-1 AC Power Supply. The HA-202 2-Meter Amplifier puts out 40 watts for 10 watts in, and externally it's a perfect mate for your HW-202.

Kit HW-202, 11 lbs., mailable **179.95***

Kit HWA-202-2, Tone Burst Encoder, 1 lb. . . **24.95***

Kit HWA-202-1, AC Power Supply, 7 lbs. . . **29.95***

Kit HWA-202-3, Mobile 2-Meter Antenna, 2 lbs. **17.95***

Kit HWA-202-4, Fixed Station 2-Meter Antenna, 4 lbs. **15.95***

HW-202 SPECIFICATIONS — RECEIVER — Sensitivity: 12 dB SINAD* (or 15 dB of quieting) at .5µv or less. Squelch threshold: 3 µv or less. Audio output: 2 W at less than 10% total harmonic distortion (THD). Operating frequency stability: Better than ±.0015%. Image rejection: Greater than 55 dB. Spurious rejection: Greater than 60 dB. IF rejection: Greater than 75 dB. First IF frequency: 10.7 MHz ±2 kHz. Second IF frequency: 455 kHz (adjustable). Receiver bandwidth: 22 kHz nominal. De-emphasis: —6 dB per octave from 300 to 3000 Hz nominal. Modulation acceptance: 7.5 kHz minimum. **TRANSMITTER** — Power output: 10 watts minimum. Spurious output: Below —45 dB from carrier. Stability: Better than ±.0015%. Oscillator frequency: 6 MHz, approximately. Multiplier factor: X 24. Modulation: Phase, adjustable 0-7.5 kHz, with instantaneous limiting. Duty cycle: 100% with ∞ VSWR. High VSWR shutdown: None. GENERAL — Speaker impedance: 4 ohms. Operating frequency range: 143.9 to 148.3 MHz. Current consumption: Receiver (squelched): Less than 200 mA. Transmitter: Less than 2.2 amperes. Operating temperature range: —10° to 122° F (—30° to + 50° C). Operating voltage range: 12.6 to 16.0 VDC (13.8 VDC nominal). Dimensions: 2 3/4" H x 8 1/4" W x 9 7/8" D.

*SINAD = $\frac{\text{Signal} + \text{noise} + \text{distortion}}{\text{Noise} + \text{distortion}}$

...and here!

NEW Heathkit
2-Meter Amplifier for cleaner
FM copy on the fringe... 69⁹⁵*

40 watts nominal out for 10 watts in —
requires only 12 VDC supply.


Fully automatic operation — with any
2-meter exciter delivering 5-15 watts drive.

Solid-state design — all components
mount on single board for fast,
easy assembly.

If you're regularly working from a fringe area, the new Heathkit HA-202 can boost your mobile output to 40 watts (nominal), while pulling a meager 7 amps from your car's 12-volt battery.

Install it anywhere...in the trunk, under the hood or dashboard. Use it with any 2-meter exciter delivering 5-15 watts drive. Features fully automatic operation. An internal relay automatically switches the antenna from transmit to receiver mode when you release the mike button.

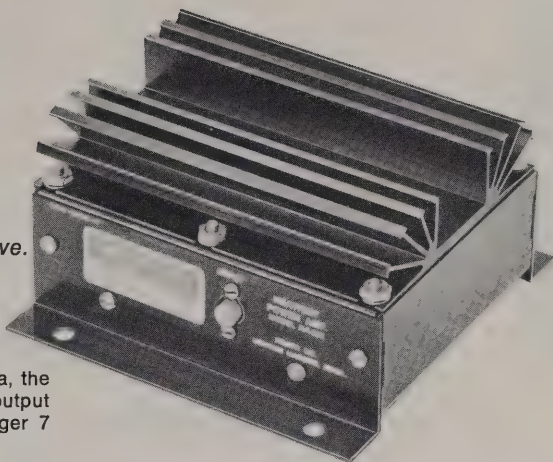All solid-state design features rugged, emitter-ballasted transistors, combined with a highly efficient heat sink, permitting high VSWR loads. Tuned input-output circuits offer low spurious output to cover the 1.5 MHz segment of the 2-meter band without periodic readjustment. All components mount on a single printed circuit board for easy,




4-hour assembly. Manual shows exact alignment procedures using either a VOM or VTVM. And installation is just as simple.

Kit includes transceiver connecting cable, antenna connector. Operates from any 12 VDC system — additional power supplies are not required. Add HA-202 power to your mobile 2-meter rig, and boom out of the fringe. **Kit HA-202, 4 lbs.**

HA-202 SPECIFICATIONS — Frequency range: 143-149 MHz. Power output: 20W @ 5 W in, 30W @ 7.5W in, 40W @ 10 W in, 50W @ 15 W in. Power input (rf drive): 5 to 15W. Input/output impedance: 50 ohms, nominal. Input VSWR: 1.5:1 max. Load VSWR: 3:1 max. Power supply requirements: 12 to 16 VDC, 7 amps max. Operating temperature range: -30° F. to +140° F. Dimensions: 3" H x 4 1/4" W x 5 1/2" D.

...and here!

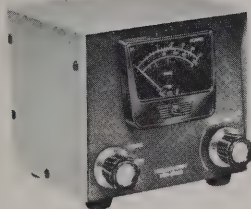New Heathkit
VHF Wattmeter/SWR Bridge ... 29.95*



Perfect tune-up tool for your 2-meter gear. Tests transmitter output in power ranges of 1 to 25 watts and 10 to 250 watts $\pm 10\%$ of full scale. 50 ohm nominal impedance permits placement in transmission line permanently with little or no loss. Built-in SWR bridge for tuning 2-meter antenna for proper match, has less than 10-watt sensitivity. **Kit HM-2102, 4 lbs.**

HM-2102 SPECIFICATIONS — Frequency range: 50 MHz to 160 MHz. Wattmeter accuracy: $\pm 10\%$ of full-scale reading.* Power capability: To 250 W. SWR sensitivity: less than 10 W. Impedance: 50 ohms nominal. SWR bridge: Continuous to 250 W. Connectors: UHF type SO-239. Dimensions: 5 1/4" H, 5 1/4" W and 6 1/2" D, assembled as one unit.

*Using a 50 Ω noninductive load.

See them at your Heathkit Electronic Center —
or fill out coupon for FREE Heathkit catalog

HEATHKIT ELECTRONIC CENTERS

ARIZ.: Phoenix, 2727 W. Indian School Rd.; CALIF.: Anaheim, 330 E. Ball Rd.; El Cerrito, 6000 Potrero Ave.; Los Angeles, 2309 S. Flower St.; Pomona, 1555 Orange Grove Ave. N.; Redwood City, 2001 Middlefield Rd.; San Diego (La Mesa), 8363 Center Dr.; Woodland Hills, 22504 Ventura Blvd.; COLO.: Denver, 5940 W. 38th Ave.; CONN.: Hartford (Aven), 395 W. Main St. (Rte. 44); FLA.: Miami (Hialeah), 4705 W. 16th Ave.; GA.: Atlanta, 5285 Roswell Rd.; ILL.: Chicago, 3462-66 W. Devon Ave.; Downers Grove, 224 Ogden Ave.; IND.: Indianapolis, 2112 E. 62nd Ave.; KANSAS: Kansas City (Mission), 5960 Lamar Ave.; MD.: Baltimore, 1713 E. Joppa Rd.; Rockville, 5542 Nicholson Lane; MASS.: Boston (Wellesley), 165 Worcester St.; MICH.: Detroit, 18645 W. Eight Mile Rd. & 18149 E. Eight Mile Rd.; MINN.: Minneapolis (Hopkins), 101 Shady Oak Rd.; MO.: St. Louis, 9296 Gravois Ave.; N.J.: Fair Lawn, 35-07 Broadway (Rte. 4); N.Y.: Buffalo (Amherst), 3476 Sheridan Dr.; New York City, 35 W. 45th St.; Jericho, L.I., 15 Jericho Turnpike; Rochester, Long Ridge Plaza; OHIO: Cincinnati (Woodlawn), 10133 Springfield Pike; Cleveland, 5444 Pearl Rd.; PA.: Philadelphia, 6318 Roosevelt Blvd.; Pittsburgh, 3482 Wm. Penn Hwy.; TEXAS: Dallas, 2715 Ross Ave.; Houston, 3705 Westheimer; WASH.: Seattle, 221 Third Ave.; WIS.: Milwaukee, 5215 Fond du Lac.

HEATH COMPANY, Dept. 122-4		HEATH
Benton Harbor, Michigan 49022		Schlumberger
<input type="checkbox"/> Please send FREE Heathkit Catalog. Enclosed is \$ _____, plus shipping. <input type="checkbox"/> Please send model(s) _____		
Name _____		
Address _____		
City _____ State _____ Zip _____		
*Mail order prices; F.O.B. factory AM-282		

first wireless

in Alaska

The frigid weather
and frozen tundra
were overcome
to place a
commercial wireless system
in operation
in 1903

Ed Marriner, W6BLZ, 528 Colima Street, LaJolla, California 92037

At the turn of the century the Alaskan gold rush was in full swing. Army forts had been established to look after the gold seekers, and a reliable communications system was needed. A wireless communications system was established, later to be called the Western Alaska Military Communication and Telegraph System, which eventually employed many radio amateurs who as civilians became speed operators on one of the country's fastest CW nets. They were called WAMCATS.

How did it all start? Historically, it was the first communications system on all of the West Coast of America. During the various Alaskan gold rushes, starting in 1898, towns and camps mushroomed overnight, with plenty of tin horn gamblers and other characters (as described in the poems of Robert W. Service) wandering from place to place. By 1900, better communications than messages by boat or dog teams became a necessity.

In 1900 Congress gave the U.S. Army Signal Corps money to improve wireless communication and charged them with the responsibility for a cable line to Alaska and the interior. This cable line was constructed under great difficulty for the poles had to be set into permanently frozen ground. This was the first of many factors which launched the Army into wireless communications.

In 1903 the U. S. Army had strung


wires to St. Michaels, Alaska, and was faced with the problem of making it to Nome. This meant the choice of going around Norton Sound with a pole line under the worst of primitive conditions or laying a cable which would be carried away by ice each year.

The Signal Corps, by now, had used wireless telegraphy and decided that the last link between the stations at Nome and St. Michaels was to be a wireless one. The entire system consisted of 107 miles via wireless, followed up by 3883 miles of cable to Seattle. This same year, 1903, Dr. Lee DeForest experimented and exchanged satisfactory communication between Fort Safety, Alaska, and these stations which was the final report of the project which started back in 1899.

Leading up to the Alaskan Wireless Network was a report by the Chief Signal Officer who, in 1899, announced that the Signal Corps had devised a system of wireless telegraphy. This was the first publicly operated network in America. Improved in detail, it worked successfully over limited ranges between the harbor fortifications for which it was planned. Recognizing, however, that rapid advances were sure to be made by civilian experts, the Chief Signal Officer decided to adhere in this matter to his general policy. This meant that experimental work would be carried out by the Signal Corps only under those conditions where there wasn't any easy recourse to the commercial and industrial establishments of the United States.

Owing to repeated failure of several wireless telegraph companies to furnish a reliable and satisfactory system of wireless telegraphy in Alaska over a distance of 100 miles, the Chief Signal Officer decided in 1903 to have all existing systems examined with reference to their practical qualities. He decided to obtain by elimination, substitution or invention some system for Army use which would result in the reliable and successful transmission of messages.

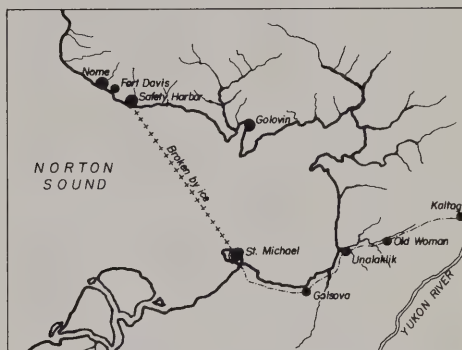The farsightedness of the Chief Signal Officer had already accumulated information and instruments which facilitated the solution of the problem. In addition to the systematic collection of all published data on wireless telegraphy, no efforts had been spared to supplement these by obtaining information from various inventors and experimenters. In addition,



Map showing the wireless circuit between Nome and Fort St. Michael, Alaska, a distance of 100 miles. This circuit was put into operation by the U.S. Signal Corps in 1903 to replace the cable which was washed out by ice every year.

the Signal Corps purchased sample instruments and installations pertaining to every system that seemed worthy of test where a title to the instrument could be obtained for a reasonable price. In this way they acquired essential parts of important systems. Experimental work in wireless telegraphy had also been done by Maj. Samuel Reber, George O. Squier and Edgar Russel, all Signal Corps people, but none of these officers were available for assignment to the work.

For experimental work in connection with perfecting a permanent plant, Capt. Leonard D. Wildman, a graduate of Stevens Institute of Technology, who had displayed resourcefulness in various phases of field duty, was selected. With full authority to call on Major Reber and Capt. Russel for advice, the accumulated data and instruments were turned over to

Capt. Wildman, who began his work by testing the capacity and efficiency of the Braun-Halske wireless transmitter, a duplicate of the plant which operated successfully during the German maneuvers. While this transmitter was not unsuccessful, its maximum capacity for transmission of messages over 63 miles was not entirely satisfactory.

In addition to determining the best type of field wireless apparatus suited to the Army, he was particularly charged with the setting up of a permanent wireless plant which should be able to work successfully over distances exceeding 100 miles.

The chosen field of operation was between Fort Wright, Fisher Island, and Fort Schuyler, New York, 97 miles apart, of which 20 miles was across land. The use of these forts was a factor in the national defense as it established a wireless system over which, in times of great disturbance, a message could be quickly exchanged between the outlying defenses of New York.

With these ends in view, experiments were carried on under Capt. Wildman's personal supervision during the latter part of the year with instruments purchased from the Lodge-Muirhead Wireless Telegraph Company of Great Britain, the Brau-Siemans-Halske Wireless Telegraph Company of Germany, the National Electric Signal Company of Washington, D.C., and from the DeForest Wireless Telegraph Company of New York.

In addition to the instruments furnished by the above companies, experimental apparatus was purchased by the Chief Signal Officer from time to time. Comparative tests were also made between all receivers, responders and coherers on the market, as well as with many different types of special equipment.

Notwithstanding the popular idea that wireless telegraphy over great distances was an accomplished commercial fact, *none* of the systems investigated proved satisfactory for Army use. (Have times changed?) Wireless telegraph systems seemed to have been developed by their

inventors in the laboratory for their own use rather than to electrical and mechanical standards in which a reliable piece of equipment could be placed on the commercial market.

After an investigation of the existing systems, Capt. Wildman formulated, with the approval of the Chief Signal Officer, the following changes as being necessary for practical military uses:

1. Eliminate the necessity for an absolute electrical ground.
2. Construct all parts of the apparatus so that in case of the failure of any part, that part can be replaced without elaborate machinery by intelligent unskilled labor. Even in those days they had trouble getting technicians.
3. Replace all adjustments which require a knowledge of mathematics, or experience in manipulation by lettered dials or definite switch positions so that highly skilled operators would be unnecessary.
4. Reduce the necessary height of the antenna wires.
5. Produce a receiver which would not only receive the message intended for it, but which could, by adjustment, also receive any electromagnetic wave.
6. Eliminate disturbances due to atmospheric or static electricity.
7. Avoid, as far as practicable, all dangerous high-potential currents at points where there was a possibility of danger to employees.
8. Provide devices which would protect the instruments and machinery from destructive potentials.
9. Avoid, as far as possible, the use of patented devices and the consequent payment of large royalties.
10. Devise a system which could be easily transported in time of war and which would be capable of transmitting messages under all climatic and topographical conditions.

Extended tests were made on the DeForest System which in its original and earlier forms was successfully operated during the Army and Navy maneuvers in 1902 on Long Island Sound. This was the first time the Signal Corps applied wireless telegraphy to military purposes. During these tests the DeForest system barely covered the Schuyler-Wright course. Under the most favorable conditions a signal could be exchanged successfully, but when there were nearby interfering stations, signal exchange was impossible.


Undismayed by the situation Capt. Wildman applied himself to the problem of supplementing and improving the system, to the point that he solved the problem as far as the needs of the Signal Corps were concerned. His improvements were formulated and patented equally in the interests of the United States, to whom the patents were assigned, and of the inventor.

Although the Signal Corps system was not perfect, it was better than any system previously tried. It was not absolutely unbreakable, it could not be operated by men of a low order of intelligence, and it was not entirely free from interference from nearby stations, nor could it be operated during heavy thunderstorms. Although, from the looks of the tests, it did not meet many of Capt. Wildman's specifications, the U.S. Army was eager to give it a try in Alaska. A good substitute for a good electrical ground had been found, the operations and adjustments were simple enough, there was only one place within reach of the operator where there was a destructive potential, and the equipment was decided to be repairable enough.

Messages during the tests were sent daily in great numbers over the ninety-seven mile path for five weeks without any apparent deterioration in apparatus or machinery. The experiments furnished a large amount of accurate and valuable data on placement of antenna poles, their rigging, construction, dynamos and their design, transformers and their durability in moist weather, induction coils and

their action, the various methods of tuning the antennas to each other, and to the closed oscillating circuits by which they were fed. The tests proved very valuable.

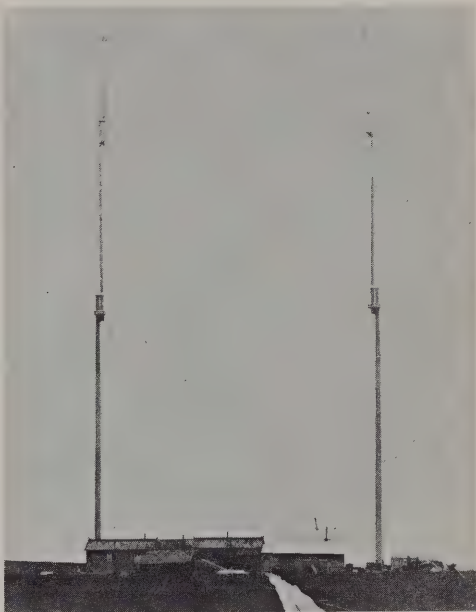With the exception of the DeForest receiver, the Signal Corps system had no patentable devices other than those invented and designed by the officers and



Old wireless telegraph station at Fort St. Michael, Alaska. (Photo courtesy U.S. Signal Corps)

enlisted men of the Signal Corps. As usual, the general public recognized that they had been taken in by the extravagant claims of wireless telegraph experimenters. The public would have to wait for experience alone to prove whether the devices adopted by the Signal Corps performed properly when transferred from a temperate climate to places like Alaska where they had to be operated and maintained by unskilled labor in an unfavorable environment.

It appeared for certain, however, that for Army uses this system was better than anything previously available on the market. Time might disprove the utility of

some of the features which seemed promising, but the Army felt it was an advance over other wireless systems then in use.

Capt. Wildman was about to tackle the job of installing a communications system in the cold wilds of Alaska, and acknowledged his indebtedness to Major Reber and Capt. Russel for valuable advice and assistance. Special commendation is due Capt. Wildman for the persistent and skillful manner in which he contributed to the efficiency of the Army in perfecting the Signal Corps system of wireless telegraphy. The improvements were largely his own devices. Two patents were obtained by him for wireless inventions and were assigned to the government. He went on to Alaska, completed his task and wrote the following report to the Chief Signal Officer in 1903:

wireless telegraphy

"The system of Wireless Telegraphy devised by the Signal Corps of the Army in 1899 has been improved in details, but its range of operation is limited. It was deemed advisable to stop experimental work along these lines pending the development of this science by experts in civil life.

In 1901, however, it became a matter of practical importance to the Signal Corps to establish wireless telegraphy over extended distances. A contract was made looking into the establishment of the wireless telegraph by the Fessenden system across Norton Sound from Nome (Fort Davis) to St. Michael, about 110 miles. The contractors failed, however, to make the installation and the contract was revoked.

In view of the failure of the contractor to install the wireless system across Norton Sound, Alaska, and in order to meet the desire of the Commanding General, Department of Columbia, for telegraphic communication with Fort Davis, the Signal Corps took up this problem and is now engaged in an effort to install a system that shall work from St. Michael to Safety Harbor, near Nome, Alaska, a distance of about 105 miles.

Experimental work with separate and composite systems is being carried out in Long Island Sound by Capt. L.D. Wildman, Signal Corps, with a view to eventually be working between Fort Schuyler and Fort H.G. Wright, a distance of 105 miles, and of which about 10 miles are lowland. For this purpose masts 140 feet high have been constructed, and completed in order to make final tests. Captain Wildman now awaits special motor dynamos and transformers.

Meanwhile to the delay, installations of masts and antennas are now being made at Safety Harbor and St. Michael, so that whatever system proves satisfactory in Long Island Sound, can be utilized in Alaska by 1904 with the suitable sending and receiving apparatus. At both St. Michael and Safety Harbor the permanent plants are now in process of transportation and erection. There are to be at each station two triple masts 200 feet high, between which are to be a suspended fan shaped antenna, consisting of 125 copper wires one-foot apart. The motor power is to consist of a 5 hp gasoline engine and a 3 kW motor dynamo, 60-cycle alternator. At one station will be a transformer, stepping up from 500 to 20,000 volts, and at the other, stepping up from 500 to 25,000 volts. The large Muirhead receivers, which now seem to be the best available type, are to be utilized in this work unless meantime other experiments produce something superior.

Another contract was made with the American-Marconi Wireless Telegraph Company to establish wireless communication between two points in the Tanana Valley where great difficulties were expected in constructing an ordinary telegraph line and in maintaining it satisfactorily, the contract locating the connecting of two points about 164 miles apart with an intermediate station should the Marconi company so decide. It was hoped that this installation would be made by October 1902, but the contractors were not able to install the system last year. They were at work

during the summer of 1903, but to this date no success has been reported. It has, therefore, been necessary for the Chief of Signal Officer of the Army to direct the efficient maintenance of the land lines in the lower valley of the Tanana, such action being imperatively necessary in view of the failure of the wireless installations in a reasonable time.

cycles. This runs through a two-kilowatt transformer, which steps up the voltage across the spark gap. Messages are received by the telephone and DeForest responder."

**Report to the War Department,
Washington, D.C., October 3, 1903**

"While communication is now heard



United States Signal Corps station FD at Nome, Alaska, 1903. (Photo courtesy U.S. Signal Corps)

As we stated in the last annual report, the DeForest system of wireless telegraphy was utilized during the Army and Navy maneuvers on Long Island Sound. This year the same system has been used to replace a broken cable in New York Harbor, between Forts Wadsworth and Hancock, and it has worked most satisfactorily over this distance of 12 miles. In this system a motor dynamo of one kilowatt capacity, driven by the power of the post plant at 110 volts, produces an alternating current of 500 volts at 60

regularly by telegraph between the civilized world and the Yukon Valley westward to St. Michael, yet restoration of communication with Nome has so far proved impractical. The cable between Nome and St. Michael was so badly injured by ice, some 40 miles of it having been carried away, that its repair meet the urgent recommendations of the Commanding General, Department of Columbia. Efforts are being made, with prospects of success in 1904, to establish communication by wireless telegraphy

between St. Michael and Nome across Norton Sound, Alaska, a distance of 108 miles."

**October 4, 1904, from
Capt. Wildman**

"The Signal Corps wireless station at Nome could communicate with a similar station on the Kamchatka Coast, but the infertile and sparsely inhabited country

through that section, and it became necessary for the Chief Signal Officer of the Army to undertake through the officers and men of his Corps, a wireless installation across Norton Sound, and work commenced along two lines: First, to install those available and then perfecting the system later. Second, as the short navigable season of four months in Norton Sound rendered it impracticable to



Inside the Signal Corps station FK at Circle City, Alaska, 1909. (Photo courtesy U.S. Signal Corps)

thence to the nearest Russian station of Nikolaevsk would render any such enterprise unlikely should it be suggested. As has been stated in previous annual reports, efforts to establish a wireless system across Norton Sound and in the valley of the Tanana, awarded to different companies under public proposals, failed entirely.

The contract to establish communication was abandoned in its primary stages in one case, while in the other the efforts proved fruitless after two or more years trying to construct a permanent line

carry on experimental work in Alaska, it was decided to establish two stations in connection with the coast defenses of the United States, where they would have a permanent value, and after devising a successful typical plant, transfer its sending and receiving apparatus to Alaska."

The arrangements for the temporary plant were made under the general directions of Major Russel, whose special and important duty in connection with the Alaskan cable installation left him but scant time for arrangements, whose executive duty must necessarily be carried out

2,000 miles away by an assistant not under his personal observation.

In the late summer of 1903 the Norton Sound base was established. At Safety Harbor and St. Michael there were built portable houses, in which were installed engines, batteries and wireless instruments, supplemented by two masts at each station 210 feet high, between which were suspended fan-shaped antennas. These poles, the highest ever erected on the Pacific Coast, and the antenna were installed through the resourcefulness and professional skill of Mr. R.D. Ross, a civil engineer employed for this purpose.

Unfortunately, part of the wireless material failed to reach St. Michael because the steamer it was on, the *Meteor*, was disabled enroute. First Lt. A. T. Clifton, with a selected force of signal-men familiar with wireless work, jury-rigged instruments through which meager wireless signals were exchanged during the winter.

Meanwhile, experimental work was carried on in Long Island Sound by Capt. Wildman with separate and composite systems. He eventually devised a composite plant, originally based on the DeForest system, but largely modified by inventions of his own. This plant worked with great success between Fort Wright and Fort Schuyler New York. The transfer of the wireless equipment from Long Island Sound to Norton Sound was accomplished by Capt. Wildman during the next summer. The method of installation was such that the installation was easily made.

Capt. Wildman, at St. Michael, and Sergeant Treffinger, at Safety Harbor, installed their respective systems in less than two days. Capt. Wildman reported that the wireless material was landed and delivered at St. Michael by noon of August 4, and said:

"At 9 o'clock AM on the 6th, complete messages were exchanged, and the telegram from me at Safety Harbor was released and set forward. No serious trouble of any kind was experienced and every part of the machinery worked in a

perfectly satisfactory manner. Since that time we have been pushing the machinery about 20% overloaded in order to see if it could be broken down. The signals are fine and louder than I have ever heard them at either the stations when at Schuyler or Wright. The operators have no difficulty in reading the messages while the relay is working in the same room and with the engine running in the

table 1. Callsigns of some of the early U.S. Army Stations in Alaska.

FB	Fairbanks
FD	Nome
FE	Mouth of the Yukon
FG	Fort Gibson
FK	Circle City
FM	Ft. St. Michael
FP	Petersburg
FQ	Ft. Egbert
FX	Ft. Worden

next room and men walking about and talking in an ordinary voice anywhere in the house."

On August 17, 1903, the Nome station was thrown open for commercial business with the rest of the world, and the wireless section of the Alaskan Telegraph System was an everyday adjunct of the electrical appliances of the twentieth century. It daily transmitted the entire telegraphic business of the Seward Peninsula. In one afternoon 5000 words were exchanged between Safety Harbor and St. Michael.

Through the professional skill of Capt. Wildman and his subordinates, the Signal Corps had started operating the longest wireless section network of any commercial telegraphy system in the world. Some of this early equipment was still functioning as late as 1922, in Craig, Alaska. The old 3-kW transmitter was still run by the gas engine, and the transformer, glass-plate condensers, straight open spark gap with cup-like electrodes and plain helix were still going after all those years. Wireless proved itself easier to maintain than telegraph wires.

ham radio

NEW!



**Your finest discount antenna
and equipment supplier.**

Beat inflation.

Save time and money with mail order.

- NAME BRANDS
- **Savings up to 20%**

WRITE FOR CATALOG

ANTENNAS

TOWERS

TRANSCEIVERS

ACCESSORIES

Phone (213) 534-"KING"

ANTENNA KING

Box A

Lomita, Calif. 90717

KiNG

SIZED SPECIALS for APRIL

TRI EX HY GAIN ANTENNA TOWER PACKAGE	\$599.00
51 ft. Free Standing Tower W/Base, Hy Gain Super TH6DXX 10/15/20 Beam, 100 ft. ea. RG8 & Rotor Cable Prepaid, HAM-M Heavy Duty Rotor With Brake.	
HAM M HEAVY DUTY ROTOR W/BRAKE	\$ 89.95
RG8-LOW LOSS FOAM COAXIAL CABLE	10¢/FT.
TR44 MEDIUM DUTY ROTOR NO BRAKE	\$ 59.95
HY GAIN TH6DXX 10/15/20 BEAM	\$144.95
SWAN 500CX 550WATTS 5 BAND	Write for our best price
STANDARD 826MA 10 WATT FM 12CH.	Write for our best price
STANDARD C146A 2 WATT HAND HELD 5CH.	Write for our best price
GALAXY GT550A 5BAND 550WATTS NEW	Write for our best price
COBRA MIC, PRE-AMP MODEL 301 NEW	\$ 14.95
REGENCY HR2A 15WATT FM 6CH, MOBILE	Write for our best price
HY GAIN 5/8 WAVE 2METER MOBILE ANT.	\$ 15.95
HY GAIN BN86 3-30 MC, 2KW BALUN	\$ 10.95

("KING-SIZE SPECIALS" ARE PRE-DISCOUNTED FOR YOUR CONVENIENCE)

TAKE THE GAMBLE OUT OF SHOPPING!

Send Us Your Best Quote & We'll TOP It!

ANTENNA KING
Box A
Lomita, Calif. 90717
Phone (213) 534-"KING"

how to make your own printed-circuit boards

Complete directions
on how to make
your own
printed-circuit boards —
a practical
AFSK generator
is included
as an example

Bert Kelley, K4EEU, 2307 South Clark Avenue, Tampa, Florida 33609

Today's solid-state components are small with terminals close together. Often the mechanical support and the terminal pins are one and the same, and printed-circuit construction eliminates the difficulties of wrapping wires around IC pins only a tenth of an inch apart without shorting adjacent pins. PC boards also solve the mounting problem. Wiring then becomes very easy, high parts density is possible with little effort, and the printed-circuit assembly is rugged — not likely to fall apart under vibration or use.

The main requirement is to carefully plan the parts layout on the board. There may be a different approach from the old vacuum-tube days when wiring began when all the tube sockets were mounted often without much planning. But planning actually makes the wiring go faster because once the board is etched, the resistors, capacitors, and ICs almost literally fall in place and the project is finished in a very short time. Making your own circuit boards is not at all difficult if you assemble the material and tools I suggest and follow the following instructions.

tools

Many hobbyists already have the few tools required (see fig. 1). First of all, you

need a tool to cut the circuit board. Phenolic board is brittle and splits when cut by a hacksaw unless it is carefully clamped. If you do much construction work, you will find that a saber saw does a better and faster cutting job and is useful for chassis metal work. You will also need a quarter-inch drill, preferably variable speed.

The drills shown will handle most of the board drilling you will do. I use a no. 60 drill for all IC and transistor leads. IC pins will fit into number-77 holes but I don't recommend them as you might want to remove the component later, and the tight fit only makes the job more difficult. The rest of the drills needed will be in a small drill set. This will cover holes for PC board mounting, transformer mounting, 2-watt resistors, PC pots and the like.

The awl is used to transfer hole markings from a circuit template to the circuit board. This is shown in one of the photos. Crocus cloth is used to smooth the copper side of the board after drilling before application of resist ink.

The soldering iron should have a small tip. A device is shown for removal of solder in case you get solder in the wrong places or want to remove a component from a board. A similar tool is sold by Radio Shack (no. 64-2085). You can also remove solder by using a short length of fresh coax braid as a blotter, but since

there is some risk of overheating the circuit board it is better to equip yourself with the proper tools.

etching stand

For best results an etching stand is necessary (fig. 2). It agitates the solution and gives a uniform, faster etching job. Fig. 3 shows one large enough for almost

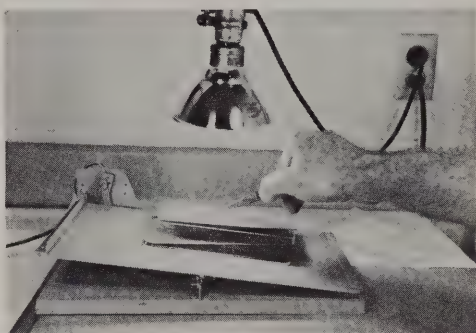


fig. 2. An etching stand is required for best results. Complete construction details are shown in fig. 3. Floodlamp is used to heat the etching solution.

any amateur project. It consists of a 1/8-inch aluminum plate (which may be cut from an old rack panel) upon which the plastic etchant tray is placed. The aluminum plate is supported by two hinges at its center of gravity and is tilted by action of a small electric motor, fig. 4. The base is cut from plywood. The motor may be from four to eight rpm, such as the motors used to operate small animated signs. They can be found in stores listed in the *Yellow Pages* under "Display Fixtures." Try to locate one with the mechanical linkage attached that fits the small diameter shaft. The detailed drawing and photos show construction and mounting of the motor mechanism.

Fasten small aluminum angles or strips to each end of the tilting plate so that large trays will not slide off the stand. Use plastic trays slightly larger than the board you intend to etch; this conserves etchant. Pyrex baking dishes and photo developing trays make good containers for the larger jobs.



fig. 1. A few simple tools are required for building your own printed-circuit boards.

A strong light suspended over the etching tray will speed the etching by keeping both the board and etching solution warm. I use an ordinary clamp-on fixture with a 150-watt floodlamp temporarily clamped to a cabinet above the sink. With this setup a board will be completely etched in less than ten minutes.

etching materials

The photograph shows the etching

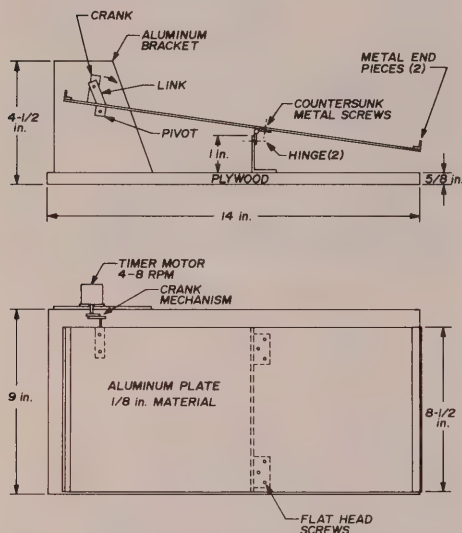



fig. 3. Construction of the printed-circuit etching stand. Sheet of 1/8-inch aluminum can be made from an old rack panel. Motor-drive system is shown on the right. A closeup photograph of the motor drive is shown in fig. 4.

materials that I use (fig. 5). There is a variety of materials available, and this is a matter of preference. I find etching powder more convenient to store and keep several bags on hand. Once mixed, the powder should be used immediately as it will not keep its etching strength. Use only as much as you need and seal the plastic bag so the etching powder will not absorb moisture from the atmosphere. The small bag shown in the photo will do about three 3 x 6-inch boards and costs \$1.00. It is sold by Amidon Associates.*

Of the various substitutes for resist such as paint, marking pens, and masking

tape, masking tape is the most reliable and covers large board areas well. Any substitute should be tested on a sample board. I use a Kepro RMP-700 resist pen which has a fine enough point to mark IC pins easily and effectively resists the action of the etchant.

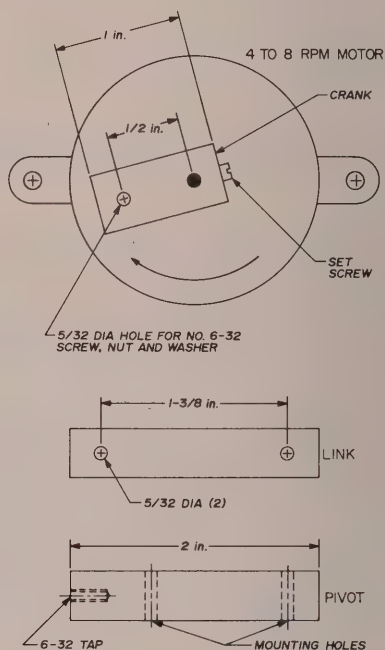The common brown phenolic circuit-board stock, copper clad on one side, is satisfactory for anything except preamps for vhf or uhf. Epoxy boards should be used where better insulation or greater



strength is required. Unfortunately, epoxy boards are relatively hard on drills. Double-sided boards are not needed for most projects and only make layout and component removal difficult. However, double-sided boards are used where an excellent ground plane is necessary.

The circuit-board template is made on a 10-line-per-inch ruled pad. Most electronic components have lead spacings that are multiples of 0.10 inch. One-half watt resistors require 5 spaces, IC pins use

*Amidon Associates, 12033 Otsego Street, North Hollywood, California 91607.

1 space, etc., so layout is facilitated by using this paper. It may be obtained at any stationery store.

procedure

All components for the project should be on hand so they can be checked for size when layout begins. You can save here because the layout may be made to fit the parts you have, rather than in reverse. When you must buy new parts get small ones. There is no advantage, for example, in getting large 600-volt paper capacitors when small 50- to 100-volt units will be more than adequate and save much space. Always pre-test the parts where this is practical. Even experienced counter personnel at supply houses will

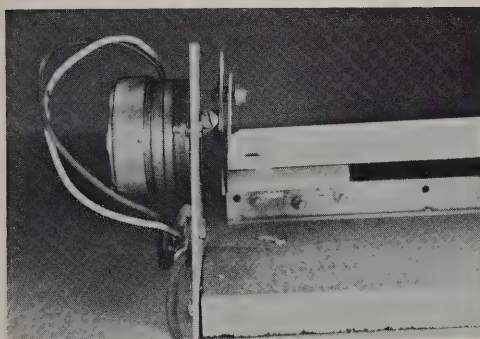


fig. 4. Small electric motor is used to agitate the etching stand.

sometimes misread the color code on resistors. Such errors can be difficult to detect after the parts are mounted on the circuit board.

Lay out the parts on the board roughly as they will appear in the schematic diagram (fig. 7.). Then, consider the layout, move components around in an effort to shorten leads, eliminate possible feedback, space parts more evenly, provide for external connections and reduce trail crossovers. This is the most important phase of the layout procedure. Where possible, refer to the author's original layout or photograph. If this is not given and the project is too complex to visualize as a complete unit, place all the components on top of the proposed

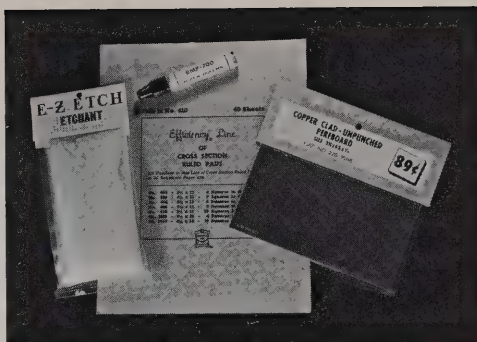


fig. 5. Etching materials are available from a variety of sources.

circuit board and measure the resulting area. This will give the size of the board needed and the size of the enclosure.

Now, select the enclosure, if you have not already done so. Miniboxes are available to fit the majority of small electronic projects. Mount the unetched board inside the enclosure. A mounting method that works well is to use threaded brass spacers like H.H. Smith no. 2372 at each board corner. Another simple mount may be constructed by running extra nuts on long 4-40 or 6-32 machine screws and using these for spacers.

layout

Now, make the detailed layout. Every hole in the circuit board should be shown in this layout and every circuit trail should be penciled in as it will appear on the finished product (fig. 9). It helps to

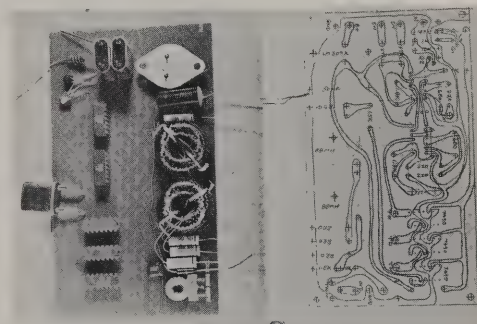


fig. 7. Before starting the printed-circuit layout, lay out the components on the board roughly as they appear in the schematic diagram.

overline a copy of the schematic so that nothing is overlooked. Try to keep trails as direct as practical, and have a minimum of crossovers. On your first few boards you may find it necessary to scrap the first effort and start over, if, during the late stages of the layout a better

arrangements for different packages of the same type IC.

A sample layout is shown for an AFSK generator intended for radio teletype use (fig. 6). The tones are crystal controlled and provide low distortion output. It is not difficult to construct and illustrate

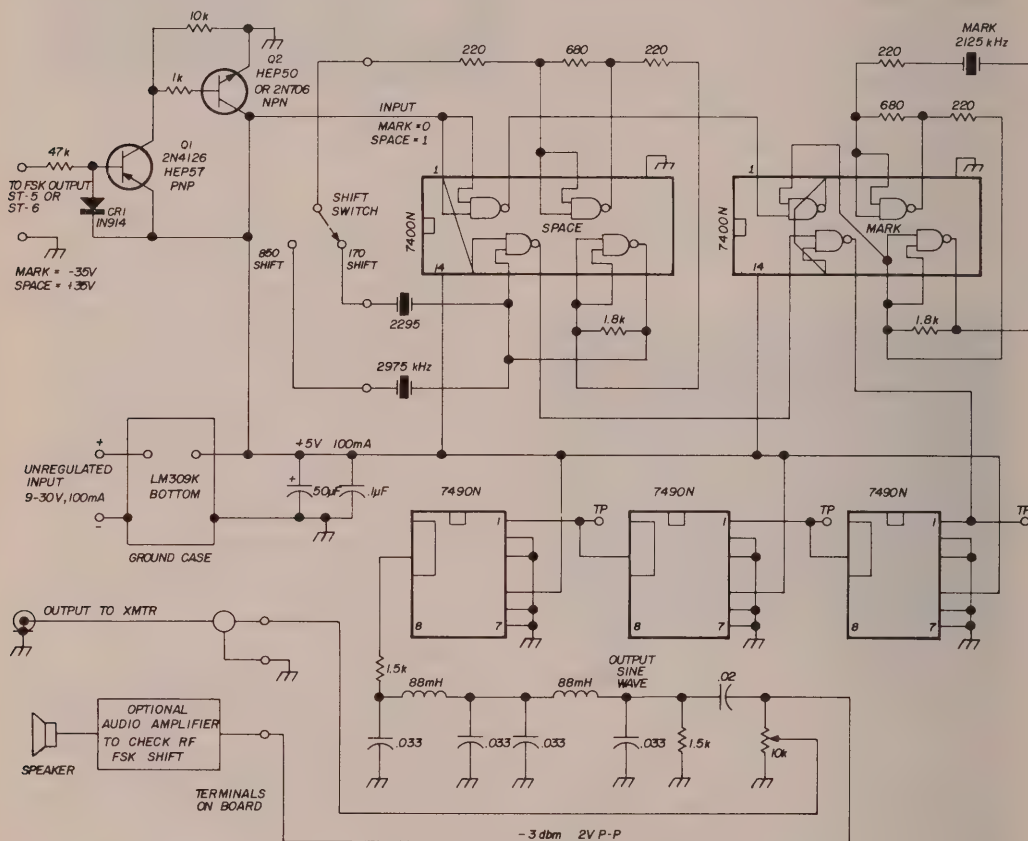


fig. 6. Circuit of RTTY AFSK generator used to demonstrate printed-circuit construction.

approach occurs to you. This is the time to make changes — when they can be easily done.

Keep in mind that the components will be mounted on the board with the leads facing you as you make the template. The pin arrangements for ICs are given as top views, while you will be laying out the pin wiring as viewed from the bottom. Also, be sure you have the pin layout for the particular IC you are using because there often are other pin

the principles of home workshop printed-circuit construction. It will be seen that the board layout closely follows the schematic and only two jumpers have been used. A common ground has been drawn around the outside edge of the board and the metal corner spacers will continue this connection to the case.

A few kinks are useful. The crystals may be made to plug in by using contacts salvaged from crushed miniature tube sockets. They are then spot soldered to

the circuit board. Faucet washers make an effective mount for the 88-millihenry inductors. Thread a long 6-32 screw through one. The taper of the washer will

make secure test points or external connection points at almost no cost.

After checking, the completed template is taped to the copper side of the circuit board and the hole centers are transferred to the copper-clad board with an awl, using light hammer blows, **fig. 10**. When all holes are marked in this way the paper is removed and all marks drilled with a no. 60 drill. Larger holes are then located and re-drilled to size. Remove all drilling burrs with the crocus cloth so the board is smooth and ready for the resist pen. Avoid coarse sandpaper as it will scratch the board and make complete application of resist difficult. The etchant will later eat through these scratches causing hairline opens in the circuit trails.

The final step before etching is application of resist ink. This only takes a few minutes since you follow the trail layout

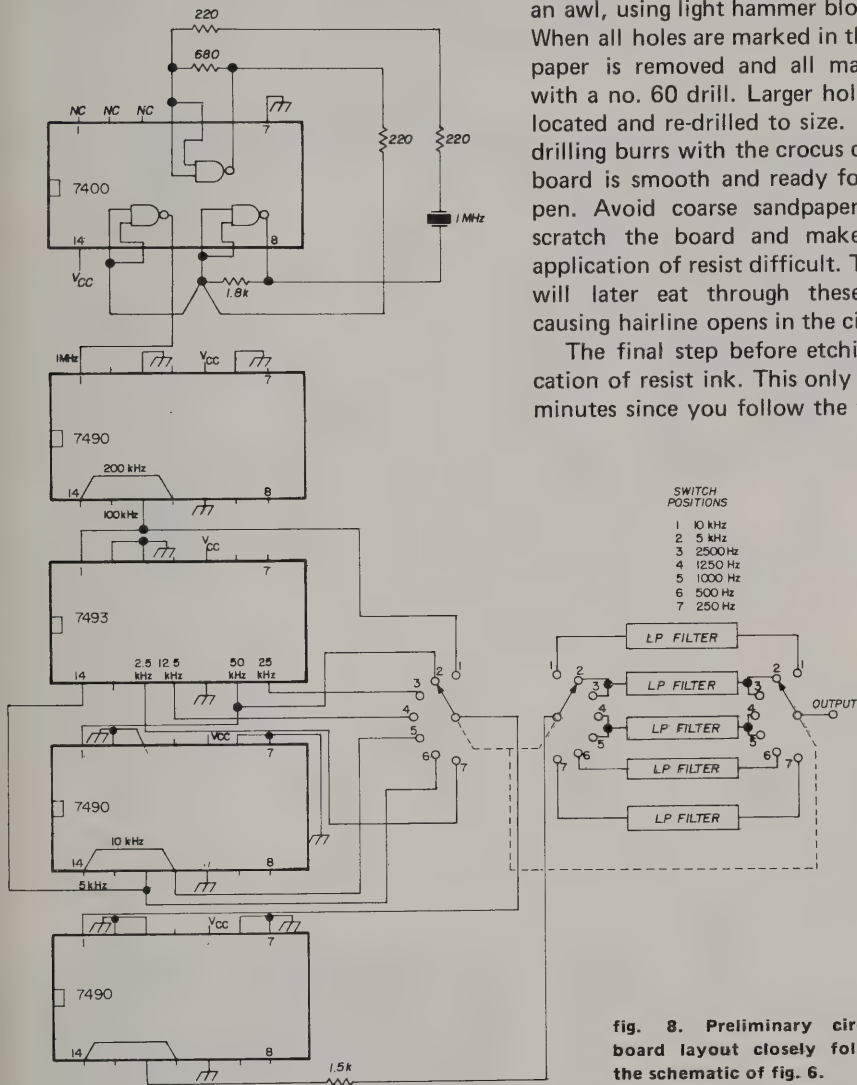


fig. 8. Preliminary circuit-board layout closely follows the schematic of fig. 6.

center the screw and the resilient washer material will prevent coil damage.

An excellent way to connect to circuit boards is also shown. Force 1/4-inch lengths of no. 12 wire in 5/64-inch holes in the circuit board and etch trails to these points, under the board. These

you have previously marked on the template. Make the resist trails solid and dark.

The etching stand is set up and the lamp secured in place over it. Mix the required amount of etchant in hot water and float the board, copper side down, in

this solution. The board should be frequently lifted during the etching process to free accumulated air bubbles, **fig. 11**. One way to do this is to attach a small enameled wire through existing holes near the center so that it may be grasped by long-nose pliers. Do not overetch. As soon as the board is finished, remove it from the tray, turn off the light, and

10-, 2-, and 1-kHz outputs would be available. The lowpass filter would not be used.

Perhaps you need a no-drift audio oscillator. Crystals could be selected by plug-in or by rotary switch and different filters switched in as needed. Such an oscillator would not drift even one hertz and would have excellent distortion char-

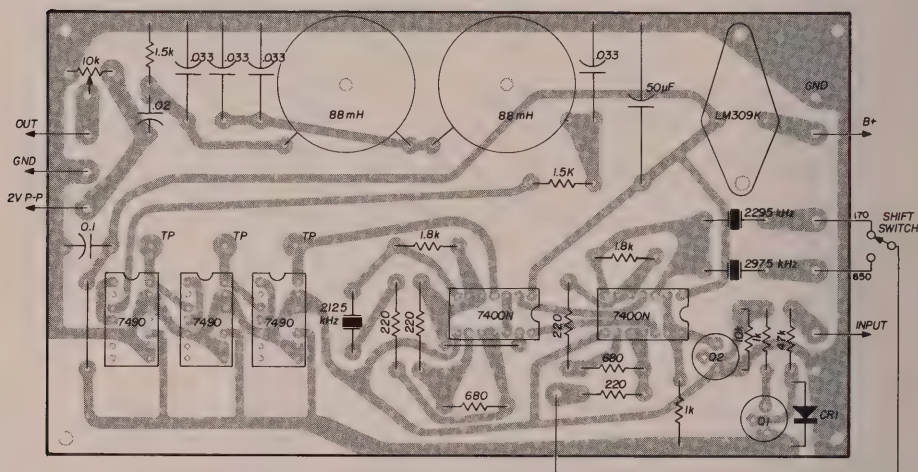


fig. 9. Detailed layout of the AFSK generator circuit board.

wash the board with cool water. Scrub the resist ink off with steel wool. The used etchant will be greenish in color and hot. Handle it carefully, dump it down the drain, and immediately flush with plenty of water.

weekend project

This audio frequency shift keyer is an example of the type of equipment you can rapidly assemble on your own circuit boards. Though designed for teletype, with slight modifications the same circuit may be used as a crystal calibrator or as a high precision audio oscillator. As a crystal calibrator only one 7400 IC would be needed, a crystal zeroing trimmer added, and a rotary selector switch installed to tap into different points in the 7490 divider chain. Each 7490 IC divides by 5 and then by 2. The divide-by-5 point is at the strap between pins 11 and 14. With a 1000-kHz crystal, 200-, 100-, 20-,

acteristics. If you want to divide the crystal frequency by some other factor, the 7492 IC will divide by 2, 6 and 12; the 7493 IC will divide by 2, 4, 8 or 16 without changes.

As an AFSK keyer, this unit has excellent performance at low cost. The original design by WB8AAK used RTL

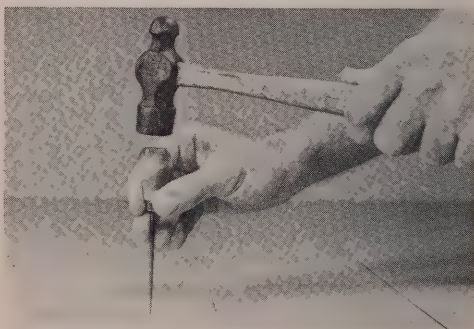


fig. 10. Component mounting points on the paper layout are transferred to the copper-clad board with an awl.

logic. However, the price of TTL devices has dropped so much that it was worthwhile to re-design the circuit to use TTL. The two 7400 gates are 22 cents each and the 7490 decade dividers are only 90 cents each, bringing total logic cost to \$3.14. It does not require a counter to set up or adjust.

Even the most inexpensive crystals may be used. JAN stocks the 2125- and 2976-kHz crystals for \$1.75 each. Use of a 2976-kHz stock crystal instead of the nominal 2975-kHz crystal only results in a one hertz error in output frequency which is undetectable for most purposes. The remaining crystal — the 2295 kHz unit for 170 shift — may be custom made for \$3.00. Everything used in the generator is available from advertisers in *ham radio*. Note that IC supply house prices will be higher than those quoted, which are for surplus devices.

Transistors are another item that may vary considerably in price depending on source. Feel free to substitute. There is nothing critical about the two transistors used in this unit except that they must be silicon types. There are dozens of transistors which may be used. Two types are given as examples.

the circuit

Both crystal oscillators run continuously. Sections of the 7400 ICs gate the oscillator output desired to the 7490 divider string. The output of the 7490 dividers is a square wave which aids in

filtering. The TTL dividers are powerful enough to drive the filters and output directly. With the recommended 5 volts on the TTL devices the current drain is 100 mA. The input to the LM309K regulator should be connected to a dc voltage source of from 8 to 30 volts. This may be an existing unit or built for this purpose. The output level is adjustable



fig. 12. Completed audio-frequency shift keyer board provides crystal-controlled, low-distortion audio tones.

from -3 dBm down to any value to suit your transmitter.

performance

The completed keyer run through checks to verify its performance. The generator was keyed with a 100-Hz square wave and observed on a dual-trace scope to confirm equal *mark* and *space* audio levels and good keying (see fig. 13). Filter ringing accounts for the small transient I observed. Frequency measurement with a digital counter confirmed that output frequencies were accurate to the hertz. Several crystals were tried to confirm this.

Audio distortion was then measured on a Hewlett-Packard distortion analyzer with some interesting results. Harmonic distortion measured only 0.25% at 2975 Hz but 3% at 2295 Hz and 4.2% at 2125 Hz. Scope analysis of the distortion products showed them to be almost entirely third harmonic, as was expected. Obviously, the filter was doing an excellent job at 2975 but only fair at 2125 Hz. The filter design was an old standard and had been used in the original design and other

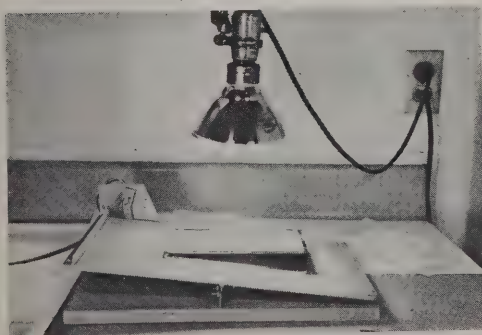


fig. 11. After inking in the circuit traces with the resist pen the board is placed in a tray of etching solution.

TEMPO — KENWOOD NEW-TRONICS

Best values at best prices. Available
in Cleveland, Ohio at

COMMUNICATIONS WORLD, INC.

4788 STATE RD. 44109

(216) 398-2955

ALSO STOCKING A/S, ASTATIC,
CDE, CLEGG, CUSHCRAFT, PACE,
REGENCY, STANDARD, & TEN-TEC
G. C. & CALECTRO PARTS.
SAMS, & ARRL PUBLICATIONS

— PCB KITS —

RTTY SPEED CONVERTER Drilled PCB 5 & 11 VDC \$40.00
DRILLED PCB ONLY \$ 6.00
RTTY AFSK Gen. All Shifts & CW I.C. 9 VDC @ 2ma \$6.60
100 KHz XTAL CALIBRATOR Less Xtal 9 VDC @ 2ma \$4.75
100 KHz XTAL (Limited Supply) \$2.50
PREAMP MICROPHONE, 26 DB Gain 9 VDC @ 1ma \$3.50
LIMITER PREAMP For High Z Mike 9 VDC @ 1ma \$4.80
PRODUCT DETECTOR For Your Receiver 9 VDC @ 1ma \$3.60
1/2" METER KIT Less 1ma Meter 6.3VAC \$4.75
WWV CONVERTER 3.5-4.0 MHz Output 9 VDC @ 5ma \$5.25
Requires 6-6.5MHz Crystal
6 METER CONVERTER FET Front End 9 VDC @ 5ma \$5.95
7-11 MHz Output, Less 43 MHz Xtal \$4.70
CW KEYING MONITOR, RF Keyed, Less Spkr. 9 VDC @ 9ma \$4.70
POWER SUPPLY - 9 VDC @ 50ma Output 115VAC \$4.85
6 OR 2 METER CASCODE PREAMP, 80 VDC @ 4.5ma \$4.95
Wired & Tested Less 2 ea 6CW4
Nivutors, Specify 6 or 2 Meter Model
DRILLS, #54, 56, 58 or 60 (each) \$4.40
Finest Quality for PCB'S, Made in USA Three For \$1.00

EXCEPT AS NOTED ABOVE, ALL KITS ARE NEW,
100% SOLID STATE, AND COME COMPLETE WITH AN
UNDRILLED G-10 PCB (PRINTED CIRCUIT BOARD) AND
ALL PCB MOUNTED COMPONENTS. KITS ARE LESS
POWER SUPPLIES, CHASSIS, AND ENCLOSURE HARD-
WARE. SEND SELF-ADDRESSED, STAMPED ENVELOPE
FOR COMPLETE DATA SHEET AND SCHEMATIC.

SATISFACTION GUARANTEED.* RETURN IN 30 DAYS
FOR REFUND. ALL KITS POSTPAID. INCLUDE 25¢
HANDLING CHARGE. WASHINGTON RESIDENTS ADD
5.3% SALES TAX.

P. M. ELECTRONICS INC.

519 SOUTH AUSTIN, SEATTLE, WASH. 98108

highly regarded AFSK keyers when 850 shift was popular.

However, 850 shift is now becoming obsolete. If you use only 170 shift, a minor modification of the lowpass filter will give excellent distortion characteristics. Simply add one .022- μ F capacitor across each of the .033- μ F capacitors in the filter. The distortion will then measure 1% at 2125 Hz (*mark*) and 0.7% at 2295 Hz (*space*) frequencies. This is good enough so that it may be used with any filter-type ssb transmitter.


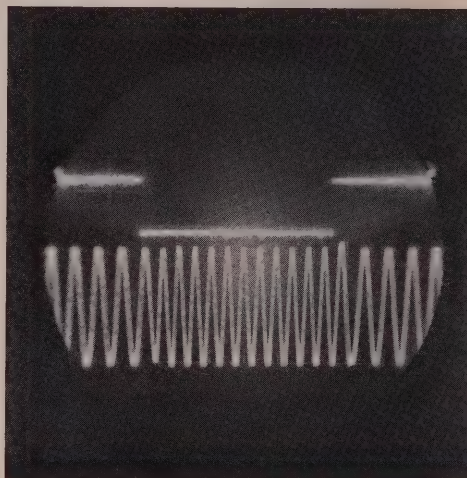


fig. 13. Audio output of AFSK unit provides excellent waveform continuity between mark (2295 Hz) and space (2975 Hz).

references

1. B.L. Stuecker, WB8AAK, "Crystal-Controlled AFSK Generator and Standard," *RTTY Journal*, June, 1970.
2. A.A. Kelley, K4EEU, "Crystal-controlled AFSK," *RTTY Journal*, September, 1972.
3. W.H. Craig, WB4FPK, "Crystal-Controlled AFSK Generator, Updated," *RTTY Journal*, September, 1972.
4. Howard Phillips, Jr., W6FOO, "Radio Teletype with SSB Transceivers," *ham radio*, November, 1970.
5. Irvin M. Hoff, W6FFC, "AFSK for RTTY," *QST*, February, 1969.
6. Larry L. Hutchinson, "Photofabrication of Printed-Circuit Boards," *ham radio*, September, 1971.
7. "Circuit Board Fabrication," *Radio Amateur's Handbook*, A.R.R.L., 1972 edition, page 547.

ham radio

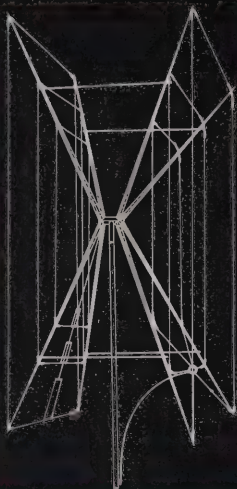

feature this one . . .

On top of your tower, the exciting Structural Glass GEM-QUAD* for 10, 15 and 20 meters.

A two element fibre glass quad antenna designed for better signal discrimination & directivity on 10, 15 & 20 meters!

NEW

Improvements
for better
than ever
performance.

- Stronger Arms (closer wound).
- Strong alloy RF wire.
- Improved quality nylon straps.
- UV resistant.
- Low wind resistance (2.4 sq. ft.)

1. Non-corrosive fibreglass construction.
2. Double "Cone-shaped" design maintains critical measurements under severe weather conditions.
3. Lightweight (complete antenna weighs approximately 22 lbs.)
4. Simple T.V. Rotator will rotate antenna.
5. Maximum front to back ratio and side discrimination.
6. Maximum capture area.
7. Low angle radiation.
8. Forward gain for 2 element quad 8db.

9. Optional 3rd element easily installed with no conversion required. Forward gain up to 8.9 db on DX.
10. Single 52 ohm feed line to all bands.
11. No switches or coils required.
12. Low SWR easily obtained.
13. Arm mounts designed for exact element spacing and optimum performance.
14. Nylon tension wire holders eliminate wire strain and breakage.
15. Designed to withstand high winds.

\$107 Two Element Quad **\$60** Extra Element

* Patented

Includes U.S. Customs Import Duty or Canadian Federal Sales Tax. Shipped Collect. Please include check or M. O. with your order.

STRUCTURAL GLASS LIMITED

20 BURNETT AVENUE
WINNIPEG, MANITOBA

USE CHECK OFF ON PAGE 110 FOR FULL DETAILS

speed standards for international morse code

How to use
standard words
to determine
the words-per-minute
speed of your keyer

In the formation of the International Morse code used by amateurs, there are two basic *sounds* and three basic *spaces*: the dot, which is 3 time-unit or baud, the dash, which is 3 bauds, a space between each element of a Morse character, which is one baud, a letter space of 3 bauds and a word space of 7 bauds.

Numerals are separated in the same way, and punctuation is preceded by a 3-baud space and followed by a 7-baud

space. Therefore, the letter E, one dit, consists of two bauds — a one-baud sound plus a one-baud space. The letter T, one dah followed by a one-baud space, contains four bauds. With this in mind, the ratio of the dit with its space to the dah with its space is 1:2.

counting words per minute

If you key a string of dits for one minute at a constant rate to obtain a total of 25 dits you have used 25 bauds for sounds and 25 bauds for spaces, for a total of 50 bauds in 60 seconds. This rate represents one word per minute. If you only count the number of dits, dividing that total by 25 will also give you the keyer speed in words per minute.

However, it's much easier to count dahs, particularly at higher speeds. Since the ratio of dots to dashes (including spaces) is 1:2, simply count the number of dahs per minute and divide that total by 12.5 to arrive at the equivalent speed in words per minute.

adjusting your keyer

To obtain the proper ratio of dots to dashes first count the number of dits per minute. Then adjust your keyer so you have exactly half the number of dahs in the same time span. When this is done your keyer is properly adjusted, including the spaces. For example, if you key a

Gaspard Lizée, VE2ZK, 135 Carillon, Sherbrooke, Quebec, Canada

string of 250 dits in one minute, you must adjust your keyer to provide 125 dahs in one minute to provide the proper timing ratio.

To arrive at the word-per-minute speed of this keyer setting simply divide the 250 dits by 25 (or the 125 dahs by 12.5) to arrive at 10 words per minute. To calibrate the speed dial for other speeds simply count the number of dahs in one minute and divide by 12.5. If you want to use less than one minute, count the number of dahs in 24 seconds and divide by 5 — it will give you the same result.

automatic keyers

Automatic Morse Keying heads used by the FCC and ARRL are adjusted to a 50-baud word standard. That standard word is PARIS. If the speed of the automatic keyer is set to send the word PARIS ten times in one minute, the sending speed is exactly 10 words per minute.

If you count the total number of bauds in PARIS you come up with a total of 50:

- - - -	P	8 bauds sound	
		3 bauds element space	
		3 bauds letter space = 14 bauds	
- -	A	4 bauds sound	
		1 baud element space	
		3 bauds letter space = 8 bauds	
- - -	R	5 bauds sound	
		2 bauds element space	
		3 bauds letter space = 10 bauds	
- -	I	2 bauds sound	
		1 baud element space	
		3 bauds letter space = 6 bauds	
- - -	S	3 bauds sound	
		2 bauds element space	
		7 bauds word space = 12 bauds	
		total	50 bauds

Any other word that has a total of 50 timing units could also be used for the same purpose. It doesn't matter if it has

more or less letters so long as it contains a total of 50 bauds.

military stations

Most military stations use a standard 60-baud word to set the speed of their keying heads, using the standard word CODEZ for this purpose. If you count the number of bauds in CODEZ you will come up with a total of 60.


With a 60-baud standard, the number of words per minute appears to be much faster. If you want to experiment a bit, listen to an automatic Morse station that announces its code speed. Copy the station for one minute, count the total number of bauds, and divide by 50. You'll quickly find out what standard they use for setting up their keying heads.

The ARRL code-practice sessions transmitted by W1AW, for example, are based on a 50-baud standard. For comparison, try to copy WAR on a Tuesday evening — it will be much faster than the announced speed. It takes only a minute to figure out that 10 words per minute using the 50-baud standard is only 8.33 words per minute with a 60-baud standard.

The two different standards are a result of two different types of transmission. Most military stations transmit 5-letter code groups; amateur radio operators transmit clear text which uses a larger number of the letters E and I. The two different standards compensate for this difference.

The difference in words per minute with the two standards increases markedly at higher speeds. Sixty words-per-minute clear text (50-baud base) is equivalent to 41.66 words per minute of coded letter groups (60-baud base). This is probably very near the upper possible limit that a human ear is able to differentiate. The current world record, held by the late Ted McElroy, is 75.2 words per minute. This might stimulate someone to suggest a new award, "The Ted McElroy Gold Medal." Anyone interested?

ham radio

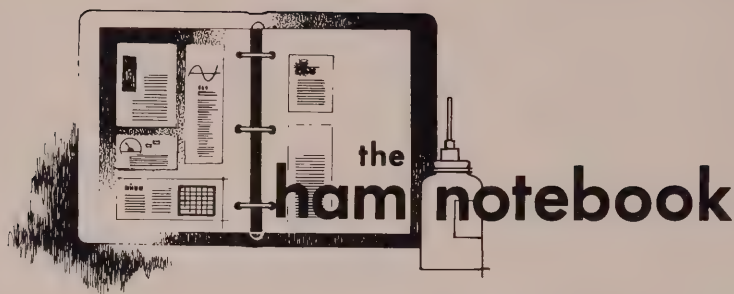

5/8-wave whip for 2 meters

A standard 102-inch Citizens Band whip can be easily converted into either a fixed station 5/8-wave groundplane or an effective mobile gain antenna. Gain for

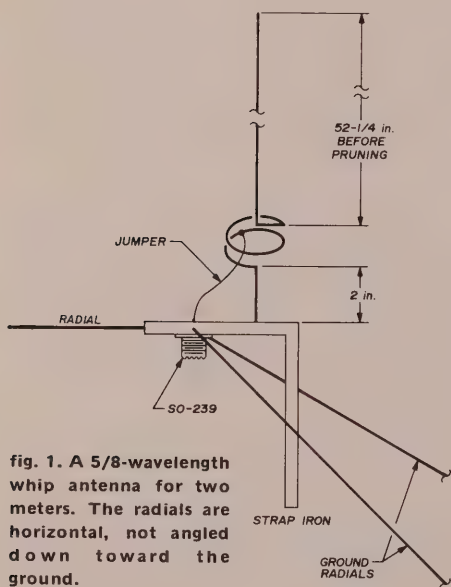


fig. 1. A 5/8-wavelength whip antenna for two meters. The radials are horizontal, not angled down toward the ground.

either antenna was measured at about 2.5 dB over a quarter-wave groundplane. Both antennas are electrically sound and do not have mechanical joints to corrode and break down. The overall view of the home-station version is shown in fig. 1, and the mobile version in fig. 2.

For the home-station groundplane, measure down 52¼ inches from the antenna's tip and place the antenna in a vise. Using a torch (propane does well), heat the whip cherry red and bend a 90° angle when the metal will allow itself to be bent without undue force. Using a jig made from 2-inch diameter pipe (fig. 3), bend the coil slowly while constantly applying heat. Bend 1½ turns with at least ½-inch spacing and finish the coil so that the straight section of the antenna below the coil is lined up with the longer section above the coil. Leave 2 inches of wire below the coil and remove the rest.

The antenna base is made from a seven-inch section of 3/8-inch by 2-inch galvanized flat iron. Drill the flat iron as shown in fig. 4 for an SO-239 coax

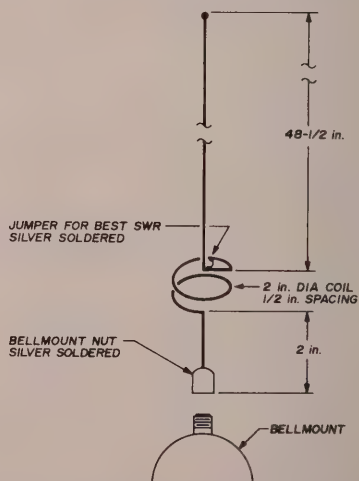


fig. 2. Using the 5/8-wavelength antenna for mobile operation.

connector and its mounting screws. Be sure to ream out the underside of this hole to allow the connector to sit flush with the flat iron. Drill 1/8-inch holes for the ground plane elements and the whip. Heat the iron and make a 90 degree bend as illustrated.

Cut three ground radials from 1/8-inch round rod such as galvanized lathers ceiling rod. Each radial should be 19-inches long. Insert them into the three holes drilled into the side of the bracket and bend the two side radials so there is 120° spacing between all three radials. Insert the whip into its mounting hole until its bottom is flush with the bottom of the hole. Weld or silver-solder the whip and the radials in place. Install the coax connector and solder a short length of solid number 12 copper wire to the center pin (this will go to the tap on the base coil eventually).

The rest of the procedure is simply tuning and pruning. Wrap the free end of the copper wire about one half turn from the bottom of the coil and, with a vswr meter in the feedline, adjust the tap point for best swr. Trim the end of the antenna by filing a notch and breaking off about 1/8-inch of rod at a time. By working

back and forth between readjusting the tap and trimming the antenna length, you should be able to tune the antenna for zero reflected power. At this time, silver-solder the copper wire to the coil. Seal around the coax connector and around the copper wire with silicon seal to protect your rf feedline in case of heavy

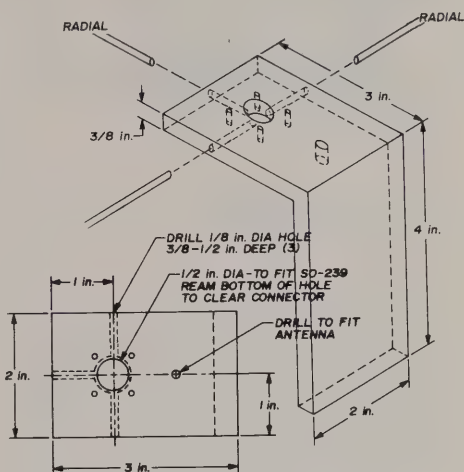


fig. 4. Construction of the antenna base. Horizontal radials are installed and welded in place.


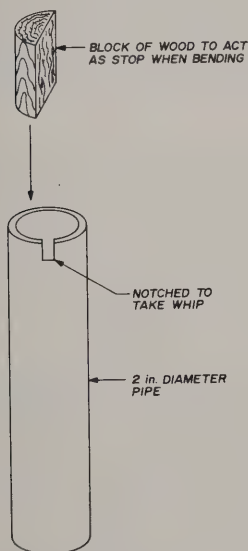


fig. 3. Jig used for bending the base coil (see text).

rain or ice build up. It is also worthwhile to paint any spots that might have been exposed to excess heat in the construction. Simply mount the base to your tower or mast.

A mobile version of this antenna is made in basically the same manner. The radiator (after the coil) is cut to 48½-inches rather than 52¼-inches, and the base of the coil is connected to an ordinary bell mount. The base coil is wound just like the home-station version. The mobile antenna is not a grounded system, however. It is tuned for minimum vswr by adjusting the tap point for a short jumper from the junction of the base of the radiator section and the top of the coil to a point on the coil. In my case, by juggling the antenna length and the tap point, I found the best tap point by shorting about 1¼ turns. Silver solder the jumper in place.

John Dobroshinsky, VE3DDD

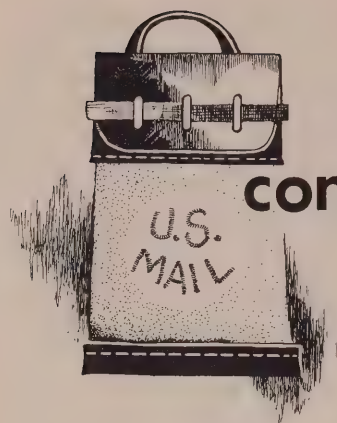

comments

ssb detector

Dear HR:

Regarding the ssb detector circuit on page 68 of the December, 1972, issue of *ham radio*, the tuning capacitors required to resonate the Collins filter at 455 kHz are omitted, which will result in a substantial insertion loss. The input impedance at pin 1 of the CA-3028 is specified at from 3k to 5k ohms and the impedance at the source of the MPF102 is approximately 2.7k ohms. The lack of matching to these impedances will result in shape and ripple degradation. Therefore, it would be necessary to provide proper matching for either series resonance of the filter which is 600 ohms, or parallel resonance at 100k ohms.

Also omitted is the required bypass capacitor from the drain of the MPF102 to ground.

M.H. Gonsior, W6VFR
Fullerton, California

As I pointed out in my article, there are quite a few things left out. W6VFR has found them.

I do not have any data on the Collins filter and when I breadboarded the circuit back in March, 1972, I felt such a sense of urgency that I did not stop to investigate the impedance of the filter. Now that I have been given the impedance values, finding the capacitor values will be easier.

The gain of the amplifier was marginal;

however, I was testing the detector, not the amplifier. It is too bad that I have already disassembled the circuit. It would be interesting to see how much of an improvement could be gained by matching the impedances.

In the circuit, the MPF102 and the NE561B were physically close together and the 0.5 μ F capacitor shown near the IC served as a bypass capacitor for both devices.

Max Robinson, K40DS

touch-tone modification

Dear HR:

I have not had a single transistor failure due to the mobile touch-tone circuit as originally presented in the August, 1972 issue of *ham radio*. However, I will admit that WB8NAT's change was better.

The following addition to the unit, one which I did not think of originally, will

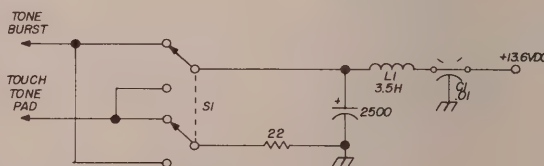


fig. 1. Improved Touch-Tone circuit.

prevent any filter capacitors from charging up, discharging, then re-charging after the +12 volts dc has been removed. In short, the switch labeled *burst/pad* for dc switching is changed to a dpdt switch rather than a center-off spdt unit. The improved circuit is shown in fig. 1.

Bill Lambing, W0LPQ
Marion, Iowa

satellite communications

Dear HR:

In the satellite communications article by K1TMA in the November, 1972, issue the comment concerning antenna gain on page 55 states: "The primary concern of the system loss formula is to know the amount of rf gain there is in a particular array in the desired direction of transmission, relative to half-wavelength dipole or that hypothetical antenna, the isotropic source."

Actually, there is a 2.14 dB theoretical gain that a dipole has over an isotropic radiator, so to be on the level in calculations the isotropic radiator should always be chosen as the reference antenna. This will entail a knowledge of the gain-over-isotropic of a particular array. It should be borne in mind that some handbooks use gain over isotropic, while others, notably the *ARRL VHF Manual*, use gain over an ideal dipole. Most commercial manufacturers use gain over isotropic in the specification sheets. In any case, use of the system loss formula in engineering fashion means referencing all antennas to the point source or isotrope.

Another point not specified is the reference for computing transmitter output power in dB; power output should be specified in dBW, or dB above 1 watt.

While this parameter is not specified in the system loss formula, it is nonetheless important; the result of the system loss formula, as indicated in the article, will be a large negative number in dB. Thus,

$$LS + \frac{S + N}{N} = P_0 + S$$

where LS is system loss, P_O is power output in dBW, S is effective receiver sensitivity in dBm, and $(S + N)/N$ is the required signal to marginal communications (use 3 dB for CW, 6 dB for ssb).

P.H. Bock, Jr. K4MSG
Ayon, North Carolina

sstv synch generator

Dear HR:

I have just finished reading WA2EWO's article on the sstv synch generator, and in my opinion, the design is too costly and complex. I have a similar unit which is built on a piece of Vector board, 2 x 5 inches. Total cost for all the ICs is \$4.04 including three 74121 single-shots, one 7473 divide-by-four, one 7490 divide-by-ten and one 7492 divide-by-12 connected as shown in **fig. 2**. The cost of WA2EWO's synch generator is nearly \$20.

Gordon P. Stanys, W1IA
Stamford, Connecticut


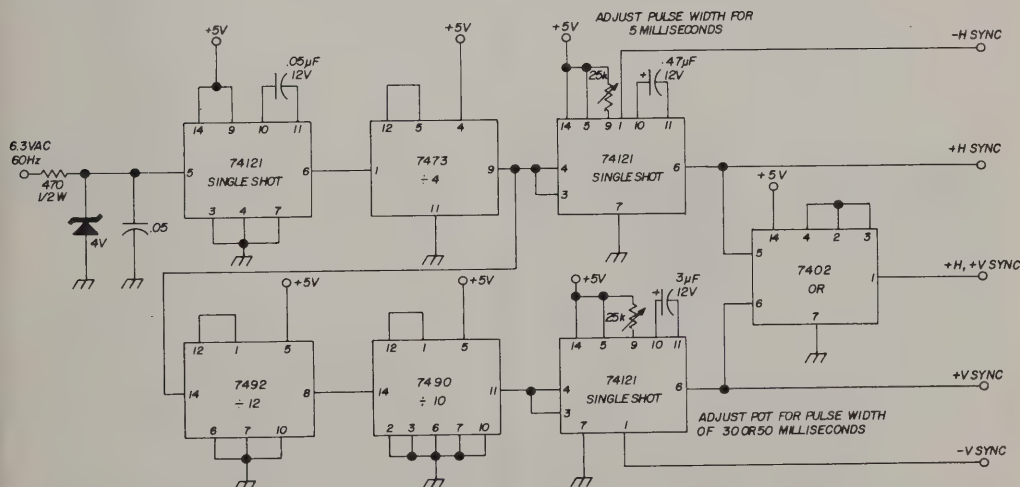


fig. 2. Block diagram of the sstv synch generator.

new products

memory-matic 500-B

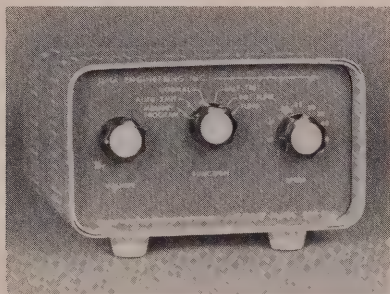

Data Engineering's reprogrammable memory keyer has been improved and updated. The Memory-Matic 500-B today features a choice of 500-bit or 800-bit memory and provision for remote control of the message start and message stop function. The dot to dash weight ratio is also completely variable and the type of keying is selectable — choosing, dot memory only, dash memory only, no memory operation or full dot and dash memory operation — all with or without automatic character and word spacing.

A memory stop switch allows the insertion of some information in the midst of a list of sequential memory transmissions. An example of this operation would be the manual insertion of a station's signal report in a preprogrammed message including a greeting, your location and your name.

The unit features iambic squeeze keying, built-in adjustable monitor and speaker, rf-proofing, and built-in 117 Vac

power supply. The new keyer sells for \$198.50 with a 500-bit memory reprogrammable memory or \$219.50 with an 800-bit reprogrammable memory. Full details on all the features of this new keyer are available from Data Engineering, Inc., Ravensworth Industrial Park, 5554 Port Royal Road, Springfield, Virginia 22151 or by using *check-off* on page 110.

sub-audible encoder




The new Tobel CTCSS encoders fill the void for a low cost, sub-audible, miniature tone encoder and are ideally suited for mounting in solid-state transceivers, as well as, larger tube-type 2-way radios. Extensive field tests have proven the CTCSS encoders to be superior in both design and performance to older mechanical reed-type devices. Tobel encoders provide faster starting time, lower power consumption and immunity to damage from mechanical vibration. Low power consumption (2.5 mA at 12 V) and small size make Tobel encoders a natural for small hand-held transceivers and other battery operated communications equipment. Minimal effort and expense is required to convert your FM radio to sub-audible tone coding.

CTCSS (Continuous-Tone, Controlled Squelch System) makes possible positive repeater access and receiver squelch control under conditions of high noise, weak signals, and mobile flutter. CTCSS encoders are available for any EIA code L1 thru 7A as standard units and must be specified when ordering. Non-standard frequencies are available on special order.

For more information, write to Tobel Electronics, 7920 Alida Street, LaMesa, California 92041, or use *check-off* on page 110.

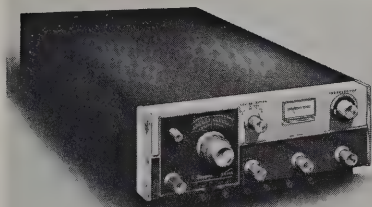solid-state high-frequency ssb transceiver



Swan Electronics has just introduced a full line of completely solid-state ssb transceivers for use on 80 through 10 meters. Models are available for 200, 100 and 15 watts PEP ssb, and all transceivers feature all solid-state, broadband transmitting circuits, as well as full coverage, 80 through 10 meters, CW and ssb. The new Swan solid-state transceivers have built-in VOX and a built-in noise blanker with variable blanking control. The transmitter circuits, which require no tuning, have infinite vswr protection from an open to a short circuit, so it's impossible to damage the final power transistor because of poor antenna matching.

Receiver sensitivity for the solid-state Swan transceivers is less than 0.5 microvolt at 50 ohms impedance for a signal-plus-noise-to-noise ratio of 10 dB. Minimum image rejection is -55 dB at 30 MHz, increasing to better than -75 dB at 3 MHz. Audio response is essentially flat from 300 to 3000 Hz ± 3 dB. Audio output, to an external 3.2-ohm speaker, is 4 watts with less than 10% distortion. I-f selectivity is provided by a 2.7-kHz wide crystal filter with a 1.7 shape factor.

In the transmit mode the unwanted sideband is down more than 50 dB and the carrier is suppressed greater than 60 dB. Distortion products are approximately -30 dB. Transmitter output impedance is 50-ohms nominal. An audio sidetone is



Hobby Industry




**DON'T FOOL
AROUND -!**
Ask about my

HI-SAVINGS PLAN-SAVE \$

NO FOOLING! Real Bargains
GREAT performance-521
Astatic:Hi-Z ceramic &
coil cord, PTT. \$5.95 post
paid in the USA.



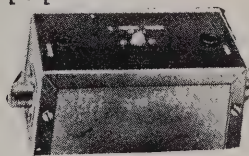**AMECO 2 meter
filter reduces
TVI and receiver
cross-mod. A
value at \$9.95
p. paid.**



NOVICE -VFO

**Wired ,solid-state modules
to make a VFO/QRP Xmtrr.**
**As low as \$17.40 ,less case
etc.**

Especially for "hams"



CALL:Tues./Sat.-Noon/5PM
Al McMillan WØJJK
(712) 323-0142

WRITE: HOBBY INDUSTRY
4HRBox 864
Council Bluffs, Iowa - 51501

SUPER CRYSTAL THE NEW DELUXE DIGITAL SYNTHESIZER!! FROM **R_p**



MFA-22 DUAL VERSION
Also Available MFA-2 SINGLE VERSION

- Transmit and Receive Operation: All units have both Simplex and Repeater Modes
- Accurate Frequency Control: .0005% accuracy
- Stable Low Drift Outputs: 20 Hz per degree C typical
- Full 2 Meter Band Coverage: 144.00 to 147.99 MHz, in 10KC steps
- Fast Acting Circuit: 0.15 second typical settling time
- Low Impedance (50 ohm) Outputs: Allow long cable runs for mobiles
- Low Spurious Output Level: similar to crystal output

SEND FOR
FREE DETAILS

R_p Electronics

Prices MFA-2 \$210.00 BOX 1201H
MFA-22 \$275.00 CHAMPAIGN, ILL.
Shipping \$3.00 extra 61820

VHF-FM HEADQUARTERS FOR SOUTH FLORIDA OFFERS YOU CRYSTALS AT A PRICE YOU CAN AFFORD!

for

DRAKE	SBE
SWAN	INOUE
REGENCY	STANDARD

ALL \$3.25 ea. TRANSMIT OR RECEIVE
prepaid USA

EMPORIUM SOUNDS OF POMPANO
51 North Federal Highway
Pompano Beach, Florida 33060
305-782-3464

provided to CW monitoring, and CW keying is equivalent to grid-block keying and features semi-break-in with VOX.

The vswr protection circuit cuts output power by 20% when the vswr is 3:1 or higher. Under these conditions, infinite vswr protection is provided, including open or short circuits.

Three models are available, the SS-200, with 200 watts PEP ssb minimum on all bands and 200 watts dc input on CW; the model SS-100, 100 watts PEP minimum on ssb and 100 watts CW; the model SS-15, 15 watts PEP minimum on ssb and 15 watts CW. All transceivers are designed for 13.5 Vdc power supplies, the nominal supply voltage of a 12-volt automobile system. All units require 500 mA in the receive mode. For ssb transmission, the SS-200 requires 6 amps average; the SS-100, 3.5 amps average, and the SS-15, 800 mA average. For CW operation, the current drain is higher, being 20, 11 and 2 amps respectively for the SS-200, SS-100 and SS-15. Accessory power supplies are available for operation in the home station from 117 Vac utility lines.

Other accessories include the SS-208 external vfo for split-frequency operation, the 610X crystal-controlled oscillator, the SS-16B 16-pole super-selective crystal filter with a 1.28 shape factor, and the SS-1200 1200-watt PEP linear amplifier using four 6LQ6 tubes for 117-Vac operation.

The SS-15 ssb transceiver is priced at \$579.00. The SS-100 is \$699.00, while the SS-200 is \$779.00. The 1200-watt SS-1200 linear amplifier is priced at \$299.00.

For more information, write to Swan Electronics, 305 Airport Road, Ocean-side, California 92054, or use *check-off* on page 110.

great circle charts

As a service to radio amateurs WB5CBC is making available, to amateurs anywhere in the world, a comprehensive chart of great-circle bearings to 660 locations throughout the world for the unbelievable price of \$1.00, postpaid. These

charts, which are a handy 8½ by 11 inches, contain great circle bearings to the nearest degree, distances in miles and kilometers, and return bearings. Directional accuracy of the charts is to the nearest degree while distances are to the nearest mile and kilometer.


The magnetic bearing is not given on these charts because magnetic declination at any location varies from year to year, sometimes as much as 10°. It is easier to zero your antenna on true north (using the North star) and forget it.

The return bearing, a particularly useful feature of this chart, is the bearing from the distant location to your station. The return bearing is *not* a simple 180° difference from the outward bearing, but must be derived through spherical trigonometry. The ability to give a station being worked the correct bearing for aligning his antenna will produce results which are nothing short of amazing. When the chart indicates a distance greater than 8000 to 10,000 miles, the long path, which is simply 180° opposite the indicated bearing, can be considered. The same is true for the return bearing.

Charts consist of six pages and are available for any location in the world. To order a chart, the following information is needed:

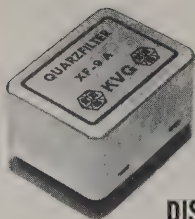1. Name and postal address.
2. The city for which the chart is wanted (include state and/or country).
3. If the population of the city is less than 10,000 or if the location is a rural area, also include the latitude (indicate north or south) and longitude (east or west) in degrees and minutes.
4. Include payment of \$1.00 (postpaid worldwide) or \$1.75 (airmail worldwide). Cost to overseas stations is 7 IRCs (12 IRCs for airmail).


Send your order to William D. Johnston, WB5CBC, Great Circle, 1808 Pamona Drive, Las Cruces, New Mexico 88001. Queries for additional information should be accompanied by a self-addressed, stamped envelope.



**CRYSTAL
FILTERS**

and

DISCRIMINATORS



K.V.G.

Unfortunately, due to uncertainties left by the dollar devaluation, we cannot quote prices in this ad. Please write directly or use check-off to get our latest quotations.

VHF UHF

HIGH POWER

VARACTOR

M.M. TRIPLERS M.M.

<p>MMv 432</p> <p>INPUT: 140-153 MHz</p> <p style="padding-left: 40px;">20 watts max.</p> <p>OUTPUT: 420-459 MHz</p> <p style="padding-left: 40px;">12 watts min.</p>	<p>\$69.95</p>
<p>MMv 1296</p> <p>INPUT: 420-459 MHz</p> <p style="padding-left: 40px;">12 watts max.</p> <p>OUTPUT: 1260-1377 MHz</p> <p style="padding-left: 40px;">6 watts min.</p>	<p>\$79.95</p>

si

**SPECTRUM
INTERNATIONAL**


BOX 1084 CONCORD

MASSACHUSETTS 01742

ALPHA 77

by

ETD

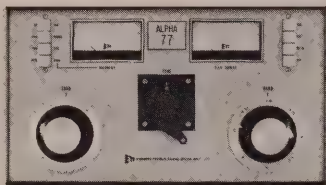

Featuring the new Giant from Eimac, the 8877, with 1500 watts of plate dissipation: \$1495.

Warranty: One Year
Power Supply - Two Years

Phone/write DON PAYNE, K4ID for a brochure, and a King-Size trade on your gear.

Days (615) 384-5573

Nites (615) 384-5643

PAYNE RADIO

BOX 525

SPRINGFIELD, TENN. 37172



ELECTRONICS

P.O. BOX 1672
VISTA, CA. 92083
714-726-1313



This New Frequency Counter has the following Specifications to recommend it:

Direct Counting: 10Hz to 80MHz guaranteed (1Hz to over 100MHz typical)

10MHz xtal time base

Readout: 5 digit LED plus over-range

Input Sensitivity: 100 millivolts max. on any freq.

Input Impedance: 1MΩ paralleled with 15pf.

Power Requirement: 120VAC or 12VDC

SMALL SIZE 2 1/8" H, 5 1/4" W, 6 3/4" D.

Guarantee 1 year all parts, 90 days labor


PRICE \$250.00

FOB Vista, Ca. 92083

Y & C ELECTRONICS

P. O. Box 1672, Vista, CA. 92083, 714-726-1313


inspection lamp

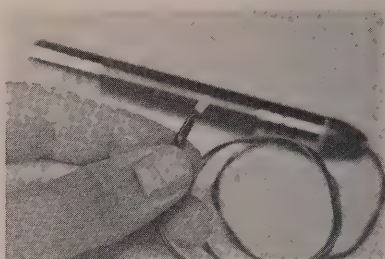

Put an end to the frustration of attempting to look into a small opening while shining a flashlight into that same opening. This ultra miniature grain-of-wheat inspection lamp can be inserted into the opening and will illuminate the entire interior without blocking your vision. It can be used in the repair of radio equipment, typewriters, engines and other mechanical gadgets, as well as the inspection of gun barrels, dies, machined parts, plumbing, etc.

The price for the inspection lamp and flashlight is \$2.50 postpaid. Write to Spacetrom, Box 84, Broadview, Illinois 60153, or use *check-off* on page 110.

mobile gain antenna

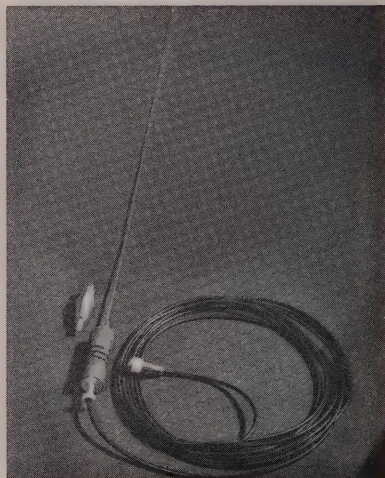

The new Antenna Engineering M-series antenna is a full 5/8-wavelength vertical whip with a bottom-load matching transformer which is designed for vehicle mounting. The adjustable threaded bushing allows for either roof-mounting or mounting through double-panels. The

matching transformer is encased in a fiberglass sheath which is nearly indestructible. The whip is of 1/8-inch spring-temper type 302 stainless steel; the coil tip unscrews to accept a chrome-plated spring (optional at extra cost) for severe service applications.

This antenna is available for all amateur and commercial frequencies in the 140-175 MHz, 220-225 MHz and 420-470 MHz bands. The M-series antennas are at dc ground for dissipation of static, and are supplied with 20 feet of type RG-58A/U coax and ugf connector. Prices range from \$16.95 for the 140-175 MHz version to \$15.95 for the 420-470 MHz version. For more information, write to Antenna Engineering Company, Inc., Box 19449, Indianapolis, Indiana 46219, or use *check-off* on page 110.

solid-state ssb radiotelephone



Stoner-Goral Communications has introduced their new ssb radiotelephone. It is believed to be the first all solid-state 100-watt MF/HF marine single-sideband radiotelephone and was designed as a direct replacement for obsolete a-m equipment.

The unit operates on frequencies between 1.6 and 9.0 MHz and has a capacity for 11 duplex or 22 simplex channels. Any channel may be programmed for AME as well as suppressed or reduced (-16 dB) carrier operation. A variety of power supplies and accessories permit its use in land-based, mobile and marine stations.

The exciter portion of the radiotelephone is an up-conversion scheme and uses integrated circuits almost exclusively. Simplified channelizing involves inserting crystals and "netting" to fre-



DIODES





NEW NEW NEW

Tubular Polystyrene Capacitors. All 125 Volts
 — 2.5% tolerance. .003 Mfd. .01 mfd. .018 mfd. .022 mfd. Your Choice 15 for \$1.00 ppd.



NEW NEW NEW

MYLAR CAPACITORS. All 200 Volts Radial Leads. .01mfd. .05 mfd. .1mfd. YOUR CHOICE.
 14 for \$1.00 ppd.

100 kc. XTAL. Octal Plug-in. High Quality.
 \$3.50 ea. ppd.



High quality American Made TO-5 Transistor sockets. Ideal for PC board use.
 10¢ ea. ppd.



3000 MFD @ 30 Volt Capacitors.
 Size 1" Diameter x 3" Long. 75¢ Each or 3 For \$2.00 ppd.



Black, Aluminum Anodized, Heat Sink. Size Approximately 4 3/4" x 1 3/8" h. x 1 1/2" w. Predrilled For TO-3 Transistors. Delco Factory New. 75¢ Each 3 for \$2.00 ppd.

BACK IN STOCK
 Unpotted Toroids. All centertapped.
 88 mhy or 44 mhy. Your choice 5 for \$2.00 ppd. 15 for \$5.00 ppd.


NEW

Transformer, 115 VAC Primary, 12 Volt, 4 Amp Secondary
 \$4.00 Each ppd.

115 VOLT AC TRANSFORMER @
 Secondary 12-0-12 Volts @ 800 ma. Very Nice. \$2.40 ea. ppd.



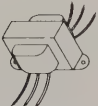High quality, American Made Transformer. 115 Volt Primary. Secondary 17-0-17 Volt @ 150 ma. Tap At 6.3 Volt For Pilot Light. Ideal For Transistor Pre-Amps, VFO's, etc. Fully Shielded.
 \$1.50 Each ppd.



Power Transformer. 115 Volt AC Primary. Secondary #1: 32-0-32 Volt @ 1 Amp. Secondary #2: 6.3 Volts. Low Current For Pilot Lights. Size 2 1/2" x 2 1/2" x 3".
 Price: \$2.50 Each ppd.

6.3 Volt 1 Amp Transformer. Fully Shielded
 \$1.60 Each ppd.

Transformer — American Made fully shielded. 115 Volt Primary
 Secondary #1 18-0-18 Volts @ 4 Amps
 Secondary #2 5 Volts @ 2 Amps
 A very useful unit for LV Power supply use.
 Price — A low \$4.75 ppd.

SEND STAMP FOR BARGAIN LIST
 Pa. Residents add 6% State sales tax
 ALL ITEMS PPD. USA




m. weinschenker

K 3DPJ BOX 353 • IRWIN, PA. 15642

NEW! IC KEYER

Only
\$87.50
PPD
USA

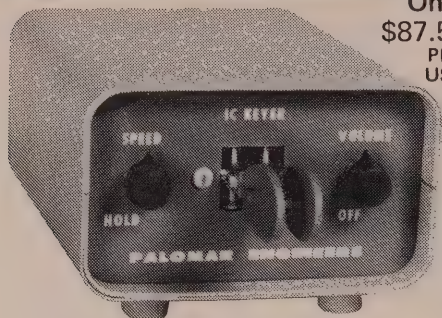

- Self completing dots and dashes.
- Dot memory for easy keying.
- Precision feather-touch key built-in.
- Sidetone oscillator and speaker built-in.
- Relay output keys 300-V @ 100-ma.
- Keyed time base. Instant start.
- 5-50 wpm. Perfect dot-dash ratio.
- Send QSL or postcard for free brochure.

PALOMAR ENGINEERS

BOX 455, ESCONDIDO, CAL. 92025

GATEWAY ELECTRONICS

8123 PAGE AVENUE
ST. LOUIS, MISSOURI 63130
314-427-6116

12/24 VOLT TRANSFORMER — 5 AMP — 4 x 3 1/2 x 3 — ship wt. 7 lb. \$5.00

955 TUBE — Oscillator tube for Model 80 etc. hard to find — new \$1.50

L.E.D. — 7 SEGMENT READOUT — MAN 1 TYPE — NEW \$2.75

THUMBWHEEL SWITCHES

— 0.5 x 2.125 x 1.78 — 10 position decimal \$2.75
— 10 position BCD & Complement \$3.75
— End Plates (per pair) \$1.00

MINIATURE SIZE

— 0.312 x 1.3 x 1.3 — 10 position decimal \$2.00
— 10 position BCD & Complement \$2.75
— End Plates (per pair) \$.50

10 MHz CRYSTAL — Standard HC-6/U style in 24 volt oven. — ship wt. 1 lb. \$2.50


Visit us when in St. Louis
\$5.00 Minimum Order

quency. The use of bandpass filters eliminates tuned circuits and individual channel alignment, even in the transmitter.

Exceptional reliability is claimed for the new SG-711. Heating has been reduced through the use of solid-state power amplifiers. They are fully protected against problems caused by open or shorted antennas and high temperature operation. The SG-711 is small and light weight, less than 7 pounds.

For additional information, contact Donald L. Stoner, Director of Marketing, Stoner-Goral Communications Co., Box 233, Mercer Island, Washington 98040, or use *check-off* on page 110.

switchable keyer

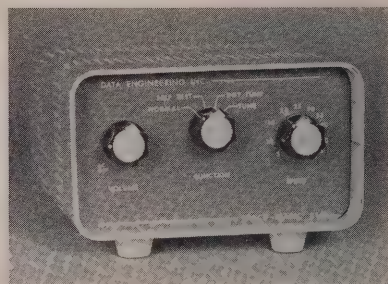

The Space-Matic 21-B electronic keyer is the only non-reprogrammable keyer that lets you select your particular input keying preference. With three switches, you can select from a keyer with no dot or dash memory, just a dot memory, just a dash memory or with both dot and dash memories — all with or without automatic character and word spacing.

The unit features iambic keying, jam-proof spacing and self-completion.

The unit can be used with any key, features a regular tune position and a dot tune position for ssb transmitters. An adjustable monitor is built in, the unit is rf-proofed and can be run from 12 Vdc or 117 Vac. There are many other features of this \$89.50 keyer. Details are available by writing to Data Engineering, Inc., Ravensworth Industrial Park, 5554 Port Royal Road, Springfield, Virginia 22151 or by using *check-off* on page 110.

know this sign



To most people this is a symbol from Greek mythology. But to hundreds of thousands of active amateurs, Pegasus is the symbol of the Radio Amateur CALLBOOK the single most useful operating reference for active amateur stations. The U.S. Edition lists over 285,000 Calls, Names and Addresses in the 50 States and U.S. possessions while nearly 200,000 amateur stations in the rest of the World are listed in the DX edition.

Both editions contain much other invaluable data such as World Maps, Great Circle Maps, QSL Managers around the World, ARRL Countries list and Amateur Prefixes around the World, Time information, Postal Information and much, much more. You can't contest efficiently, you can't DX efficiently, you can't even operate efficiently without an up to date CALLBOOK.

To make the CALLBOOK even more valuable, three supplements are issued each year which bring your copy completely up to date every three months. These are available at a modest extra cost. Full details in every CALLBOOK.

Get your copies of the big new 1973 CALLBOOKS today.

US CALLBOOK
(less service editions)
Just \$8.95

DX CALLBOOK
(less service editions)
Just \$6.95

US CALLBOOK
(with service editions)
\$14.95

DX CALLBOOK
(with service editions)
\$11.45

Mail orders add 50¢ per CALLBOOK postage and handling.

See your favorite dealer or send today to:

WRITE FOR
FREE
BROCHURE

RADIO AMATEUR
callbook INC.
Dept. E 925 Sherwood Drive
Lake Bluff, Ill. 60044

INCREASE YOUR TALK POWER!

PROVEN ON-THE-AIR PERFORMANCE



MODEL ACA-1

\$49.95 KIT

ASSEMBLED

\$69.95

MODEL ACA-1 AUDIO COMPRESSOR features 45 DB compression range ■ Flat 20-20,000 Hz response ■ Extremely low distortion ■ Front panel compression meter and in/out switch ■ Accepts both high and low-impedance mikes ■ Easily installed in mike line ■ 110-volt a.c. or 12-volt d.c. operation ■ Only 5" W x 2 1/4" H x 4 1/2" D.

MODEL ACP-1

\$24.95 KIT

ASSEMBLED

\$34.95



MODEL ACP-1 COMPRESSOR-PREAMP has 30 DB compression range ■ Flat 20-20,000 Hz response and low distortion ■ Designed for high-impedance mikes ■ Easily installed in mike line ■ 9-volt battery operation ■ Only 4" W x 2 1/2" H x 3 1/2" D.

IDEAL FOR TAPE RECORDERS!

Try one of these compressors as an automatic recording-level control. Used by recording studios, schools, and radio-tv stations. Great for p.a. systems, too!

3-CHANNEL WWV RECEIVER

(5, 10, and 15 MHz)



\$74.95 KIT

ASSEMBLED

\$99.95

0.25 microvolt sensitivity ■ Crystal controlled ■ 110-volt a.c. or 12-volt d.c. operation ■ Compact size only 4 1/2" W x 2 1/2" H x 5 1/2" D.

Send check or money order, plus \$1.50 for shipping anywhere in U.S.A. California residents add 5% sales tax.

DEALER INQUIRIES INVITED





CARINGELLA ELECTRONICS, INC.
P.O. Box 327 □ Upland, California 91786
Phone 714-985-1540

W6SAI's Antenna Books

Bill Orr's Newest **WIRE ANTENNAS** for Radio Amateurs

This 192 page book describes over 40 horizontal, vertical, and multi-band trap antennas. Invisible antennas for apartment houses, high gain beam antennas. Covers novice antennas, tuners and ground systems. It's all here in this exciting new book by "the antenna expert."

Only \$3.95 ppd.

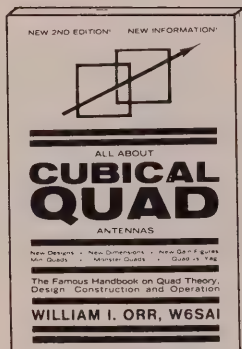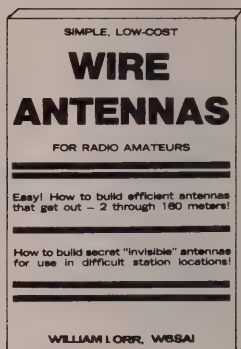

The "bible" on Quads

ALL ABOUT CUBICAL QUAD ANTENNAS

Long considered "THE BOOK" on Quads this latest edition has more information on these popular antennas than you will find anywhere else. Everything you need to design, build and adjust your Quad for top performance.

- Revised gain figures for Quads
 - Delta Quad, Swiss Quad, Birdcage Quad
 - Analysis of Quad vs. Yagi — which is best?
 - Miniature Quad construction and performance
 - Monster Quads — power gains up to 14!
 - Correct dimensions for single and multiband Quads, 6 thru 80 meters
 - Improved Tri-Gamma match feeds tri-band Quad efficiently with one line
- PLUS . . .** Exhaustive detail on every aspect of quad antennas

Only \$3.95 postpaid

The complete reference on beams **BEAM ANTENNA HANDBOOK**

For many years the "BESTSELLER" on beam antennas, this handbook covers all areas of the subject, both theory and practice.


This new fourth edition has been updated to insure that the reader has the very latest information available.

It includes many special features such as:

- Correct dimensions - 6 thru 40 meters
- Are 40 meter compact beams worth the effort?
- Exclusive 25 year bibliography of important beam antenna articles

Whether you plan to build or buy — DX or rag chew — you need this book

Just \$4.95 Postpaid

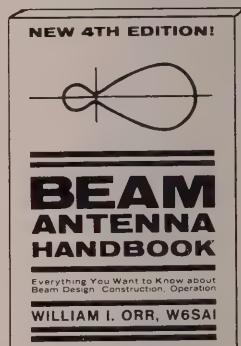

comtec


BOOKS

Greenville, New Hampshire 03048

New for FM'ers


Scanner-Monitor Servicing Data

Contains comprehensive servicing data for 30 of the most popular UHF and VHF receivers now in use, including B & K, Brown-ing, Johnson, Midland, Pace, Pearce-Simpson, Penneys, Realistic, Sonar, and Teaberry. As the first guide ever released for scan-ners and monitors, it is an invaluable aid for service technicians. Its last-minute information includes schematics, voltages, align-ment, parts lists, crystal formula data, pictorial presentations, and general troubleshooting information.

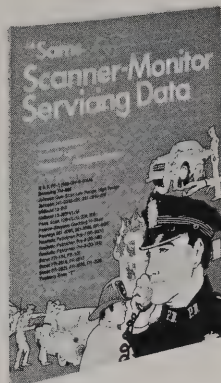

\$4.95 Postpaid

HANDBOOKS We have all three

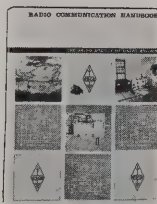

The Radio Amateur's Handbook

ARRL Staff

The standard reference for the radio amateur. Latest 1973 edition covers everything from the basics to such new areas as FM and slow-scan TV. The largest selling technical book ever published.

702 pages, softbound

Only \$4.50

Radio Handbook, 19th Edition

by William I. Orr, W6SAI

Latest updated edition of this famous hand-book which is the standard for engineers, tech-nicians and advanced amateurs. Explains in detail how to design and build all types of radio equipment, RTTY circuits, latest semiconductor and computer circuitry. 896 pages; hardbound.

Only \$14.95

RSGB:

Radio Communication Handbook

Amateur Radio's most complete technical ref-erence. This book covers virtually every phase of radio theory and practise in very complete and useful detail. Whether you use HF or VHF, SSB or RTTY you need this handbook.

832 pages, hardbound

Just \$12.95

SPECIAL HANDBOOK PACKAGE

All 3 for just \$27.50

Save nearly \$5.00

CLOSEOUT SALE!

A SPECIAL PURCHASE ALLOWS US TO OFFER THE 18TH EDITION (JUST NOW SUPERSEDED) OF W6SAI's RADIO HANDBOOK (SEE ABOVE) FOR ONLY \$7.95 WHILE THEY LAST.

comtec

BOOKS

Greenville, New Hampshire 03048

GIANT B-7971 NIXIES (2) with 2 sockets and driver board containing hi voltage transistors. Complete plug-in board as removed from operational equipment. Schematics included. Unbelievable but true . . . just \$2.50 for the complete package. #72S-10 \$2.50



Mod. 28-LPR Typing Reperf, 5 level 100 wpm w/motor **\$35.00**

Mod. 28-LARP non-typing reperf, 5 level less motor **\$10.00**

Mod. 28-LBX-D1 Trans/Dist, with motor, 5 level **\$25.00**

COMBO DEAL — 1 ea. of above 3 units; **\$60.00**

Please add postage for above.

JOHN MESHNA JR. ELECTRONICS P. O. Box 62 E. Lynn, Mass. 01904

15¢ IC BONANZA

Brand new DTL dual inline (DIP) package, factory marked ceramic type. The price is too good to be true. Fully guaranteed and with specs.

- 930 Dual 4 input NAND gate** similar to 7420
- 931 Clocked flip flop** similar to 74110
- 932 Dual 4 input Expand Buff** similar to 7440
- 933 Dual 4 input expander** similar to 7460
- 936 Hex Inverter** similar to 7405
- 945 JK Flip Flop** similar to 74110
- 946 Quad 2 input gate** similar to 7400
- 962 Triple 3 input gate** similar to 7410

15¢ each
Buy \$100 worth and deduct 10%
24 hour delivery guaranteed

RCA MEMORY CORE STACK \$50.00
32x32x9 9 frames with 1024 cores/frame and diode matrix attached. **1024 Memory Area** measures only 2x2 inches. Full stack of 9 planes only **\$50.00**
1024 Core Memory Frames cut from above core stack **6.00 ea.** postpaid.



CAMP ALBERT BUTLER RADIO SESSION

14th year - July 28th - Aug. 10th

Courses Taught: General Theory and Code
Advanced Theory and Code
Amateur Extra Theory and Code

Golf privileges at New River Country Club; also fishing!
TRULY A VACATION WITH A PURPOSE!!!

People attended from the following states and areas:
North Carolina, South Carolina, Missouri, Tennessee, Utah, Florida, Oklahoma, West Virginia, Alabama, New Hampshire, Iowa, District of Columbia, Vermont, Arizona, Indiana, Ohio, New Jersey, New York, Massachusetts, Maryland, Virginia, Illinois, Michigan, Georgia, Kansas, Mississippi, Nebraska, Maine, Kentucky, California, New Mexico, Arkansas, Texas, Wisconsin, Louisiana, Oregon, Connecticut, Minnesota, Pennsylvania.

OUT OF STATE:

Puerto Rico; Saskatchewan, Canada; Ontario, Canada; Quebec, Canada; Granada, Spain; London, England; Geneva, Switzerland; Netherland, Antilles; St. Croix, Virgin Islands.

C. L. Peters, K4DNJ, Executive Director
Gilvin Roth Y.M.C.A., Elkin, North Carolina 28621
Please send me the Booklet and Application Blank for the Camp Albert Butler Radio Session.


Name _____ Call _____
Address _____
City/State/Zip _____

Model 372 Clipreamp



Increase your talk power without exceeding legal limits. The Model 372 Clipreamp will keep your audio levels uniform for maximum efficiency of your transmitter. Compression level variable to meet your requirements.

PRICE **ONLY \$19.95**

See your dealer or write:
Barker & Williamson, Inc. 
Canal Street, Bristol, Pa. 19007

TTL OPERATING RULES **\$ 0.50**

MINITRON 5-VOLT 16-PIN DIP READOUT

7-SEGMENT W/RH DECIMAL **\$ 3.25**
± 1 W/RH DECIMAL **\$ 3.25**

DIGITAL CLOCK SEMI-KIT **\$ 32**

15 IC'S & 4 MINITRONS (ONLY) + RED FILTER & INSTR.

DIGITAL CLOCK INSTRUCTIONS ONLY **\$ 1.50**

QUAD OP AMP LM 3900 **\$ 1.15**

REGULATOR 5-VOLT 1-AMP μ A 7805 **\$ 2.50**

Arizona Semiconductor

PO BOX 112 GOODYEAR, ARIZONA 85338

SBE

feature after feature after feature


There's a new enjoyment horizon waiting on 420-450MHz, an amateur band 7½ times wider than 144-148MHz! Here's wide open space for the ragchewer—paradise for the antenna experimenter. With half-wave antennas only about a foot in length, "dream beams"—the kind that literally **drip** with gain—become practical realities.

The highly knowledgeable repeater group has, of course, had equipment operating in this band for years. However, SB-450, SBE's exclusive, all-new FM transceiver gives the amateur something he has long needed, equipment with small size, convenience and performance characteristics considered to be indigenous to the "DC" bands. It is certain that repeater and 450MHz band activity will be given a big boost with this fine unit.


Beautifully constructed, book size, the SB-450 has 12 channel capability, delivers 5 watts FM output. It's all solid-state—no warmup—low drain from 12V car battery (operates on 115VAC for base station use with available accessory supply). Two sets of crystals are supplied for repeater and simplex operation.

Try UHF! Try SB-450! Enjoy!


SB-450 UHF/FM TRANSCEIVER

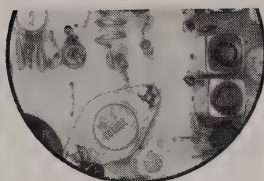

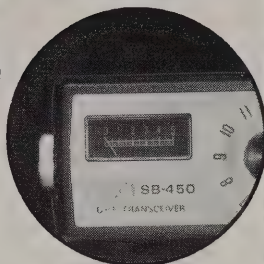
All solid state,
1-SCR, 4-IC's,
29 transistors



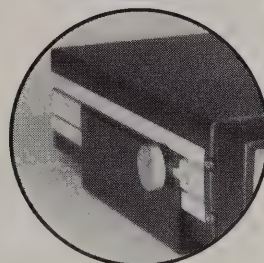Panel meter
shows relative
response on
receive — power
output on
transmit



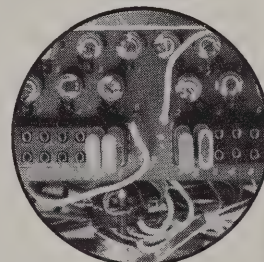
Housing slides in
and out of fixed
bracket, taper
locks with
knurledge
thumb screws.



Two sets of
crystals are
supplied.
Transmit and
receive
crystals have
individual
trimmers for
exact frequency
centering



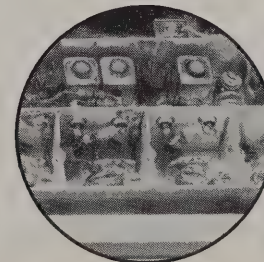Uses exclusive
SBE Super Shape
crystal lattice
BP filter



Silver plated
brass shielded
construction.

SBE

**LINEAR
SYSTEMS INC.,**
220 Airport Blvd.,
Watsonville, CA
95076

TX 144-220 TRANSMITTER KIT



A one watt exciter using four RF transistors, two diodes, and one integrated circuit. The RF transistors are operating well below their ratings allowing long keying periods without damage. The exciter may be used alone as a transmitter or with our PA-144 or 220 amplifier for a 15 watt station. Some of the features are:

- Typically 1½ watts output at 12.6 volts (1 watt on 220)
 - Adjustable deviation to 10 KHz
 - Audio clipping and active filter
 - Crystal netting trimmer
 - Double tuned RF stages for a clean signal
 - Standard 12 MHz crystals (14 MHz for 220)
 - Zener regulated oscillator
 - Provisions for metering each RF stage
 - Predrilled and tinned glass circuit boards
 - Measures only 2" x 6" x 1"

Order TX-144 or TX-220, \$29.95; PA 144 or PA-220, \$29.95. Add \$1.00 postage and handling for each kit ordered. New York state residence add sales tax.



VHF ENGINEERING

1017 CHENANGO ST. BINGHAMTON NY 13901

USED TEST EQUIPMENT

All checked and operating unless otherwise noted, FOB Monroe. Money back (less shipping) if not satisfied.

HP100D-Freq. stand. w/scope-Acc. 1ppm	125
HP100ER Freq. stand. w/scope-Acc. .05ppm	195
HP212A-Pulse Gen. var. width and rate	65
HP430CR Microwave pwr. mtr-rack mnt.	50
HP522B-Freq. Counter-10Hz-120kHz-digital	45
L&N 7592 Voltbox 3-750v Acc. .02%	60
NE 14-20C-Freq.-counter (sim. HP524C)	209
PRD707 Broadband Microwave osc. .9-2.2GHz 170	
PRD708 Broadband Microwave osc. 2-4.2GHz 170	
Republic VA260 Q-mtr (sim. Boonton 160A) 185	
Singer SPA-1 Spec. Anal w/ps less rf unit	375
Singer SSB-4 SSB Spec. Anal complete. 0-40MHz coverage — 10Hz resolution	1465
Solitron 200A SCR tester-checks anode, gate volts current, leakage and holding	165
Stoddart NM10A (URM-6) RF intens mtr 10-250kHz, complete with acc.	630
Stoddart NM20A (PRM-1) RF intens mtr .15-25MHz, complete with acc.	825
Stoddart NM52A-RFI mtr, .375-1gHz, w/acc.	985
Tek RM15-DC-15MHz GP scope	295
Tek 181 Time mark generator	95
Tek 190A Const. Ampl. Sig. Gen .35-50MHz 125	
Tek 531 DC-15MHz scope-takes letter plug-in 360	
Tek 945 (mil 545) 30MHz scope w/dual trace 525	
Weinschel 70 Prec RF step attn DC-1gHz	625
Weinschel PB-1A Prec RF power bridge	875
SG24/TRM3 Sweep Gen. 15-400 MHz, CW, AM, FM Xtal markers, scope-Dev. to 20%	245
TS268D/U Crystal diode test set (1N21, etc.) ..	25
TS-403A-Sig. Gen. (HP616) 1.8-4gHz	385
URM 7 RI-FI mtr (sim. NF-105) 20-400MHz	750
URM-26 Stand. Sig. Gen. 3-400MHz	225
USM24C Scope-8MHz, time-base, triggered 125	
(Send SASE for complete list)	

GRAY

Electronics

P. O. Box 941, Monroe, MI 48161

Specializing in used test equipment

Central New York Specialty Headquarters

**FM by STANDARD COMMUNICATIONS
and CLEGG**

ANTENNAS by HY-GAIN

Quality-Selected Used Ham Gear

Write for listing, updated twice monthly

CFP ENTERPRISES

866 Ridge Road

Ludlowville, N. Y. 14862

STAR-TRONICS

**INDUSTRIAL AND GOVERNMENT
ELECTRONIC SURPLUS**

PARTS & PIECES FOR SCHOOLS, SHOPS, HAMS & HOBBYISTS

**SEND FOR OUR LATEST ALL DIFFERENT
MONTHLY PICTURE CATALOG. NOW!**

Box 17127, Portland, Ore. 97217

SAROC

9th annual fun convention

Best of Las Vegas — Best of Amateur Radio

January 3-6, 1974

SAROC Box 73 Boulder, Nev. 89005

MAN 1

LED

- high brightness--350ft-L @20ma
- single plane, wide angle-viewing---150°
- standard 14 DIP
- long life---solid state
- operates with IC voltage requirements
- displays all digits and 9 distinct letters



\$4.25 EACH

7400 series DIP

7400	.25	74H11	.50	7451	.25	74H74	.85
74L00	.35	7413	1.75	74L51	.35	7475	1.15
74H00	.35	7420	.25	74H51	.35	7476	.55
7401	.25	74L20	.35	74H52	.40	74L78	1.00
74H01	.35	74H20	.35	7453	.25	7480	.50
7402	.25	74H22	.50	74H53	.40	7483	1.15
7403	.25	7430	.25	7454	.30	7486	.65
7404	.25	74L30	.35	74L54	.35	7489	3.00
74L04	.35	7440	.25	74L55	.35	7490	1.00
74H04	.35	74H40	.40	7460	.25	7491	1.15
7405	.25	7441	1.30	74L71	.50	7492	.90
74H05	.35	7442	1.00	7472	.40	7493	.90
7406	1.00	7446	1.50	74L72	.50	7495	1.15
7408	.40	7447	1.50	7473	.55	74L95	2.00
74H08	.50	7448	1.25	74L73	.80	74107	.55
7410	.25	7450	.25	7474	.40	74153	1.75
74L10	.35	74H50	.40	74L74	.80	74192	2.25
						74193	2.00
						74195	1.00

all IC's shipped within 24hrs.


Schottky TTL \$3.00 EACH

- 82S30 8 input multiplexer
- 82S33 2 input 4 bit multiplexer
- 82S41 quad EX/OR element
- 82S42 4 bit comparator
- 82S62 9 bit parity gen./checker
- 82S67 2 input 4 bit multiplexer

CD-3 universal counter

Can be programmed to count to any modulus 2-9 for one kit, 2-99 for two kits, etc. Includes board, 7490, 7447, RCA DR2010 Numitron display tube and five programming components. Full instructions included - perfect for displaying second, minutes and hours, etc.

KIT \$8.95

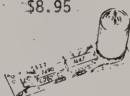

CD-2 digital counter

Unit includes board, 7490, 7475 quad latch, 7447 seven segment driver, and RCA DR2010

KIT \$9.95
ASSEMBLED 12.00

8000 series TTL DIP

8200	4 bit comparator	1.60
8210	8 line to 1 line selector	1.40
8220	parity gen/checker	1.00
8223	256 bit programmable ROM	7.50
8230	8 input multiplexer	2.00
8233	2 input 4 bit multiplexer	1.75
8242	4 bit comparator	1.00
8251	BCD to decimal decoder	1.00
8261	fast carry extender	2.00
8266	2 input 4 bit multiplexer	1.50
8270	4 bit PI, SI, PO, SO	2.00
8271	4 bit shift register	2.00
8273	10 bit SI, PO register	3.00
8274	10 bit PI, SO register	3.00
8280	45MC presetable decade counter	1.15
8281	45MC presetable binary counter	1.15
8290	presetable dec. counter 75MC	3.50
8292	presetable dec. counter 10MC	.90
8520	25MC divide by "N" 2 to 15	2.00
8551	tri state quad latch	2.00
8570	8 bit SI, PO	2.50
8590	8 bit PI, SO	1.50
8275	quad bistable latch	.90

748	op amp T05	1.50
NE555	prec. timer MINI	1.25
CA3065	TV/FM sound system DIP	.75

All IC's are new and fully tested - leads are plated with gold or solder. Orders for \$5 or more will be shipped prepaid. Add 35¢ handling and postage for smaller orders. California residents add sales tax. IC orders are shipped within two workdays of receipt of order - kits are shipped within ten days of receipt of order. MONEY BACK GUARANTEE ON ALL GOODS SOLD.....

BABYLON ELECTRONICS

P.O. BOX J, CARMICHAEL, CALIF.
95603 (961) 966-2111

linear

LM100	positive DC regulator T0-5	.80
NE526	high speed comparator DIP	1.00
NE560	phase lock loop DIP	3.25
NE561	phase lock loop DIP	3.25
NE565	phase lock loop T0-5 or MINI	3.25
NE566	function generator T0-5 or MINI	3.50
NE567	tone decoder T0-5 or MINI	3.50
709	popular op amp DIP	.35
710	voltage comparator DIP	.50
711	dual comparator DIP	.75
723	precision voltage reg. DIP	1.00
5558	dual 741 op amp MINI	1.00
810	dual op amp DIP	.80
747	dual 741 op amp DIP	1.00
LM302	op amp voltage follower T0-5	1.25
LM308	op amp T0-5	2.00
LM311	comparator T0-5	1.50
LM380	2W audio amp DIP	1.50
LM703	RF-IF amp epoxy T0-5	.80
LM309K	5V-1A power supply module T0-3	2.50
LM309H	5V-200ma power supply T0-5	1.00

calculator on a chip 40 pin DIP

Add, subtract, multiply, and divide
12 digit display and calculate
Chain calculations
True credit balance sign output
Automatic overflow indication
Fixed decimal point at 0, 2, 3, or 4
Leading zero suppression
Complete data supplied with chip


SILICON
signal diodes
100 PIV - 80 ma
60 for \$2.50

\$9.95




RCA 2010

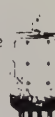- digital display tube
- incandescent 5V
- 7 segment
- .6" high numeral
- visible at 30 feet
- left hand decimal
- 9 pin base (solderable)



EACH \$ 5.00
5 FOR 20.00

The incomparable *ALPHA 77* by ETO

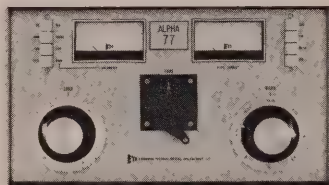

The finest amplifier ever offered for Amateur, Commercial & Military service. 3000 watts PEP continuous-duty. Perfect companion to the CX7A.

Write for information & Barry's Best Deal

ALPHA PA-70-V LINEAR AMPLIFIER Write or Call

DRAKE

TR4/C new, \$599.95 W4new, \$ 61.95
R4C Rec. \$499.95 TR22 new, \$199.95
T-4XC Trans. \$530.00
AA-10 2 meter 10 watt linear amp. for use with TR-22, etc. \$ 49.00
AA-22 2 meter 25 watt linear amp. plus pre-selector, for improved sensitivity and rejection \$149.95
2B with 2BQ Multiplier Write

TEN TEC

All below is new merchandise

ARGONAUT MODEL 505 \$288.00
ARGONAUT 405 LINEAR AMP. 50w. out \$149.00
210 POWER SUPPLY for Argonaut 505 only \$ 24.95
250 POWER SUPPLY, powers 505 & 405 \$ 49.00
315 RECEIVER 10-80 meters SSB, AM, CW \$229.00
CW FILTER FOR 315 \$ 14.95

All above in stock

AC4 SWR Bridge KR20 \$ 59.95
 KR40 \$ 89.95
KR1 \$ 18.95 PM2B \$ 64.95
KR2 \$ 12.95 PM3A \$ 79.95
KR5 \$ 34.95 AC5 Tuner \$ 8.95

COLLINS

MP1 mobile supplygood, \$ 95.00
30L1 spare parts kit less chassis/cab. etc., Write

HALLICRAFTERS

FPM-300new, \$595.00

LINEAR SYSTEMS

SB-36 5 Band 500W SSB/CW Digital readout transceiver complete with AC power supply and speakerBrand new in stock, Write

DYCOMM

2 Meter Amplifiers (Power ratings approx.)
BRICK BOOSTER, 2w in 35w out \$ 79.95
BLOCK BOOSTER, 10 in 50w out, new, \$ 99.95
 demos, \$ 79.95

CLEGG FM-27B NO XTALS 25w out Synthesized

Write for fantastic
trade in or real deal
Latest Model

INSTRUMENTS

GR 1001A SIGNAL GENexcellent, \$425.00
DIGIPET 60 digital freq. counter, with 160 scaler. Range 1 kHz - 160 MHz \$349.00
FR-114U 6 digit E-put meter, frequency .1 - 10k, .0001 to 10 sec.like new, \$195.00
SIMPSON 270 VOM with probes & leather case new, \$ 81.00
SIMPSON 2701 Digital Multimeter reg. approx. \$895 Special, \$595.00
Hewlett Packard 236A Audio osc., 50 Hz-560 kHz excellent/like new, \$175.00

12 VOLT DC POWER SUPPLIES: 110 AC INPUT

MODEL 102, is a 4 amp overload protected power supply that automatically resets itself when the overload is removednew, \$24.95
MODEL 104R, is a regulated power supply with the same electronic overload protection as the model 102. MODEL 104Rnew, \$34.95
MODEL 107M is a heavier duty supply with the same features as the Model 102 but puts out 6 amps, useful for Clegg 27 series, etc.new, \$27.95

INVERTER/CONVERTER:

MODEL 612 is a special purpose unit to provide 12 VDC negative ground power in automobiles with either 6 volt negative ground or 12 volt positive ground. 10 amp surge, 3 amp continuousnew, \$22.95
INVERTER, 12 volt DC input, 115 volt AC out, Model 12-115 solid state power supply, 200 watts continuousnew, \$ 59.95

TEMPO

2 Meter Linear Amplifiers, 502, 5-12 watts input, 35-55 watts output \$105.00
1002-313 1-2½ watts input, 120-130 watts output \$235.00
802-B 1-2½ watts input, 80-90 watts output \$195.00
TEMPO FMH 2 Meter Transceiver, 2 watt, 6 channel, handheldnew, \$189.00

BIRD

4350 80-10M 2KW Ham Mate \$ 79.00
4351 80-10M 1KW Ham Mate \$ 79.00
4352 6-2M 400W Ham Mate \$ 79.00
43 Wattmeter \$100.00
BIRD 43 SLUGS, spec. freq./power \$ 35.00

Large stock of inductors by B & W and Air Dux. Write or Order.

CASH PAID . . . FAST! For your unused TUBES, Semiconductors, RECEIVERS, VAC. VARIABLES, Test Equipment, ETC. Write or call Now! Barry, W2LN1. We Buy!

We ship all over the World.

☐ Send for Green Sheet Supplement 23.
Send 10¢ plus 40¢ postage & handling (refund 1st order).

BARRY ELECTRONICS CORP.

DEPT. H-4 — PHONE A/C 212-925-7009
512 BROADWAY, NEW YORK, N. Y. 10012

MISC.

2 METER VHF DUMMY LOAD/WATTMETER
Good up to 15 watts — w/SO-239 CONNECTOR \$19.95

LAFAYETTE HA-460 6 meter transceiver with
VFO, 20 watt, AC & DC pow. sup., new, \$ 95.00
NC-400 540 kHz - 31 MHz 7 bands USB, LSB
CW fair to good, \$150.00
HEATH DX-100, 10, 11, 15, 20, 40, 80, 160M
100 watts AM & CW

checked out w/manual, \$ 95.00
HEATH HP-23A AC Supplylike new, \$ 45.00
HEATH SHAWNNEE, 6 meter transceiver, Model
HW-10, 10 watts RF out, built-in 117 AC & 6 or
12 volt DC power supply, built-in VFO \$ 95.00
SWR BRIDGE COUPLER, DC-500 MHz (no indi-
cator) full amateur power

With N fittings \$ 9.95

With BNC fittings \$10.95

MODEL 70 ROBOT SSTV Monitor in stock Write

ANTENNAS

MOSLEY LANCER "1000" mobile antenna, all
coils 10, 11, 15, 20, 40, 80 good, used,
complete, \$ 50.00

MOSLEY TA-36 write
2M MAGNETIC MOUNT w/RG58 & PL259

with 10 ft. RG 58 ready to go \$ 9.95

14AVQ/WB VERTICAL \$ 47.95

18AVT/WB VERTICAL \$ 69.95

HY GAIN 2 METER, 15 element beam write

NEW ULTRA BALUN 1:1 \$ 9.95

C.D. HAM "M" ROTATORS, new, complete \$99.95

HAM "M" CABLE@ 12¢/ft.

C.D. TR-44 ROTATORS, new, complete \$63.95

CABLE FOR TR-44 6¢/ft.

RG-8A/U 100 ft. rolls. VHF connector PL-259

one end Type "N" (UG-21E/U) other end \$ 12.50

RG8A/U — 65 feet with PL-259 connectors on

each end \$9.50

Authorized factory dealers for Antenna Special-

ists, CushCraft, Gam, Heights Towers, Hy Gain,

Mor-Gain Antenna, Mosley, Newtronics, Tri-Ex,

Rohn, E-Z Way

B & W Vacationer apartment house antenna, 2,

6, 10, 15 & 20 meters. Hang out your window.

Take along on your vacation \$ 24.95

DX ENGINEERING SPEECH COMPRESSORS

DIRECT PLUG-IN FOR COLLINS 32S \$79.50

DIRECT PLUG-IN FOR KWM — 2 \$79.50

DIRECT PLUG-IN FOR DRAKE TR3 OR DRAKE

TR4 \$98.50

BARKER & WILLIAMSON

Dummy Load - Wattmeters - 520

333 DC - 300 MHz, 1000 watts int. \$139.95

334A DC - 230 MHz, 1500 watt \$169.95

374 DC - 300 MHz, 250 watt int. \$ 79.95

Transistorized Little Dipper, battery operated,

2 MHz-230 MHz continuous $\pm 3\%$ accuracy

with modulation \$ 94.50

850A, 852 Inductors \$ 59.95

851 Inductor \$ 24.95

425 Low Pass Filter, 10-80 meters \$ 24.95

210 Audio Osc., ideal for lab & broadcast

..... \$329.95

410 Distortion Meter, ideal for lab & broadcast

..... \$369.95

AM-141 Amplifier, 2000 watts RF output, con-

tinuous 2-18 MHz, complete with coils and

833-A's. Built-in 115 VAC Supply, unused

..... \$950.00

E. F. JOHNSON

275 watt Matchbox complete with directional

coupler and indicator, 10-80 meters, new \$94.95

Same as above but 2KW PEP, 1 KW AM

new, \$154.50

151-1.4 Variable Capacitor, 250 pF, medium

Xmitting type \$2.95 ea.

.....

Luxo-Lil swinging lamp, beautiful desk lamp

..... \$ 15.00

.....

Write for free Deluxe B & W Catalog

BUILDERS!

Barry has lots of James Millen and National

Radio parts in stock.

Write for Barry's latest Green Sheet, No. 23.

.....

A New Magazine?

Not really. New in the U.S.A. perhaps,
but very well known in Great Britain and
now being offered to you here.

RADIO CONSTRUCTOR is almost exclu-
sively construction material. Clearly writ-
ten, concise articles give you full details
on:

- Audio Construction Projects
- Receiver Construction Projects
- Transmitter Construction Projects
- Test Equipment Projects
- Radio Control Projects
- ... and much more

Try a subscription to this interesting
magazine, we are sure that you will not
be disappointed.

ONE YEAR SUBSCRIPTION — \$7.00

Write

RADIO CONSTRUCTOR

Greenville, N. H. 03048

SPACE-AGE TV CAMERA KITS & PLANS



BE A PIONEER IN HOME TELECASTING! Build your own
TV CAMERA. Model XETA, Series D, \$119.95 pp. Self-
Start. Step-by-step construction manual. High quality.
Connects to any TV without modification. Ideal for home,
experimenters, education, industry, etc.

PHONE OR WRITE FOR CATALOG.

DIAL 402-9807-3771

Many other kits, parts and plans available including starter
kits, focus/drift, coils, video, tubes, const. plans, etc.

1301 BROADWAY, N.W. **ATV Research** DAKOTA CITY, NEBR. 68731

NEW - 440 MHz PREAMPS

\$54.95

POSTPAID

432PA-1



Two stage preamps use KMC Bipolar and Mos-
fet Transistors. 20db gain, 20 MHz bandwidth.
These are high quality preamps suitable for the
most demanding applications. AC models have
die cast case, others have metal enclosure.

432PA 3.5db NF 12VDC \$29.95
432PA-1 3.5db NF 117VAC \$54.95
432PC 1.5 to 2.0db NF 12VDC \$69.95
432PC-1 1.5 to 2.0db NF 117VAC \$94.95
Write for our new catalog.

JANEL

LABORATORIES

P. O. BOX 112
SUCCASUNNA, N. J. 07876
201-584-6521

ANNOUNCING
A NEW DEALER FOR
YAesu FT 101
AND OTHER MODELS
RACOM ELECTRONICS, INC.
15051 SE 128 STREET - RENTON, WASH. 98055
Tel: 206-AL 5-6556

G&G CATALOG MILITARY ELECTRONICS

24 PAGES, crammed with Gov't Surplus Electronic Gear - the Biggest Bargain Buys in America! It will pay you to for your copy - Refunded with your first order.

SEND 25¢

BRAND NEW BC-645 TRANSCEIVER

EASILY CONVERTED FOR 420MC OPERATION
This equipment originally cost over \$1000. You get all in original factory carton.



Dependable Two Way Communication more than 15 miles.

- FREQUENCY RANGE: About 435 to 500 Megacycles.
- TRANSMITTER has 4 tubes: WE-316A, 2-6F6, 7F7.
- RECEIVER has 11 tubes: 2-955, 4-7H7, 2-7E6, 3-7F7.
- RECEIVER I. F.: 40 Megacycles.
- SIZE: 10 1/2" x 13 1/2" x 4 1/2".

Makes wonderful mobile or fixed rig for 420 to 500 Mc. Easily converted for phone or CW operation

"SPECIAL PACKAGE OFFER"

BC-645 Transceiver, Dynamotor and all BRAND NEW, accessories below, including conversion in while stocks last. **\$26.95**

F.O.B. N.Y. City or Ogden, UT for Savings on Freight Charges.

Accessories for BC-645 transceiver
PE-101C Dynamotor, 12-24 V (easily converted to 6 volts). Mounting for PE-101C Dyna-
motor
UHF Antenna assemblies (set of 2)
Complete set of 11 connectors
Control Box BC-646
Mounting for BC-646 ctr. box.

TRANSCEIVER ONLY \$16.95


BC-1206-C RECEIVER Aircraft Beacon Receiver 200 to 400 Kc. Operates from 24V DC 1.5A. Continuous tuning, vol control, on-off switch and phone jack. Very sensitive. Compact. Complete with tubes, NEW **\$12.50**



CRYSTAL BARGAINS

Depend on ...

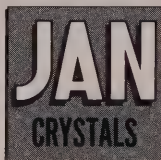We supply crystals from 16KHz to 100MHz. Over 6 million crystals in stock.



DIVISION OF BOB WHAN & SON ELECTRONICS, INC.

SPECIAL

Crystals for most amateur 2-Meter F.M. Transceivers:

\$3.75 Each

Inquire about quantity prices. Order direct. Send check or money order.

For first class mail add 15¢ per crystal...for airmail add 20¢ ea.

2400 Crystal Dr.
Fort Myers
Florida 33901
(813) 936-2397

Send 10¢ for new catalog with oscillator circuits and lists of thousands of frequencies in stock.

SPECIALS! CRYSTALS FOR:

Frequency Standards	
100 KHz (HC13/U)	4.50
1000 KHz (HC6/U)	4.50
Almost All CB Sets, Trans. or Rec. (CB Synthesizer Crystal on request)	2.50
Any Amateur Band in FT-243 (Except 80 meters)	1.50
80 Meter Range in FT-243	4 for 5.00
Color TV 3579.545 KHz (wire leads)	2.50
	1.60
	4 for 5.00

HANDMIKE

Rugged, heavy-duty carbon handmike with press-to-talk switch. Equipped with 4-ft cord & phone plug. SPECIAL
NEW, boxed, Each **\$1.88** 2 for \$3.25



HEADSET Low impedance. With large chamomise ear cushions. 4-ft cord and plug. Reg. \$12.50. Our Special Price **\$2.95**
Less ear cushions..... \$1.95
High impedance adaptor for above... \$.69




SCR-274-N, ARC-5 COMMAND SET HQ!

Freq. Range	Type Complete with Tubes	Exc. Used	Like New	BRAND NEW
RECEIVERS				
190-550 Kc	BC-453	\$16.95	\$23.50	—
6-9.1 Mc	BC-455	—	—	—
1-5.3 Mc	R-25	—	—	\$21.50
TRANSMITTERS	Complete with Tubes			
4-5.3 Mc	BC-457	\$8.95	—	\$11.95
5-3.7 Mc	BC-458	\$8.95	—	\$11.95

CRT AGEING & CHECKING TESTER

\$6.95

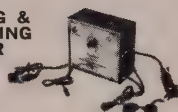

WILLARD 2-VOLT STORAGE BATTERY (Model 20-2)
Rated at 20 ampere hours. Compact, rechargeable, fine for models. **\$2.79**



CATHODE RAY TUBES All New in Original Carton

STANDARD MAKE

3AP1*	2.95	5MP1	2.75
3FP7*	1.45 ea.	9GP7	4.95
3CP1	1.98 ea.	*Sold in Lots of 3 Only	
3" Shield	\$1.49	5" Shield	\$3.25
3" and 5" Sockets			69¢ ea.
3" and 5" tubes sold with shields and sockets only.			



TERMS: F.O.B. NYC, 25% deposit with order, balance COD or remittance in full. MINIMUM ORDER \$5.00. Subject to prior sale and price change

G&G RADIO ELECTRONICS COMPANY

45-47 Warren St. (2nd Fl.) New York, N.Y. 10007 Ph. 212-267-4605

FM Schematic Digest

A COLLECTION OF
MOTOROLA SCHEMATICS

Alignment, Crystal, and Technical Notes
covering 1947-1960

136 pages 11 1/2" x 17" ppd **\$6.50**

S. Wolf

P. O. Box 535

Lexington, Massachusetts 02173

DIGIPET-60

SEE NOV. '72 "CQ" REVIEW

Digipet-60

Frequency Counter

1 KHz-60 MHz
(130-160 MHz with optional converter)
Reg. \$299



A frequency counter with a range of 1 KHz to 60 MHz (or 130-160 MHz when used with our Digipet-160 Converter). With a resolution of 1 KHz or 1 Hz (at 1 ms. or 1 s. gate times). It can be operated on either AC or DC, with complete overload protection. Plus a stability aging rate of 1 part in 10⁶/week. And the whole unit is a mere 7 1/2" deep by 2 1/2" high!

Superb precision quality at LESS THAN KIT PRICES. Call or write for literature and trade in or our LOW INTRODUCTORY PRICE. 1 YEAR WARRANTY. NO ONE ANYWHERE BEATS OUR DEAL!



AMATEUR-WHOLESALE ELECTRONICS
8817 S.W. 129 Terrace • Miami, FL 33156
Days (305) 233-3631
Nights-Weekends (305) 666-1347

CW or RTTY, whichever way you go, HAL HAS TOP QUALITY YOU CAN AFFORD!



TOP QUALITY RTTY...WITH THE HAL MAINLINE ST-6 TU. Only 7 HAL circuit boards (drilled G10 glass) for all features, plug-in IC sockets, and custom Thordarson transformer for both supplies, 115/230 V, 50-60 Hz. Kit without cabinet, only \$135.00; screened, punched cabinet with pre-drilled connector rails, \$35.00; boards and complete manual, \$19.50; wired and tested units, only \$280.00 (with AK-1, \$320.00).*



TOP QUALITY...WITH THE HAL 1550 ELECTRONIC KEYSER. Designed for easy operation; perfectly timed CW with optional automatic ID for sending call letters, great for DX and RTTY; TTL circuitry, transistor switching for grid block, cathode keying. Handsome rugged crackle cabinet with brushed aluminum panel. With ID, only \$90.00; without ID, \$65.00.*

OTHER HAL PRODUCTS INCLUDE:

ID-1 Repeater Identifier (wired circuit board) . . .	\$ 75.00*
ID-1 (completely assembled in 1½" rack cabinet) . . .	\$115.00*
HAL ARRL FM Transmitter Kit . . .	\$ 50.00*
W3FFG SSTV Converter Kit . . .	\$ 55.00*
Mainline ST-5 TU Kit . . .	\$ 50.00*
Mainline AK-1 AFSK Kit . . .	\$ 27.50*



TOP QUALITY... WITH THE HAL MKB-1 MORSE KEYBOARD.

As easy as typing a letter—you get automatic CW with variable speed and weight, internal audio oscillator with volume and tone controls, internal speaker, and audio output jack. Smooth operation; completely solid-state, TTL circuitry using G10 glass boards, regulated power supplies, and high voltage transistor switch. Optional automatic ID available. Assembled MKB-1, \$275.00. In kit form, \$175.00.*




NEW FROM HAL—TOP QUALITY RVD-1002 RTTY VIDEO DISPLAY UNIT. Revolutionary approach to amateur RTTY... provides visual display of received RTTY signal from any TU, at four speeds (60, 66, 75, and 100 WPM), using a TV receiver modified for video monitoring. Panasonic solid-state TV receiver/monitor, or monitor only, available. RVD-1002, \$525.00; Panasonic TV receiver/monitor, \$160.00; monitor only, \$140.00.*

TOP QUALITY...WITH THE HAL RKB-1 TTY KEYBOARD. Gives you typewriter-easy operation with automatic letter/number shift at four speeds (60, 66, 75, and 100 WPM). Use with RVD-1002 video display system, or insert in loop of any teleprinter, for fast and easy RTTY. Completely solid state, TTL circuitry using G10 glass boards, regulated power supplies, and transistor loop switch. RKB-1 assembled, only \$275.00.*

HAL provides a complete line of components, semi-conductors, and IC's to fill practically any construction need. Send 24¢ to cover postage for catalog with info and photos on all HAL products available.

*Above prices do not include shipping costs. Please add 75¢ on parts orders, \$2.00 on larger kits. Shipping via UPS whenever possible; therefore, street address required.

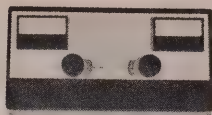HAL COMMUNICATIONS CORP., Box 365 H, Urbana, Illinois 61801



THE HENRY 3K-A

COOL AND EASY MAX.
LEGAL POWER • SSB
CW, RTTY or SSTV
THROUGH COMMERCIAL
RATINGS • 3.5 TO
30MHz • CONTINUOUS
DUTY • SILVER PLATED
PI-L PLATE TANK • DC
RELAYS • ALC • BUILT IN SWR BRIDGE • OUT-
PUT POWER 2 KW MIN. IN COMMERCIAL
SERVICE • THE FINEST COMMERCIAL GRADE
AMATEUR LINEAR AMPLIFIER AVAILABLE ANY-
WHERE IN THE WORLD AT ANY PRICE FOR
ONLY \$1080 • THE HENRY 3K-A • THE LINEAR
FOR THE CX-7A

YOU will never know how little it costs to
own THE incomparable CX-7A or Henry 3KA
until YOU write or phone us and let
us know the trade in deal YOU WANT.
We usually say yes! NO ONE ANY-
WHERE BEATS OUR DEAL.

● Credit terms available on export orders to qualified firms.



signal/one
CX-7A*

exclusive
export
agent
for
signal/one



- 160-10 Meters — 300 Watts
- Transceiver or split frequency with two built in VFOs — CW keyer built in
- IF shift — new superior QRM remover
- IF noise blanker — digital noise frequency readout — superb computer grade construction
- FSK keyer — adjustable output power — broadband tuning — output wattmeter and re-lected power meter **\$2395**

*Service manual CX7-CX7A \$29. — postpaid.

AMATEUR-WHOLESALE ELECTRONICS

8817 S. W. 129 Terrace-Miami, FL 33156

Telephone — days (305) 233-3631

— nights and weekends (305) 666-1347

Q BOARD 5-16 pin ic's
round ic's
Universal PCB designed for modern ic's, transistors,
components—quicker cheaper—epoxy glass—solder
plated and drilled—power and ground buses—
1"x5.6"—make better smaller stackable circuits—
Chronometric Products Dept. H \$3.20 Ca. res.
16530 Ardita Dr. Whittier Ca. 90603 add 5%

THE ULTRA-BAL 2000
NOW -----An extremely rugged, weather-proof BALUN!
• Full 2KW, 3-30 MHZ., 1:1 or 1:4 ratios.
• Special Teflon insulation. May be used
with tuned lines and tuners.
• With dipole insulator and hang-up hook.
ONLY \$ 8.95ppd. (state ratio)
At your dealer or order direct
K.E. Electronics Box 1279, Tustin Calif. 92680

ACTIVE AUDIO FILTERS
CW: IC'S FOR SUPER HIGH PERFORMANCE
Get razor sharp selectivity
No impedance matching BW
(selectable) 180 Hz and
80 Hz Center frequency ...
F = 750 Hz Skirts 60 db
down at 1/2F and 2F 4 op
amps, 2" x 3" PC Board
\$12.95 wired, tested,
guaranteed
LOW PASS:
Resistors set cutoff .5
to 20 kHz. Factory set
for 2.5 kHz; Input imp 1M;
Load > 2K; Gain = 1
Rolloff max 48db/oct, min
40 5 op amps, 2" x 3"
PC Board \$15.95 wired, tested, guaranteed
WRITE FOR FREE SPEC SHEETS! (DEALERS INVITED)
MFJ ENTERPRISES P. O. Box 494
State College, Ms. 39762

**WE PAY HIGHEST
PRICES FOR ELECTRON
TUBES AND SEMICONDUCTORS**
H & L ASSOCIATES
ELIZABETHPORT INDUSTRIAL PARK
ELIZABETH, NEW JERSEY 07206
(201) 351-4200

**CW / RTTY /
REPEATER
IDENTIFIER**
Uses 256 bit read-only-memory programmed for your call
or message. NE555 timers for clock, tone generator and
5 minute timer. Apply 5 volts and COR and it outputs
tone and PTT. Board: \$8 Kit: \$30 Tested: \$35
OTHER BOARDS AVAILABLE:
Two Tone Decoder: \$25 Tested 16 Button Decoder: \$95
Phase Locked Loop RTTY Converter: \$30 RX Generator: \$8
2 Meter Preamp: \$13 8 Channel Scanner: \$25
WRITE FOR FREE FLYER

SIGNAL SYSTEMS
2650 DURANGO DR.
COLORADO SPRINGS
COLORADO 80910
(303) 4750380

Digipet-60 Frequency Counter 1 KHz-60 MHz

(130-160 MHz with optional converter)

only \$299

A frequency counter with a range of 1 KHz to 60 MHz (or 130-160 MHz when used with our Digipet-160 converter). With a resolution of 1 KHz or 1 Hz (at 1 ms. or 1 s. gate times). It can be operated on either AC or DC, with complete overload protection. Plus a stability aging rate of 1 part in 10^6 /week. And the whole unit is a mere 7" deep by 2 1/4" high! In other words, a fine piece of equipment at a terrific price: \$299. From one of the most respected names in electronics, no less. For further information, contact: Miida Electronics, a division of Marubeni America Corp., 2 Hammariskjold Plaza, New York, N.Y. 10017 Phone (212) 973-7152.

Miida



ECHO II



ALL
SOLID
STATE

STOCK
FREQS:
16/76
22/82
28/88
34/94

2 METER AMATEUR REPEATER — ONLY \$600.00

PROVEN STATE OF THE ART DESIGN

INSTALLATIONS WORKING GREAT IN U.S., EUROPE AND ASIA

STOCK FREQS DELIVERED IMMEDIATELY, OTHERS 3-4 WEEKS

WRITE FOR FREE DATA SHEET — FULL MANUAL \$5.00

DYCOMM

948 AVENUE E P.O. BOX 10116
RIVIERA BEACH, FLA. 33404

GROTH-Type

COUNTS & DISPLAYS YOUR TURNS

- 99.99 Turns
- One Hole Panel Mount
- Handy Logging Area
- Spinner Handle Available

PRICES

	POST PAID
TC 2	\$7.00
TC 3	\$7.50
Spinner (-S)	\$1.00
Add \$0.75 for Air or UPS	

Case: 2x4"; shaft 1/4"x3"
Model TC2: Skirt 2 1/8"; Knob 1 1/8"
Model TC3: Skirt 3"; Knob 2 3/8"

R. H. BAUMAN SALES

P.O. Box 122, Itasca, Ill. 60143



OMEGA-T

ANTENNA NOISE BRIDGES

Precision bridges with a broadband signal source permits you to measure both antenna resonant frequency and antenna impedance at the resonant frequency when used with your receiver.

- A must for the serious antenna enthusiast.
- Replace VSWR bridges or other antenna test equipment.
- Get optimum performance from all types of mobile and fixed antennas.

MPQ

INDUSTRIES Model TE 7-01 1-100 MHz
P. O. Box 217 \$29.95 ppd
Hernando, MS. Model TE 7-02 1-300 MHz
38632 \$39.95 ppd

*See you at the
World's Largest
Hamvention!*

28 APRIL 1973

22nd
ANNUAL

DAYTON HAMVENTION

WAMPLER'S HARA ARENA

Dept. H — Box 44

Dayton, Ohio 45401

TECHNICAL SESSIONS • EXHIBITS
LADIES PROGRAM • AWARDS
FLEA MARKET • TRANSMITTER HUNT
BANQUETS

Portables for FM

Think Summer



HT200s: Ready-to-go or kits

Hi Band — \$50 and up

UHF (406-420), exc. cond. — \$100

HT220s: Ready-to-go or kits

Hi Band & UHF — \$140 and up


PT200s — \$125

Makes a great portable,
mobile or base — add a

Dycomm and get up to 100+ W out!



UHF SHOES

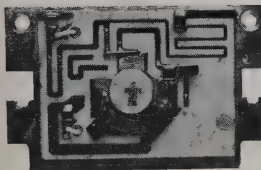

450 MHz PA DECK

$\frac{3}{4}$ W drive for 4W out.

Ready to install in your hand
held. Less drive limiter.

While they last . . . Only \$10

BATTERIES

SPEC 2



SYNTHESIZED

Covers 144.00-147.99

2W Tx; .2 μ V Rx

Combines RP synthesizer

with all Motorola Rx and Tx components

Terms of Sale: Sales to licensed Radio Amateurs for use on Amateur freqs only. All prices FOB Oak Park, IL. Check with order, COD or you can charge to your BankAmericard or Master Charge.



FOR ALL YOUR PORTABLE NEEDS

We are Alexander's sole national
amateur market distributors

In Stock fresh new:

- Ni-Cads
- Alkalines
- Mercurys

NEW! Standard SR-146A Ni-Cad \$38



SPECTRONICS

the FM people

1009 Garfield St.

Oak Park, Ill. 60304

Area Code 312-848-6778



Mon. — Thurs. 9:30-6:00 Fri. 9:30-8:00 Sat. 9:30-3:00 Closed Sundays and Holidays
INQUIRIES WITHOUT ZIP CODE OR CALL LETTERS . . . NO ANSWER

SSB CONVERTER CV-591A: Get upper or lower sidebands from any recvr. OK gtd. w/book \$137.50
 SP-600(*) RECEIVER 0-54-54 MHz continuous, overhauled, aligned, grtd, w/book 250.00

BRAND NEW FREQ-SHIFT TTY MONITOR

NAVY OCT 3: FM Receiver type, freq. range 1 to 26 MHz in 4 bands, cont. tuning. Crystal calib. Reads up to 1500 Hz deviation on built-in VTVM. Cost \$1100.00 each! In original box, with instruct. book & cord. fob Mariposa, Cal. Min. signal needed: 15 mv. Shpg wt 110 lbs 49.50

HIGH-SENSITIVITY WIDE-BAND RECEIVER

COMMUNICATIONS • BUG DETECTION
 • SPECTRUM STUDIES

38-1000 MHz AN/ALR-5: Consists of brand new tuner/converter CV-253/ALR in original factory pack and an exc. used, checked OK & grtd main receiver R-444 modified for 120 v. 50/60 hz. The tuner covers the range in 4 bands: each band has its own Type N Ant. input. Packed with each tuner is the factory inspector's checkout sheet. The one we opened showed SENSITIVITY: 1.1 uv at 38.4 mhz. 0.9 at 133 mhz, 5 at 538 mhz, 4½ at 778 mhz. 7 at 1 ghz. The receiver is actually a 30 mhz IF ampl. with all that follows, including a diode meter for relative signal strengths: an atten. calibrated in 6 db steps to -74 db, followed by an AVC position; Pan., Video & AF outputs; switch select pass of ±200khz or ±2 mhz; and SELECT AM or FM! With Handbook & pwr. input plug, all only 375.00
 CV-253 Converter only, good used w/book 89.50

30 MHz PANADAPTER OK grtd \$137.50

Meas. Corp. #59 Grid Dipper 2.2-420 MHz, 75.00

NEMS-CLARKE #1670 FM Rcvr 55-260 MHz

like new 275.00

WWV Rcvr/Comparator 2½-20 MHz, w/scope 250.00

RECEIVER/COMPARATOR FOR 60 KHz WWVL standardizes to 1 part in 10 billion with inexpensive oscillators 495.00

Attention!

Buyers, Engineers, advanced Technicians:

We have the best test-equipment & oscilloscope inventory in the country so ask for your needs . . . don't ask for an overall catalog . . . we also buy, so tell us what you have. Price it.

R. E. GOODHEART CO. INC.

Box 1220-HR, Beverly Hills, Calif. 90213

Phone: Area Code 213, Office 272-5707

**300 MHz Prescaler w/preamp
 and post amp.**

Gated Marker Generator

**FM Channel Standard
 and Peaking Generator**

300 MHz Counters

Send for free catalog

K-Enterprises

1401 N. Tucker Shawnee, Ok. 74801

WORLD QSL BUREAU

THE ONLY QSL BUREAU to handle all of your QSLs to anywhere; next door, the next state, the next country, the whole world. Just bundle them up (please arrange alphabetically) and send them to us with payment of 5¢ each.

5200 Panama Ave., Richmond, CA USA 94804



KM-420 CW MESSAGE MEMORY
 100 OR 200 CHARACTERS . . . \$299.95



EK-420 C-MOS DELUXE KEYER
 FOR QRP OR KW . . . \$139.95

CURTIS

**ELECTRO
 DEVICES**

TEL: (415) 964-3136
 INC., BOX 4090, MOUNTAIN VIEW, CA. 94040

NEW FOR **1973**

Portable Radio Phone Model FLIP-2/CBFL, 31.5 MHz, AM. Made by Morrow Radio. Easy to convert. Approx. 1w input pwr/squelch. Mic. included. A1 CONDITION \$14.95
 Headset-Microphone H-63/U 600Ω earphones 100 ohm mike suspended on headband. NEW \$4.95
 Chest Set AN/GSA6 adapts above to GRC-VRC equipment NEW \$2.95



Potter & Brumfield industrial control relay
 New KU-4129-2 SPDT, SPST 115 VAC 60 cps 50¢
 Teletype Ribbons — 35¢ ea., 12 for \$3.50

Sales Sheet now available. Send SASE for copy.
FRANK ELECTRONICS, 407 Ritter Rd., Harrisburg, PA 17109

MINIATURE SUB-AUDIBLE TONE ENCODER

**\$14.95
 Wired-
 Tested**



- Compatible with all sub-audible tone systems such as Private Line, Channel Guard, Quiet Channel, etc.
- Glass Epoxy PCB, silicon transistors, and tantalum electrolytics used throughout
- Any miniature dual coil contactless reed may be used (Motorola TLN6824A, TLN6709-B — Branco RF-20)
- Powered by 12vdc @ 3ma
- Use on any tone frequency 67Hz to 250Hz
- Miniature in size 2.5 x .75 x 1.5" high
- Complete less reed (Available in 33 freqs. for \$17.50 ea)
- Output 3v RMS sinewave, low distortion

Postpaid — Calif. residents add 5% sales tax

COMMUNICATIONS SPECIALISTS

P. O. Box 153, Brea, CA 92621



**Radio Amateurs
 Reference Library
 of Maps and Atlas**

WORLD PREFIX MAP — Full color, 40" x 28", shows prefixes on each country . . . DX zones, time zones, cities, cross referenced tables postpaid **\$1.25**

RADIO AMATEURS GREAT CIRCLE CHART OF THE WORLD — from the center of the United States! Full color, 30" x 25", listing Great Circle bearings in degrees for six major U.S. cities: Boston, Washington, D. C., Miami, Seattle, San Francisco & Los Angeles. postpaid **\$1.25**

RADIO AMATEURS MAP OF NORTH AMERICA! Full color, 30" x 25" — includes Central America and the Caribbean to the equator, showing call areas, zone boundaries, prefixes and time zones, FCC frequency chart, plus informative information on each of the 50 United States and other Countries..... postpaid **\$1.25**

WORLD ATLAS — Only atlas compiled for radio amateurs. Packed with world-wide information — includes 11 maps, in 4 colors with zone boundaries and country prefixes on each map. Also includes a polar projection map of the world plus a map of the Antarctica — a complete set of maps of the world. 20 pages. size 8¾" x 12" postpaid **\$2.50**

Complete reference library of maps — set of 4 as listed above postpaid **\$3.75**

See your favorite dealer or order direct.


**WRITE FOR
 FREE
 BROCHURE!**

RADIO AMATEUR



callbook INC.

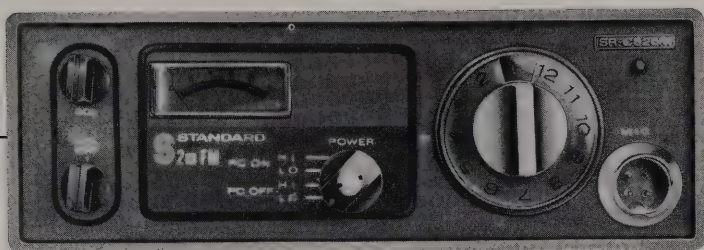Dept. E 925 Sherwood Drive
 Lake Bluff, Ill. 60044



MAXIMIZE YOUR AMATEUR RADIO

What new 2M FM gives **MONEY.** that assures: top selectivity, great sensitivity, performance vs. price? The answer's as clear as the superb reception you'll get on the new Standard 826MA, 10 watt, 2 meter FM transceiver. You'll find such outstanding features as 12 channels — with the four most popular ones included — and a RF output meter with selection of 10 watts or 0.8 watt for battery conservation. And of course, our "Astropoint" system

and rejection of unwanted signals on today's active 2M band. **Helical Resonators** & FET front end provide the performance needed for tomorrows crowded channels. Provision for **tone coded squelch** to activate modern repeaters. A radio that won't become obsolete. Occupies less than 200 cu. in. Weighs less than 5 lbs. It has all the same "Astro-points" as entire Amateur line.

NEW 22 CHANNEL BASE STATION SRC-14U

Ultimate in a 2M FM Transceiver features:

- ☐ 22 channels
- ☐ AC & DC supplies Built In
- ☐ 10W (1, 3 & 10 selectable)
- ☐ Receiver offset tuning
- ☐ VOX
- ☐ Three Front Panel Meters
- ☐ Plus many more exciting features.



For detailed information on these; the complete Standard line and the name of your nearest dealer write:




Standard
Communications Corp.

213 / 775-6284 • 639 North Marine Avenue, Wilmington, California 90744

EPOXY FULL WAVE SILICON BRIDGE RECTIFIERS

PV 2 Amp	6 Amp
100	\$.69
100	\$.79
200	\$.95
400	\$ 1.19
600	\$ 1.35
800	\$ 1.59
1000	\$ 1.79

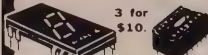Code: 2 amp TO-6 case
6 Amp 1/2 x 1/2 x 3/16 sq



Only **\$3.95**
MAN-4 EQUAL
LED 7-SEGMENT
READOUTS


0-9 plus letters.
Snaps in 14-pin DIP socket. 3/4" x 3/4" x 3/8". 5V 10ma, with decimal point. Like MAN-1.
Socket for above, 50c

6VDC 6AMP/HR MOTORCYCLE BATTERY

• Worth \$10-\$15 Only **\$5.95**

Use as power pak for mobile rigs & many "Ham" components, other electronic projects. Size: 5 1/2" tall x 4 1/2" wide overall x 2 1/2" Shipped dry, must be filled before use.

- Compact
- Needs only Electrolytic

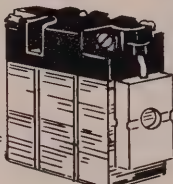

'HAM' UHF 400 MC HIGH POWER TRANSISTORS

Only **\$3.95**
3 for \$10.

By RCA or equal 2N3632, NPN, 23 watts, 3 amps, TO-6 case, with stud mtg. VCEV max 65.



PLASTICRTL'S By Fairchild

Choose Any
2 for \$1.00
900 Buffer
914 Quad 2 Input Gate
923 J-K Flip Flop



Spring Clearance Sale

12-DIGIT "CALCULATOR ON A CHIP"

Similar to Mostek 5001. Outperforms Texas 8-digit TMS1802. A 40-pin DIP. Adds, multiplies, subtracts, and divides. Use with 7-segment readouts, Nixies, and LED's. We include schematics, instructions to build calculator.

Only **\$12.95**
3 for \$35




INTEGRATED CIRCUIT SOCKETS

Buy Any 3 - Take 10% Discount!

- 14-Pin, dual in line . . . \$.45
- 16-Pin, dual in line . . . \$.50
- TO-5, 8 or 10 pins . . . \$.29

WIRE-WRAP INTEGRATED CIRCUIT SOCKETS

79c ea
3 for \$2.00

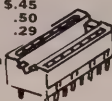

12VDC POWER PAC

110 VAC to 12 VDC @ 1.6 Amp
5 x 2 1/2 x 3 1/4"

\$3.33

LINEAR Op Amps

8 FACTORY GUARANTEES

FACTORY MARKED

Buy Any 3 PAKS - Take 10% Discount

531	Hi slew rate op-amp (TO-5)	\$2.50
532	Micro power 741 (TO-5)	2.50
533	Micro power 709 (TO-5)	2.50
536	FET input op-amp (TO-5)	3.95
537	Precision 741 (TO-5)	2.50
540	70W pwr driver amp (TO-5)	2.04
550	Precision 723 voltage reg. (DIP)	1.17
555	Timer 2 uSeconds to 1-hr (A)	1.00
556	5 Times faster than 741C	1.00
558	Dual 741 (mini DIP)	.88
560	Phase lock loops (DIP)	3.25
561	Phase lock loops (DIP)	3.25
562	Phase lock loops (DIP)	3.25
565	Phase lock loops (A)	3.25
566	Function generator (A)	3.25
567	Tone generator (A)	3.25
595	Four quadrant multiplier	3.10
702C	Hi-grain, DC amp (TO-5)	.44
703C	RF-IF, amp, 14 ckt (TO-5)	.69
709C	Operational amp (A)	.95
709CV	Op amp (mini DIP)	.49
710C	Differential amp (A)	.39
711C	Dual diff. comp (A)	.39
723C	Voltage regulator (A)	.69
741C	Frequency compensator 709 (A)	.49
741CV	Freq. comp 709 (Mini DIP)	.49
747C	Dual 741C (A)	1.25
748C	Freq. adj. 741C (A)	.44
748CV	Freq. adj. 741C (mini DIP)	.44
709-709	Dual 709C (DIP)	1.00
739-739	Dual stereo preamp	1.98
741-741	Dual 741C (A)	1.00
75450	Dual peripheral driver (DIP)	.69

(A) TO-5 or DIP dual in line pak

Largest Selection TTL IC's

Brand New "DIP" Packages Order by type number! Spec sheets on request "ONLY"

Type	Price	Type	Price	Type	Price	Type	Price
SN7400	.25	SN7437	.50	SN7476	.44	SN74151	1.13
SN7401	.25	SN7438	.51	SN7480	.65	SN74153	1.49
SN7402	.25	SN7440	.25	SN7481	1.10	SN74154	2.19
SN7403	.25	SN7441	1.30	SN7482	.88	SN74155	1.39
SN7404	.28	SN7442	1.21	SN7483	1.25	SN74156	1.39
SN7405	.27	SN7443	1.21	SN7486	.49	SN74157	1.25
SN7406	.45	SN7444	1.21	SN7489	3.50	SN74158	1.48
SN7407	.45	SN7445	1.50	SN7490	1.00	SN74159	1.48
SN7408	.29	SN7446	1.50	SN7491	1.25	SN74160	1.79
SN7409	.29	SN7447	1.50	SN7492	.75	SN74161	1.79
SN7410	.29	SN7448	1.25	SN7493	.75	SN74162	1.79
SN7411	.25	SN7449	.25	SN7494	1.10	SN74163	1.79
SN7413	.95	SN7451	.25	SN7495	.95	SN74165	3.50
SN7416	.48	SN7452	.25	SN7496	1.10	SN74180	1.10
SN7417	.48	SN7453	.25	SN74100	1.41	SN74181	4.50
SN7420	.25	SN7454	.25	SN74101	.49	SN74182	1.10
SN7421	.25	SN7455	.25	SN74107	.49	SN74184	2.50
SN7426	.32	SN7460	.21	SN74121	.49	SN74185	2.50
SN7427	.32	SN7470	.39	SN74122	.65	SN74192	1.75
SN7430	.25	SN7472	.36	SN74123	.99	SN74193	1.75
SN7432	.25	SN7473	.44	SN74141	1.45	SN74195	1.19
		SN7474	.39	SN74145	1.25	SN74198	2.65
		SN7475	1.00	SN74150	1.25	SN74199	2.65

Buy 3 or more, 10% discount



LED READOUTS

0-9 plus letters, for SN7446 or SN7447. Snaps in 14-pin DIP socket. 3/4 x 3/4 x 3/8". characters: 1/4 x 1/4". 5V, 20-mils per seg. characters: 3/4 x 3/16". Famous MAN-1 type.
Sockets .50 ea.

4.50
3 for \$12.

\$2.95
Buy 10% Take 10%

This display is excellent for small portable electronics, such as DVM's, calculators, etc. Equivalent to Monsanto MAN 3A. Operates from 5V, 20 milliamperes, with 47 ohm dropping resistor.



COUNTING SYSTEM

Includes SN7490, decade counter, SN7475 latch, SN741 BCD decoder driver, 0-9-Nixie tube, instructions.

\$4.50
3 for \$12.00



HOT MOS FETS

- 2-MOS FETS, N channel 10k u mos 3N128, TO-18, RCA \$1
- 2-MOS FETS, DUAL GATE, N chan., 3N141-1, TO-18, \$1
- 2-MOS FETS, DUAL GATE, N chan., 3N140-1, TO-18, \$1

LED-PHOTO-SOLAR "DOLLAR STRETCHERS"

- 3 - "LEDS", visible, micro-miniature, axial leads . . . \$1
- 2 - "LEDS", infrared, jumbo, TO-18 . . . \$1
- 3 - "LEDS", visible, jumbo, TO-18 . . . \$1
- 1 - "LED", invisible, parabolic reflector, RCA . . . \$1
- 2 - PHOTO TRANSISTOR, with darlington amp filter, 10u \$1
- 2 - PHOTO TRANSISTORS, with darlington amp, 2N577 \$1
- 4 - PHOTO CELLS, Clairex, pancake, 30K-70 ohms . . . \$1
- 2 - SILICON SENSORS, TEXAS, H-38 Matchstick, visible \$1

NATIONAL \$2.25 VOLTAGE REGULATOR

LM-309K 5 volts, 1 amp TO-3 case. Internally set. Overload and short circuit proof. No external components. With spec sheets. **3 for \$6.00**



Terms: add postage, cod's 25%. Rated: net 30. Phone Orders: Wakefield, Mass. (617) 245-3K29. Retail: 16-18 Del Carmine St., Wakefield, Mass. (off Water Street) C.O.D.'S MAY BE PHONED

15c CATALOG on Fiber Optics, 'IC's, Semi's, Parts

POLY PAKS

P.O. BOX 942H, LYNNFIELD, MASS. 01940



"DIGITAL CLOCK ON A CHIP"

Only **\$14.95**



NEW

Buy 3 Take 10%

SD-5314 direct substitute to famous U.S. maker. 24-Pin DIP - IMAGINE! ONE CHIP ELIMINATING 15 IC & other parts. Space Saver! Money saver! Latest in clock design. Features 12 or 24-hr. operation, 1 or 6 digits, 10 or 60 Hz operation. Internal digit multiplex oscillator, leading zero blanking, high output current for simple readout interface. Single power supply operation. Digit blanking for reduced current drain. 1 thru 19 volt range. Full MOS LSI. Spec sheets included.

flea market



■ **RATES** Commercial Ads 25¢ per word; non-commercial ads 10¢ per word payable in advance. No cash discounts or agency commissions allowed.

■ **COPY** No special layout or arrangements available. Material should be typewritten or clearly printed and must include full name and address. We reserve the right to reject unsuitable copy. **Ham Radio** can not check out each advertiser and thus cannot be held responsible for claims made. Liability for correctness of material limited to corrected ad in next available issue. Deadline is 15th of second preceding month.

■ **SEND MATERIAL TO:** Flea Market, Ham Radio, Greenville, N. H. 03048.

SIGNAL ONE OWNERS, expert and prompt service by ex-Signal/One employee. Write or call for details. Larry Pace, K2IXP/7, 1071 W. Roller Coaster, Tucson, AZ. 85704 (602-888-5234)

VERY inter-est-ing! Next 6 big issues \$1. "The Ham Trader," Sycamore IL 60178

MOULTRIE AMATEUR RADIO KLUB, 12th Annual Hamfest, Wyman Park, Sullivan, Illinois, April 29, 1973, Indoor-outdoor market. Ticket donation \$1.00 in advance — \$1.50 at the gate. For information write M.A.R.K. Inc., P. O. Box 327, Mattoon, Illinois 61938.

NEW SCANNER BOOK from Sams, includes comprehensive servicing data for 30 popular UHF and VHF Scanner-Monitor receivers including models by B & K, Browning, Johnson, Midland, Pace, Pearce-Simpson, Penney's, Realistic, Sonar and Teubury. Just \$4.95 postpaid from Comtec, Greenville, N. H. 03048.

ROCHESTER, N. Y. is the place to go for the largest Hamfest, VHF meet and flea market in the northeast, May 12th. Write WNY Hamfest, Box 1388, Rochester, N. Y. 14603.

FOR YOUR FUTURE ROBYN RADIOS send your order to, Two Way Radio Sales, 1501 Monroe Street, Bogalusa, La. 70427 or 202 Farrell Street, Picayune, Miss. 39466.

WANTED: tubes, transistors, equipment what have you? Bernard Goldstein, W2MNP, Box 257, Canal Station, New York, N. Y. 10013.

YAESU FL 2100 LINEAR, brand new, \$290.00 plus shipping. K56EQ, Courthouse, Pago Pago, American Samoa, 96799.

SWAP OR SELL CV-591A/URR SSB RECEIVING CONVERTERS — Complete, unchecked with manuals. Clem - K8HWW, 33727 Brownlea, Sterling Heights, Mich. 48077. 1-313-268-2467.

22nd ANNUAL DAYTON HAMVENTION will be held on April 28, 1973 at Wampler's Dayton Hara Arena. Technical sessions, exhibits, hidden transmitter hunt, flea market, and special program for the XYL. For info write Dayton Hamvention, Dept. H, Box 44, Dayton, Ohio 45401.

WORLD QSL — See ad page 96.

BARGAIN HUNTERS! Don't miss out. Closeout of 18th Edition of W6SAI's Radio Handbook, list \$13.50, only \$7.95 ppd. while they last. Comtec, Greenville, N. H. 03048.

COMPUTER . . . Want Heathkit analog computer. R. J. Schlesinger, K6LZM, 5108 Melvin Ave., Tazana, Calif. 91356. (213) 342-4376.

CANADA NOW HAS A NATIONAL QSL BUREAU: If your bureau sends QSL cards to Canada we invite you to use the service of this bureau. We will help you here by sorting the cards into the different Provinces. There are ten provincial bureaus in Canada. You may send Canadian cards in bulk to this address. We will promptly sort them here and distribute to the ten provincial bureaus. There is no cost to anyone for this service. The Canadian Amateur Federation Inc. is glad to make this new national bureau available to any QSL bureau in the world for cards coming into Canada. We hope it will help you in handling cards for this country.

RID-O-RAY, America's best known electric bug killer. Safe, dependable design provides years of trouble free performance. S-15 for 1/4 acre \$89.95. Model D-15 for 3/4 acre \$109.95. Shipping paid East of Mississippi. West add \$5.00. 10% discount thru April 30th. Comtec, 140 Main St., Greenville, N. H. 03048.

MOBILE IGNITION SHIELDING provides more range with no noise. Available most engines in assembled or kit forms, plus many other suppression accessories. Free literature. Estes Engineering, 543-H West 184th, Gardena, California 90248.

TUBES save \$\$\$\$\$\$ send RFQ: Tubes International, Wainright, Ak. 99782.

TOROIDS, iron "E" powder 80-10 meters. .500" — 8/\$1.00, .940" — 4/\$1.00, 1.437" — 75¢ each or 3/\$2.00, 2.310" — \$1.50 or 3/\$4.00. Please include 50¢ postage, slightly more on large orders. Fred Barken, WA2BLE, 274 E. Mt. Pleasant Ave., Livingston, N. J. 07039.

SELLING OUT. Send address for list. Cline WA7TMR, Box 216, Logan, Utah 84321.

HOOSIER ELECTRONICS has the best deal around on the ham gear you want. Write us for a quote and try our fast, friendly Hoosier service. Factory-authorized dealers for Regency, Drake, Standard, Ten-Tec, Galaxy, Hy-Gain, Cush-Craft, Hustler, Mosley, Ham-M, Bowmar Pocket Calculators, plus many more. Orders for in-stock merchandise shipped the same day. Write or call us today for our quote and become one of the many happy satisfied customers of Hoosier Electronics, R. R. 25, Box 403, Terre Haute, Indiana 47802. (812) 894-2397.

QSL'S. Second to none. Same day service. Samples 25¢. Ray, K7HLR, Box 331, Clearfield, Utah 84015.

WANT OLD RADIO SHOW TRANSCRIPTION discs. Any size or speed. Send details to, Larry Kiner, W7FIZ, 7554 132nd Ave. N.E., Kirkland, Wa. 98033.


ANTIQUE Western Electric speaker (ca 1925), needs cone, sent free to first person who sends postage for 5 pounds, parcel post. Jim Fisk, Greenville, NH 03048.

MANUALS for most ham gear made 45/65, some earlier. Send SASE for copy quote. Hobby Industry, WOJJK, Box 864, Council Bluffs, Iowa 51501.

SELL: Polytechnic Research Development — Precision Frequency Meter — Navy type 560-cavity tuned 2400-3400 MC./S. A gem instrument. Make offer. W9CO, 604 Wyatt, Lincoln, Illinois 62656.

NEED 4D32 for 32V2 rig, or circuit diagram for 6146A/B or other, will pay. Jerry, WA7RYS, Box 389, Christmas, Ariz. 85292.

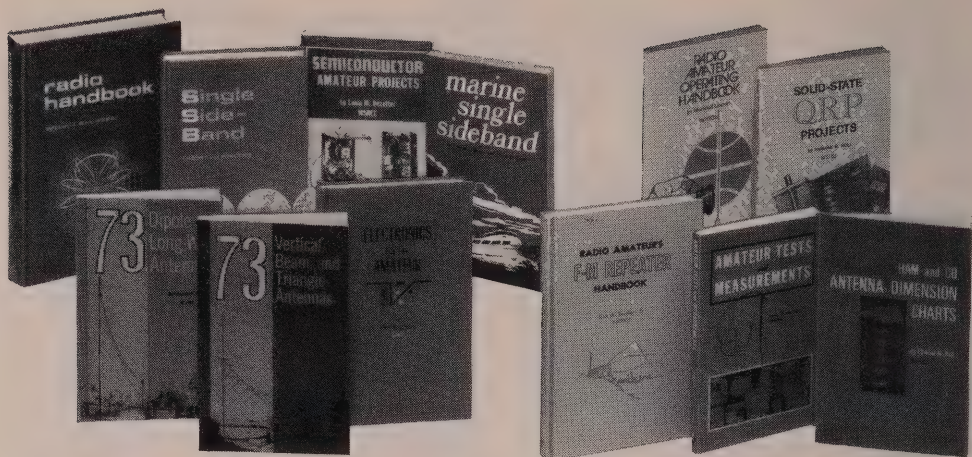TELL YOUR FRIENDS about Ham Radio Magazine.



Problem-solving handbooks

Highly popular Editors and Engineers books from Sams give amateurs everything they need to know about radio operation and technology. They're authoritative, clear, and easy to follow. You'll want them for your library.

Famous E&E RADIO HANDBOOK—19th Edition By William I. Orr, W6SAI

The completely updated electronics industry standard for engineers, technicians, and advanced amateurs. Shows how to design and build all types of radio-communications equipment. Includes ssb design and equipment, RTTY circuits, latest semiconductor circuits, IC's, and special circuitry. **No. 24030—\$14.95**

SINGLE SIDEBAND: THEORY & PRACTICE By Harry D. Hooton, W6TYH

A basic text covering the origin of ssb, derivation of signals, sideband selection, ssb generators, carrier-suppression techniques, carrier generators, speech amplifiers and filters, balanced mixers and converters, low-power ssb transmitters, linear r-f power amplifiers, and much more. **No. 24014—\$6.95**

SEMICONDUCTOR AMATEUR PROJECTS By Louis M. Dezettel, W5REZ

For the ham who still takes pride in using his hands and head, here are projects for 16 useful, money-saving accessories, using easy-to-build semiconductor circuitry. Units are for measuring equipment, increasing power and adding convenience, etc. **No. 24025—\$4.95**

MARINE SINGLE SIDEBAND

By Donald M. Stoner and Pierre B. Goral

Covers the why and how of single sideband; interpreting specifications, alignment tests and measurements, installations, securing a limited coastal license, high-seas telephone service, and marine radio terminology. **No. 24029—\$5.95**

RADIO AMATEUR OPERATING HANDBOOK By Marshall Lincoln, W7DQS

This single-source working guide is a practical aid for improving the operating methods and techniques of hams. **No. 24028—\$4.95**

SOLID-STATE QRP PROJECTS By Edward M. Noll, W3FQJ

By building QRP equipment you learn solid-state technology, since these rigs include transistors and/or integrated circuits. The low-cost units described have power ratings from less than 100 milliwatts up to about 20 watts. Both cw and phone rigs are included. **No. 24024—\$4.25**

73 DIPOLE AND LONG-WIRE ANTENNAS

By Edward M. Noll, W3FQJ

Detailed construction data for 73 different types of wire antennas. Appendices describe construction of noise bridges and line tuners, plus data on measuring resonant frequency, velocity factor, and SWR. **No. 24006—\$4.50**

73 VERTICAL, BEAM, AND TRIANGLE ANTENNAS By Edward M. Noll, W3FQJ

Design and construction of 73 different antennas used by amateurs, each built and air-tested by the author. Also construction of noise bridges, transmission-line tuners, and measurement methods. **No. 24021—\$4.95**

ELECTRONICS FOR THE AMATEUR By Louis M. Dezettel, W5REZ

Covers radio-wave propagation as it applies to amateur band frequencies, reception and transmission pertaining to ham equipment, and the special field of antennas and how to feed them. Provides you with everything needed to pass the theory sections of the FCC exams. **No. 24022—\$7.95**

RADIO AMATEUR'S F-M REPEATER HANDBOOK By Ken W. Sessions, Jr., K6MVB

The definitive work on amateur f-m repeaters. Includes: Preparing and obtaining sites for repeaters; How to build a repeater; Repeater applications; and an f-m repeater directory. **No. 24006—\$6.95**

AMATEUR TESTS AND MEASUREMENTS By Louis M. Dezettel, W5REZ

Shows how to accomplish virtually all performance tests on amateur transmitters, receivers, and antennas, and how to make required adjustments. **No. 24007—\$5.50**

HAM AND CB ANTENNA DIMENSION CHARTS By Edward M. Noll, W3FQJ

Tabulates dimension data in feet and inches for all popular antenna configurations. With this data, an antenna can be dimensioned for a specific frequency range according to license class and mode of operation. **No. 24023—\$1.95**

Order from your electronic parts distributor or send coupon below.



EDITORS AND ENGINEERS

Howard W. Sams & Co., Inc. HR043
4300 W. 62nd St., Indianapolis, Ind. 46268

Send me the following books. Nos. _____

_____ \$ _____ enc

Please include sales tax where applicable

☐ Send FREE 1973 Sams Book Catalog

Name _____

PLEASE PRINT

Address _____

City _____ State _____ Zip _____

WE BUY ELECTRON TUBES, diodes, transistors, integrated circuits, Semiconductors, Astral Electronics, 150 Miller Street, Elizabeth, New Jersey 07207, (201) 354-2420.

TELETYPE, Kleinschmidt, mite, machines, parts, ribbons, motors, gears, manuals. Buy late machines, all unused parts. Wanted: Teletype manuals, SASE for list. Typetronics, Box 8873, Ft. Lauderdale, Fla. 33310.

VALUABLE COLLECTION: Your back issues of Ham Radio are an important technical reference source. Protect them with binders (\$4.50 each, 3 for \$12.00 ppd.) and find the articles you want with our special Cumulative Index only \$1.00 ppd. Ham Radio, Greenville, N. H. 03048.

WASTMR DECEASED. Wife must sell Swan 500CX single sideband transceiver and power supply 117XC. Excellent condition. Mrs. John Sercia, Box 144, Brookfield, Ohio 44403.

REPAIR TV TUNERS — High earnings, complete course details, 12 repair tricks, many plans, two lessons, all for \$1. Refundable. Frank Bocek, Box 3236 (Enterprise Branch), Redding, Ca. 96001.

WANTED — Collins KWM2A. Must be 2A only. Price to Cal Moss, KL7HEM, P. O. Box 2191, Fairbanks, Alaska 99707.

LINEAR BUILDERS — Model DS-12 2.5A/12,000 PIV diode rectifier, replaces 866, 3B28, and 872. R-C suppressors, \$9.95. At your dealer or order direct ppd. HEP-170 2.5A/1000 PIV diodes 30¢ each, direct only. K. E. Electronics, Box 1279, Tustin, California 92680. Send SASE for information on plate chokes, filament chokes, and p-networks.

GREATER BALTIMORE HAMBOREE will be held Sunday, April 8, 1973, at 10 a.m. at Calvert Hall College, Putty Hill and Goucher Boulevard, Towson, Maryland (1 mile south of Exit 28 Beltway - Interstate 695), food service, flea market, prizes, registration \$2.00. No table charge or percentage. Info: Joe Lochte, 5400 Roland Avenue, Baltimore, Maryland 21210.

HALLICRAFTERS SR-150 & PS-150, \$275; Gonset 3212 2 meter power amplifier, \$125; PolyComm 62-B, \$100; all in good condition with manuals. W2WRI, J. A. Kammerer, 23 New Street, Katonah, N. Y. 10536 (914-232-8349).

HAMFEST — Wabash County ARC Fifth Annual Hamfest, Sunday May 20, rain or shine. Admission is still only \$1. Flea market, food, tech talks and much more. For information write Bob Mitting, 663 Spring, Wabash, In. 46992.

MODERNIZE FOR PEANUTS! Frame & Display QSL's with 20 pocket plastic holders. Two for \$1.00, seven for \$3.00. Prepaid, guaranteed. Universally used and approved. Order now. TEPABCO, Box 198H, Gallatin, Tennessee 37066.

PRINTED CIRCUIT DRILL BITS. Trumbull, 833 Balra Drive, El Cerrito, California 94530.

FOR SALE: SB-401 with xtal pack, condition good. 75A1 by Collins. Full 1 MHz coverage on each band, 80-10, condition good, \$150.00 for each, \$300.00 for both. Virgil L. Jiles, Jr., 4606 Tumbleweed, El Paso, Texas 79924.

THE SPRING AUCTION of the Rockaway Amateur Radio Club will be held Friday evening, April 27th at the Hall of Science, Worlds Fair Grounds, Flushing, N. Y. Doors will be open at 6:00 p.m. to accept items for the sale. The auction is scheduled to begin at 8:00 p.m. A one dollar donation will be accepted at the door. For further information contact: Al Smith, WA2TAQ, P. O. Box 341, Lynbrook, N. Y. 11563.

2 MTR FM CHEAP? Will convert your 2 mtr Gonset III for 2 mtr FM - \$35.00 plus shipping. Jim Gysan, W1VVB (617) 922-3850.

TEKTRONIC 545A mainframe; B, CA, S plugins, manuals, \$1100. Heathkit Q meter, \$50; IO-10 DC XY scope, \$60. Lafayette CR Analyzer, \$25. Sears #2140N lathe & accessories, \$225. All like new condition. Jim Ashe, P. O. Box 6, Cambridge, Mass. 02138. (617) 926-4189.

FM RINGO

3.75 db GAIN

AR-2 - \$12.50

**WORLD'S BEST VHF
FM ANTENNA, IN
STOCK AT YOUR LOCAL
DISTRIBUTOR.**



**Cush
Craft
CORPORATION**

**621 HAYWARD STREET
MANCHESTER, N.H. 03103**

WANTS TO BUY

All types of military electronics equipment and parts. Call collect for cash offer.

**SPACE ELECTRONICS division of
MILITARY ELECTRONICS CORP.**

76 Brookside Drive, Upper Saddle River
New Jersey 07458 • (201) 327-7640

THE RECIPROCATING DETECTOR

As a Kit \$36.....Wired \$45

State your IF Frequency

PETER MEACHAM ASSOCIATES

19 Loretta Road, Waltham, Mass. 02154

F.C.C. EXAM MANUAL

PASS FCC EXAMS! Memorize, study — "1973 Tests-Answers" for FCC First and Second class Radio-telephone licenses. Newly revised multiple-choice questions and diagrams cover all areas tested in FCC exams. — plus "Self-Study Ability Test." \$9.95 Postpaid.



**COMMAND PRODUCTIONS
RADIO ENGINEERING DIVISION** P.O. BOX 26348-K
SAN FRANCISCO, CALIF. 94126



READOUTS \$3.00

7-SEGMENT 5 VDC

Long life incandescent tube 1/2 inch high character. Drive with 7447 IC. Write for complete list including polarizing filters, complete counter modules, many more items.

Display Electronics P.O. BOX 1044
LITTLETON, CO 80120

Catalog Number	Inv. Quantity Per Item (Mix)				Multiples of 10 Per Item (Mix)				Catalog Number	Inv. Quantity Per Item (Mix)				Multiples of 10 Per Item (Mix)				
	1-	100-	1000	1000	1-	100-	1000	1000		1-	100-	1000	1000	1-	100-	1000	1000	
7400	.26	.25	.23	.22	74176	1.62	1.53	1.45	1.36	74800	.88	.84	.79	74810	.88	.84	.79	
7401	.26	.25	.23	.22	74177	1.62	1.53	1.45	1.36	74801	.88	.84	.79	74811	.88	.84	.79	
7402	.26	.25	.23	.22	74180	1.20	1.13	1.07	1.01	74803	.88	.84	.79	74813	.88	.84	.79	
7403	.26	.25	.23	.22	74181	5.20	4.90	4.59	4.28	74804	1.00	.95	.90	74814	1.00	.95	.90	
7404	.28	.27	.25	.24	74182	1.20	1.13	1.07	1.01	74805	1.00	.95	.90	74815	.88	.84	.79	
7405	.28	.27	.25	.24	74192	1.98	1.87	1.76	1.65	74808	.88	.84	.79	74818	.88	.84	.79	
7406	.52	.50	.47	.44	74193	1.98	1.87	1.76	1.65	74810	.88	.84	.79	74819	.88	.84	.79	
7407	.52	.50	.47	.44	74198	2.81	2.65	2.50	2.34	74815	.88	.84	.79	74820	.88	.84	.79	
7408	.32	.30	.29	.27	74199	2.81	2.65	2.50	2.34	74821	.88	.84	.79	74822	.88	.84	.79	
7409	.32	.30	.29	.27						74840	1.00	.95	.90	74841	1.00	.95	.90	
7410	.26	.25	.23	.22	SCHOTTKY TTL													
7411	.28	.27	.25	.24	74800	.88	.84	.79	.75	74851	.88	.84	.79	.75	74852	.88	.84	.79
7413	.58	.55	.52	.49	74801	.88	.84	.79	.75	74853	.88	.84	.79	.75	74854	.88	.84	.79
7416	.52	.50	.47	.44	74803	.88	.84	.79	.75	74855	.88	.84	.79	.75	74856	.88	.84	.79
7417	.52	.50	.47	.44	74804	1.00	.95	.90	.85	74857	1.82	1.73	1.63	1.54	74858	1.82	1.73	1.63
7418	.26	.25	.23	.22	74805	1.00	.95	.90	.85	74874	1.82	1.73	1.63	1.54	74875	1.82	1.73	1.63
7420	.26	.25	.23	.22	74808	.88	.84	.79	.75	74810	.88	.84	.79	.75	74811	.88	.84	.79
7421	.26	.25	.23	.22	74810	.88	.84	.79	.75	74811	.88	.84	.79	.75	74812	.88	.84	.79
7423	.80	.76	.72	.68	74815	.88	.84	.79	.75	74813	.88	.84	.79	.75	74814	.88	.84	.79
7425	.50	.48	.45	.43	74820	.88	.84	.79	.75	74818	.88	.84	.79	.75	74819	.88	.84	.79
7426	.34	.32	.31	.29	74821	.88	.84	.79	.75	74822	.88	.84	.79	.75	74823	.88	.84	.79
7430	.26	.25	.23	.22	74822	.88	.84	.79	.75	74840	1.00	.95	.90	.85	74841	1.00	.95	.90
7437	.56	.53	.50	.48	74823	.88	.84	.79	.75	74851	.88	.84	.79	.75	74852	.88	.84	.79
7438	.56	.53	.50	.48	74840	1.00	.95	.90	.85	74853	.88	.84	.79	.75	74854	.88	.84	.79
7440	.26	.25	.23	.22	74850	.88	.84	.79	.75	74855	.88	.84	.79	.75	74856	.88	.84	.79
7441	1.73	1.64	1.55	1.46	74851	.88	.84	.79	.75	74857	1.82	1.73	1.63	1.54	74858	1.82	1.73	1.63
7442	1.27	1.21	1.14	1.07	74860	.88	.84	.79	.75	74874	1.82	1.73	1.63	1.54	74875	1.82	1.73	1.63
7443	1.27	1.21	1.14	1.07	74860	.88	.84	.79	.75	74810	.88	.84	.79	.75	74811	.88	.84	.79
7444	1.27	1.21	1.14	1.07	74865	.88	.84	.79	.75	74813	.88	.84	.79	.75	74814	.88	.84	.79
7445	1.71	1.62	1.53	1.44	74873	1.82	1.73	1.63	1.54	74818	.88	.84	.79	.75	74819	.88	.84	.79
7446	1.24	1.17	1.11	1.04	74874	1.82	1.73	1.63	1.54	74820	.88	.84	.79	.75	74821	.88	.84	.79
7447	1.16	1.10	1.04	.98	74810	.88	.84	.79	.75	74822	.88	.84	.79	.75	74823	.88	.84	.79
7448	1.44	1.37	1.29	1.22	74811	.88	.84	.79	.75	74840	1.00	.95	.90	.85	74841	1.00	.95	.90
7450	.26	.25	.23	.22	74812	.88	.84	.79	.75	74851	.88	.84	.79	.75	74852	.88	.84	.79
7451	.26	.25	.23	.22	74813	.88	.84	.79	.75	74853	.88	.84	.79	.75	74854	.88	.84	.79
7453	.26	.25	.23	.22	74814	.88	.84	.79	.75	74855	.88	.84	.79	.75	74856	.88	.84	.79
7454	.26	.25	.23	.22	74815	.88	.84	.79	.75	74857	1.82	1.73	1.63	1.54	74858	1.82	1.73	1.63
7459	.26	.25	.23	.22	74818	.88	.84	.79	.75	74874	1.82	1.73	1.63	1.54	74875	1.82	1.73	1.63
7460	.26	.25	.23	.22	74819	.88	.84	.79	.75	74810	.88	.84	.79	.75	74811	.88	.84	.79
7470	.42	.40	.38	.36	74820	.88	.84	.79	.75	74813	.88	.84	.79	.75	74814	.88	.84	.79
7472	.38	.36	.34	.32	74821	.88	.84	.79	.75	74818	.88	.84	.79	.75	74819	.88	.84	.79
7473	.50	.48	.45	.43	74822	.88	.84	.79	.75	74820	.88	.84	.79	.75	74821	.88	.84	.79
7474	.50	.48	.45	.43	74823	.88	.84	.79	.75	74822	.88	.84	.79	.75	74823	.88	.84	.79
7475	.80	.76	.72	.68	74840	1.00	.95	.90	.85	74841	1.00	.95	.90	.85	74842	1.00	.95	.90
7476	.56	.53	.50	.48	74850	.88	.84	.79	.75	74851	.88	.84	.79	.75	74852	.88	.84	.79
7480	.76	.72	.68	.65	74853	.88	.84	.79	.75	74853	.88	.84	.79	.75	74854	.88	.84	.79
7482	.99	.94	.88	.83	74855	.88	.84	.79	.75	74855	.88	.84	.79	.75	74856	.88	.84	.79
7483	1.63	1.55	1.46	1.38	74857	1.82	1.73	1.63	1.54	74857	1.82	1.73	1.63	1.54	74858	1.82	1.73	1.63
7485	1.43	1.35	1.28	1.20	74858	1.82	1.73	1.63	1.54	74858	1.82	1.73	1.63	1.54	74859	1.82	1.73	1.63
7486	.58	.55	.52	.49	74859	1.82	1.73	1.63	1.54	74859	1.82	1.73	1.63	1.54	74860	1.82	1.73	1.63
7490	.80	.76	.72	.68	74860	1.82	1.73	1.63	1.54	74860	1.82	1.73	1.63	1.54	74861	1.82	1.73	1.63
7491	1.43	1.35	1.28	1.20	74861	1.82	1.73	1.63	1.54	74861	1.82	1.73	1.63	1.54	74862	1.82	1.73	1.63
7492	.80	.76	.72	.68	74862	1.82	1.73	1.63	1.54	74862	1.82	1.73	1.63	1.54	74863	1.82	1.73	1.63
7493	.80	.76	.72	.68	74863	1.82	1.73	1.63	1.54	74863	1.82	1.73	1.63	1.54	74864	1.82	1.73	1.63
7494	1.18	1.12	1.05	.99	74864	1.82	1.73	1.63	1.54	74864	1.82	1.73	1.63	1.54	74865	1.82	1.73	1.63
7495	1.18	1.12	1.05	.99	74865	1.82	1.73	1.63	1.54	74865	1.82	1.73	1.63	1.54	74866	1.82	1.73	1.63
7496	1.18	1.12	1.05	.99	74866	1.82	1.73	1.63	1.54	74866	1.82	1.73	1.63	1.54	74867	1.82	1.73	1.63
74100	1.52	1.44	1.36	1.28	74867	1.82	1.73	1.63	1.54	74867	1.82	1.73	1.63	1.54	74868	1.82	1.73	1.63
74107	.52	.49	.47	.44	74868	1.82	1.73	1.63	1.54	74868	1.82	1.73	1.63	1.54	74869	1.82	1.73	1.63
74121	.56	.53	.50	.48	74869	1.82	1.73	1.63	1.54	74869	1.82	1.73	1.63	1.54	74870	1.82	1.73	1.63
74122	.70	.67	.63	.60	74870	1.82	1.73	1.63	1.54	74870	1.82	1.73	1.63	1.54	74871	1.82	1.73	1.63
74123	1.21	1.06	1.00	.94	74871	1.82	1.73	1.63	1.54	74871	1.82	1.73	1.63	1.54	74872	1.82	1.73	1.63
74141	1.63	1.55	1.46	1.38	74872	1.82	1.73	1.63	1.54	74872	1.82	1.73	1.63	1.54	74873	1.82	1.73	1.63
74145	1.63	1.55	1.46	1.38	74873	1.82	1.73	1.63	1.54	74873	1.82	1.73	1.63	1.54	74874	1.82	1.73	1.63
74150	1.63	1.55	1.46	1.38	74874	1.82	1.73	1.63	1.54	74874	1.82	1.73	1.63	1.54	74875	1.82	1.73	1.63
74151	1.20	1.13	1.07	1.01	74875	1.82	1.73	1.63	1.54	74875	1.82	1.73	1.63	1.54	74876	1.82	1.73	1.63
74153	1.63	1.55	1.46	1.38	74876	1.82	1.73	1.63	1.54	74876	1.82	1.73	1.63	1.54	74877	1.82	1.73	1.63
74154	2.43	2.30	2.16	2.03	74877	1.82	1.73	1.63	1.54	74877	1.82	1.73	1.63	1.54	74878	1.82	1.73	1.63
74155	1.46	1.39	1.31	1.23	74878	1.82	1.73	1.63	1.54	74878	1.82	1.73	1.63	1.54	74879	1.82	1.73	1.63
74156	1.46	1.39	1.31	1.23	74879	1.82	1.73	1.63	1.54	74879	1.82	1.73	1.63	1.54	74880	1.82	1.73	1.63
74157	1.56	1.48	1.39	1.31	74880	1.82	1.73	1.63	1.54	74880	1.82	1.73	1.63	1.54	74881	1.82	1.73	1.63
74158	1.56	1.48	1.39	1.31	74881	1.82	1.73	1.63	1.54	74881	1.82	1.73	1.63	1.54	74882	1.82	1.73	1.63
74160	1.89	1.79	1.68	1.58	74882	1.82	1.73	1.63	1.54	74882	1.82	1.73	1.63	1.54	74883	1.82	1.73	1.63
74162	1.89	1.79	1.68	1.58	74883	1.82	1.73	1.63	1.54	74883	1							

ROCKET CITY REMAILING 25¢ each. Receiving, forwarding. Brochure. Gem, 4624H Doughty, Huntsville, Alabama 35805.

FOR SALE: By WA1EPK. Hallicrafter SX-122, mint, \$185.00. Hammarlund HQ-150, \$125.00. Lettine radio model 242, 6 meter TX, \$50.00. SRR-13 receiver, \$150.00. Box of crystals, \$10.00. Call (617) 391-4230 after 7 p.m. nites. Dwight Perkins, 559 Fulton St., Medford, Mass. 02155.

BUY your Howard Sams Books from us. Free catalog on request. Discounts on orders over \$15.00. Comtec, Greenville, N. H. 03048.

FIGHT TVI with the RSO Low Pass Filter — p115 March 73 — write for brochure — Taylor Communications Manufacturing Company, Box 126, Agincourt, Ontario, Canada.

WANTED: Lafayette HA46, Bob, K6GEV, 11 Wool, San Francisco 94110.

TELETYPEWRITERS — Kleinschmidt — portable, fixed, sets, punches, parts, reconditioned, reasonable. Mark/Space Systems, 3563 Conquista, Long Beach, Calif. 90808. 213-429-5821.

CANADA'S MOST UNUSUAL Surplus and Parts Catalog. Jam packed with bargains and unusual items. Send \$1. ETCO-HR, Box 741, Montreal, Canada.

HIGH POWER PARTS. Vacuum variable, plate and fil. transformers, choke, filter caps. Envelope for full information. Earl Eggers, 2105 West 29th, Eugene, Oregon 97405.

TECH MANUALS for govt. surplus gear, only \$6.50 each: TS-497A/URR, TS-34A/AP, R-389/URR, R-220/URR, R-274/FRR, R-390/URR, URM-25D, TS-403/U, TS-418/U, SP-600JX-17, CV-591A/URR, OS-8C/U, ALR-5, RCK, TT-98/FG, TT-107. Hundreds more available. Send 50¢ (coin) for list. W31HD, 4905 Roanne Drive, Washington, D. C. 20021.

WANTED: New or excellent AC power supply for National 200 transceiver. Charles Proffer, P. O. Box 206, Gulfport, Mississippi 39501.

RESISTORS: Carbon composition brand new. All standard values stocked. 1/2W 10% 50/\$1.00; 1/4W 10% 40/\$1.00 — 10 resistors per value please. Minimum order \$5.00. 15W RMS IC Audio Amplifier — Panasonic. Frequency response 20Hz-100kHz. 1/2% distortion. Price \$6.50. Postpaid. Pace Electronic Products, Box 161-H, Ontario Center, New York 14520.

THE FOURTEENTH ANNUAL HAMFEST, sponsored by the Southern Tier Amateur Radio Clubs, is scheduled for 2:00 p.m., April 14, 1973, at St. John's Ukrainian Hall, Johnson City, New York. Admission to lectures and flea market is free; awards and excellent dinner held to \$5.00. For tickets or further information, write STARC, P. O. Box 11, Endicott, N. Y. 13760. Advance ticket sales only by April 11, 1973.

WANTED: Magnetics specialist or college professor thoroughly familiar with conventional magnetic theory to assist the editor in evaluating a new concept in explaining magnetism. Write to Jim Fisk, WIDTY, editor, Ham Radio Magazine, Greenville, N. H. 03048.

THE GREATER BALTIMORE HAMBOREE will be held at Calvert Hall College, Putty Hill and Goucher Boulevard, Towson, Maryland (one mile south of Exit 28 of Beltway-Interstate 695), on Sunday, April 8, 1973 at 10 a.m. Food service, Flea market, prizes. Registration: \$2.00. No table or percentage charges. Info.: Joe Lochte, 5400 Roland Avenue, Baltimore, Maryland 21210.

STELMAN #TA-1 TELEPHONE ADAPTER, \$125. Heavy duty equipment slides \$15 ea. Components, equipment, etc. Inquiries invited. catalog available. B. F. Williams Co., P. O. #7057, Norfolk, Va. 23509.

HIGH-PERFORMANCE H.F. frequency synthesizer replaces VFO and delivers clean r.f. output with calibration accuracy, stability, and resolution 100 times better than the best amateur rigs of today. Write for full information. Petit Logic Systems, Box 51, Oak Harbor, Washington 98277.



bind'em and find'em

Bind your HAM RADIO'S with our handsome Ham Radio Binders then find the articles you want with our new 1968-72 Cumulative Index covering every article published in HAM RADIO from our first issue through December 1972.

Of course, if your shack is like ours you may have to find'em, bind'em and find it, but that's what this is all about. Get organized. Get maximum use from your HAM RADIO collection.

HAM RADIO GREENVILLE, NH 03048

Please send:

-Binders at \$4.50 ea.
-3 Binders for \$12.00
-Cumulative Index at \$1.00
-Super Package-5 Binders plus Index A \$23.50 value only \$18.50 (SAVE \$5.00)

Name..... Call.....

Address.....

Zip.....

NEW! FROM MATRIC

QUALITY GEAR

LOADED WITH FEATURES!



MODEL 10 • KEYER MODEL 11 • PADDLE

No bulky batteries or awkward power cords with the Model 10 Keyer. Internal penlight cells and reed relay output produce a compact, portable, and versatile unit. Also available as a circuit board kit without case for custom installation.

Keyer Kit	\$21.90
Keyer Assembled	\$26.50
P. C. Board Kit	\$12.95
Sidetone Kit	\$ 4.95
Sidetone Assembled	\$ 6.95
Paddle Assembled	\$ 9.95




MODEL 20 DIGITAL DIAL

Tune your fixed or mobile transmitter, receiver, or transceiver with 100 Hz accuracy and no last digit jitter. The Model 20 Digital Dial connects to rigs with 5-5.5 Mhz VFO's with a single wire. It can also be used as a general purpose frequency counter.

Matching accessories coming soon.

Assembled and Tested	\$169.95
Crystal Time Base	\$ 29.95

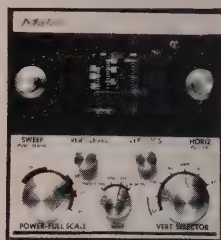

MODEL 31 MONITORSCOPE

Monitor RF output, read power output to 1500 watts, measure SWR to 3:1, and observe RTTY and trapezoid patterns all in a single instrument! The Model 31 also includes an RF actuated CW monitor, two-tone generator, and AC and DC vertical and horizontal inputs for general purpose use.


Assembled and Tested	\$169.95
----------------------------	----------

MATRIC

SEE YOUR DEALER OR ORDER DIRECT. PRICES F.O.B. SENeca, PA.

RD 1, PHONE LANE, BOX 185A • FRANKLIN, PA. 16323 • 814-432-3647

PRE-AMP

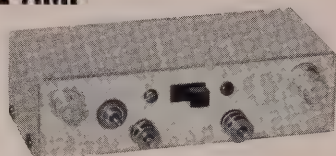

HIGH GAIN • LOW NOISE

35dB power gain, 2.5-3.0 dB N.F. at 150 MHz, 2 stage, R.F. protected, dual-gate MOSFETS. Manual gain control and provision for AGC. 4 3/8" x 1 7/8" x 1 3/8" aluminum case with power switch and choice of BNC or RCA phono connectors (be sure to specify). Available factory tuned to the frequency of your choice from 5 MHz to 350 MHz with approximately 3% bandwidth. Up to 10% B.W. available on special order.

N. Y. State residents add sales tax.

Model 201 price: 5-200 MHz \$24.95

201-350 MHz \$28.95

Vanguard Labs

196-23 JAMAICA AVE.
HOLLIS, N.Y. 11423

Many thousands of you have become very familiar with the various Radio Society of Great Britain books and handbooks, but very few of you are familiar with their excellent magazine, **Radio Communication**.

It includes numerous technical and construction articles in addition to a complete rundown on the month's events in amateur radio. Surely a most interesting addition to your amateur radio activities.

We can now offer this fine magazine to you along with the other advantages of membership in the RSGB (such as use of their outgoing QSL Bureau) for \$9.95 a year.

comtec

Greenville, New Hampshire 03048

USED MYLAR TAPES — 1800 foot. Ten for \$8.50 postpaid. Fremmerman, 4041 Central, Kansas City, Mo. 64111.

FOR SALE: SCR-522 transmitter and receiver. Like new, never modified or cannibalized. In storage since the late 1940s. Easily converted to six or two meters. This may be your last chance to buy a practically new, pristine BC-624 receiver and BC-615 transmitter. Complete conversion instructions will be furnished to buyer, on request. \$40.00, including shipping. Jim Fisk, WIDTY, Ham Radio, Greenville, NH 03048.

CERAMIC FEEDTHRU CAPACITORS, 1000 pf., solder-in type, 10 @ \$1.00. 1500 pf. ceramic feedthrus, bulkhead mount, 5 @ \$1.00. Ferrite Beads, 10 @ \$1.00. 3/4" ceramic coil forms, without slug, 10 @ \$1.00. 7-120 pf. square ceramic mica trimmer capacitors, 10 @ \$1.00. Postpaid. SASE for list. CPO Surplus, Box 189, Braintree, Massachusetts 02184.

HIGH GAIN microphone preamplifier kit. Easy assembly. Club and dealer discounts. S.A.S.E. for specifications. Superb VOX kit under development. USAT, P. O. Box 3051, Trenton, New Jersey 08619.

YAESU FTDX-560 transceiver, \$400. Heath SB-220 2KW amplifier, \$320. Heath IM-102 digital VOM, \$150. New TR-44 rotor, \$50. Hal keyboard keyer, \$75. Drake MN-4 matchbox, \$50. K4KY, 3853 Garden Terrace, Owensboro, Ky. 42301. (502) 683-9871.

TONE AND LOGIC circuit board layouts for WWV, RTTY, SSTV projects, systems. Two PCB samples, schematics, \$3.00. Hornung, Box 24614, San Jose, California 95154.

VIDEO ADAPTER converts oscilloscope into flexible 1024 letter RTTY readout for under \$400. Write for full information. Petit Logic Systems, Box 51, Oak Harbor, WA. 98277.

NEWS: Free sample copy of "Worldradio", Amateur Radio's Newspaper. 2509-C Donner Way, Sacramento, Calif. 95818.

GIVE ME FIVE MINUTES OF YOUR TIME: And I'll show you how to crack the computer code on those utility and charge card bills. Rush name, address and \$1.95 to Data Guide, P. O. Box 1205, Garland, Texas. 75040.

FOR SALE: HW100 w. AC/DC supplies \$225. West German 500W two-meter linear 4CX250B (new) \$350. Same for 432 MHz \$375. Andrews 4' dish \$25. Semco transistor VFO (48 MHz new) \$17.50. Hemco two-meter TX module (6330, new) \$25. Ingwersen, 352 Stillwater Ave., Spring Hill, Fla. 33512, (904) 683-2389.

RTTY SPEED CONVERTER. A drilled 4" x 6 1/2" PCB and all components except input output jacks, power supply and chassis. See Dec. '71 and Oct. '72 issue of Ham Radio. \$40.00 postpaid. PCB only \$6.00. P & M Electronics, Inc., 519 South Austin, Seattle, Washington 98108.


EVANSVILLE, INDIANA TARS HAMFEST, Sunday May 6, 1973. 4-H grounds, Hwy 41, north 3 miles. Auction, overnight camping, ladies bingo, reserved flea market booths, air conditioned. Advanced registration. For flyer contact Robby, W9MKZ, 502 S. Lincoln Park Drive, Evansville, Indiana 47714.

QSL'S — BROWNIE W3CJL — 3111B Lehigh, Allentown, Pa. 18103. Samples 10¢. Cat catalogue 25¢.

RID-O-RAY, America's best known electric bug killer. Safe, dependable design provides years of trouble free performance. S-15 for 1/4 acre \$89.95. Model D-15 for 3/4 acre \$109.95. Shipping paid East of Mississippi. West add \$5.00. 10% discount thru April 30th. Comtec, 140 Main St., Greenville, N. H. 03048.

YOUR AD belongs here too. Commercial ads 25¢ per word. Non-commercial ads 10¢ per word. Commercial advertisers write for special discounts for standing ads not changed each month.

The Satisfiers . . .

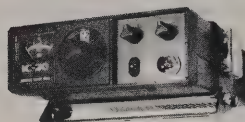

IC20 12 ch./10 watts
\$289.50 - 5 ch. supplied



IC21 24 ch./10 w.
AC & DC \$389.00
7 ch. spld base mobile

Inoue FM . . . The difference is in the Performance

Enjoy the difference in a really hot receiver that means results with the INOUE MOS/FET front end producing BETTER than .4uv/20db sensitivity.

You'll be able to forget about intermod and cross channel interference with INOUE'S unique combination of 5 helical resonators coupled with 2 I.F. filters.

Uniquely Inoue . . . Features that mean satisfaction to you

- **VERSATILITY** — Pick your power out with the High/Low power option, variable on the low position from .1 to 10 watts.
- **RUGGED DEPENDABILITY** — with exclusive modular construction. You can put your INOUE rig through rugged mobile-portable use, and count on it to keep on working. INOUE'S exclusive plug-in metal module construction frees you of the worry and frustrations of fragile single board construction.
- **ON-FREQUENCY ASSURANCE** — You can be sure you are on frequency with trimmer caps on both RX & TX for all channels, plus a built-in discriminator meter on the IC-21.
- **UNIQUE WARRANTY & SERVICING** — You'll keep your down time & service costs to a bare minimum with our 90 day warranty & module exchange program.

GET ON 2 FM NOW . . . AND DO IT RIGHT THE FIRST TIME . . . JOIN THE INOUE TEAM AND GET THE SATISFACTION YOU DESERVE FROM YOUR GEAR.

Drop us a line for more info. and the name of your nearest dealer. Dealers — Get in on the winning INOUE team, drop us a line or give us a call.

ICOM-EAST — a division of ACS

Box 331, Richardson, Texas 75080

Phone 214-235-0479

ICOM-WEST

1251 170th N.E., Bellevue, Wa. 98008

Phone 206-641-0554



ANG/GRR-5 RECEIVER

1.5 to 18MHz in 4 bands, AM, CW and MCW, continuous tuning & 10 preset frequency. 200 kHz crystal calibrator, 4" P.M. speaker, 12 tubes, with power supply for 115v. 50/60 cyc., 6, 12, or 24V. DC — Also dry cells 90 & 1.5 VDC. Size: 13 1/2" x 8 1/2" x 12 1/2". Shpg. wt.: 75 lbs. USED, repairable \$49.50

CHECKED \$59.50

Power Plug: \$2.00 Manual \$7.50

R-392 RECEIVER

— 500 kHz to 32 MHz, 32 bands, 25 tubes, 24/28 VDC. Size 11 1/2" x 14" x 11 1/2"; 70 lbs. USED, repairable \$295

Manual: \$8.50

Checked: \$350

All Prices F.O.B., Lima, Ohio — Dept. HR

SEND FOR OUR BIG NEW CATALOG

FAIR RADIO SALES


P.O. Box 1105 • LIMA, OHIO • 45802

W6SAI's RADIO HANDBOOK

WAS \$13.50

Now Just \$7.95

See Page 83

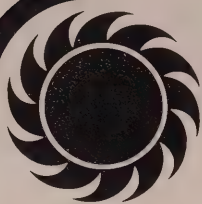

Go all the way into the REPEATER

There's nothing half-way about the new Hy-Gain REPEATER LINE.

Designed for the man who demands professional standards in 2 meter mobile equipment, the REPEATER LINE is the 2 meter HAM's dream come true. It's got everything you need for top performance...toughness, efficiency and the muscle to gain access to distant repeaters with ease. Reaches more stations, fixed or mobile, direct, without a repeater.

The right antennas for the new FM transceivers ...or any 2 meter mobile rig.

Rugged, high riding mobiles. Ready to go where you go, take what you dish out...and deliver every bit of performance your rig is capable of.

260 Commercial duty 1/4 wave, claw mounted roof top whip. Precision tunable to any discrete frequency 108 thru 470 MHz. 17-7 ph stainless steel whip.

261 Same as above. Furnished complete with 18' of coax and connector.

262 Rugged, magnetic mount whip. 108 thru 470 MHz. Great for temporary or semi-permanent no-hold installation. Holds secure to 100 mph. Complete with coax and connector. Base matching coil for 52 ohm match. 17-7 ph stainless steel whip.

260

261

262

2 meter mobile! with

LINE from hy-gain

263 Special no-hole trunk lip mount. 3 db gain. 130 thru 174 MHz. 5/8 wave. Complete with 16' coax. Operates at DC ground. Base matching coil for 52 ohm match. 17-7 ph stainless steel whip.

264 High efficiency, vertically polarized omnidirectional roof top whip. 3 db gain. Perfect 52 ohm match provided by base matching coil with DC ground. Coax and connector furnished.

265 Special magnetic mount. 3 db gain. Performance equal to permanent mounts. Holds at 90 mph plus. 12' of coax and connector. Base matching coil for 52 ohm match. 17-7 ph stainless steel whip. DC ground.


269 Rugged, durable, continuously loaded flexible VHF antenna for portables and walkie talkies. Completely insulated with special vinyl coating. Bends at all angles without breaking or cracking finish. Cannot be accidentally shorted out. Furnished with 5/16-32 base. Fits Motorola HT; Johnson; RCA Personafone; Federal Sign & Signal; and certain KAAR, Aerotron, Comco and Repco units.

Top performance for 2 meter mobiles
THE REPEATER LINE
from

HY-GAIN ELECTRONICS CORPORATION

BOX 5407-WD LINCOLN, NEBRASKA 68505


WRITE FOR DETAILS

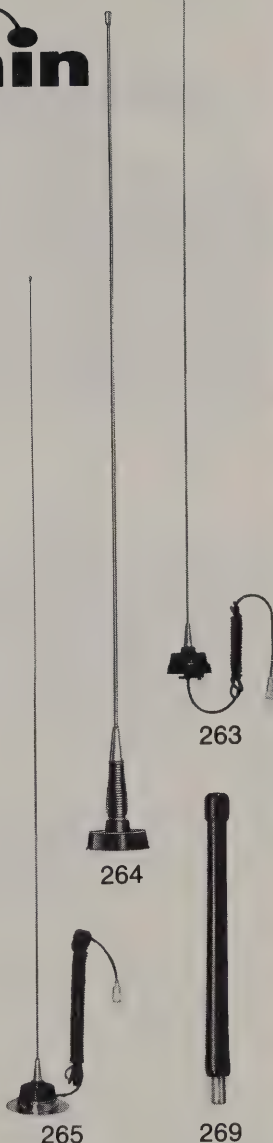

Semiconductor Supermart

• MOTOROLA • RCA • FAIRCHILD • NATIONAL • HEP • PLESSEY •

INTEGRATED CIRCUIT MICRO TRANSMITTER

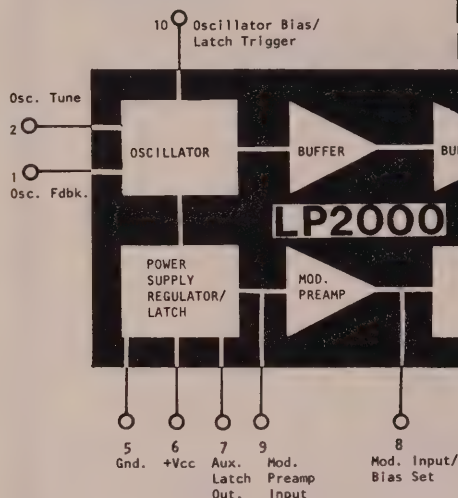

**SOMETHING NEW
FOR THE HAM
LITHIC SYSTEM'S
MICRO-
TRANSMITTER.
A COMPLETE AM
TRANSMITTER
INTEGRATED
CIRCUIT IN A
TO-5 CAN**

With just a few external components you can build a mini-mitter for 10 or 6 meters. Works with fundamental or over-tone xtals.

**Low introductory
price is only \$16.00**

ALSO FROM LITHIC SYSTEMS INTRODUCING **NEW!** DEVICES AT NEW LOW PRICES

LA3018 (Replaces CA3018)	\$1.60
LA3046 (Replaces CA3046)	\$1.60
LS370 (Replaces LM370)	\$4.00
LS1496 (Improved MC1496)	\$2.00
LS3028A (Replaces CA3028)	\$1.60
LP1000 (A new fun-type device to make LED flashers, audio osc, timer etc.)	\$1.60

NEW FAIRCHILD ECL HIGH SPEED DIGITAL IC's

9258 Dual "D" FF toggles beyond 160 MHz	\$4.65
9582 Multi-function gate & amplifier	\$3.15
95H90 300 MHz decade counter	\$16.00
A 95H90 & 9582 makes an excellent prescaler to extend low frequency counters to VHF — or use two 9528s for a 160 MHz prescaler.	

FETs

MPF102 JFET	.60
MPF105/2N5459 JFET	.96
MPF107/2N5486 JFET VHF/UHF	\$1.26
MPF121 Low-cost dual gate VHF RF	.85
MFE3007 Dual-gate	\$1.98
40673 Dual-gate	\$1.75
3N140 Dual-gate	\$1.95
3N141 Dual-gate	\$1.85

POPULAR IC's

MC1550	Motorola RF amp	\$1.80
CA3020	RCA 1/2 W audio	\$3.07
CA3020A	RCA 1 audio	\$3.92
CA3028A	RCA RF amp	\$1.77
CA3001	RCA	\$6.66
MC1306P	Motorola 1/2 W audio	\$1.10
MC1350P	High gain RF amp/IF amp	\$1.15
MC1357P	FM IF amp Quadrature det	\$2.25
MC1496	Hard to find Bal. Mod.	\$3.25
MFC9020	Motorola 2-Watt audio	\$2.50
MFC4010	Multi-purpose wide band amp	\$1.25
MFC8040	Low noise preamp	\$1.50
MC1303P	Dual Stereo preamp	\$2.75
MC1304P	FM multiplexer stereo demod	\$4.95

CORES AND BEADS

T200-2	\$2.00
KW Balun kit only	\$3.50
T68-2 3 cores	\$1.00
T50-2 3 cores	\$1.00
T50-6 3 cores	\$1.00
T50-10 3 cores	\$1.00
T44-10 3 cores	\$1.00

BEAD SPECIAL

Ferrite Beads 1 doz.	\$1.00
----------------------	--------

Please add 35¢ for shipping

Circuit Specialists

Box 3047H, Scottsdale, AZ 85257

FACTORY AUTHORIZED DISTRIBUTOR FOR
MOTOROLA HEP — CIRCUIT-STICK — PLESSEY
ALL DEVICES ARE FIRST QUALITY AND ARE
FULLY GUARANTEED.

KW107

It's beautiful!

\$134.95

SUPERMatch

Ppd in USA & Canada
Money back Guarantee

- * E-Z Match Tuner
- * SWR Meter
- * Power Meter
- * Dummy Load
- * Antenna Switch
- * 350 watts PEP

Clean up the unsightly tangle of wires around the shack and your wife will think it's beautiful



KW Electronics

10 Peru St., Plattsburgh, New York 12901
In Canada: 4544 Dufferin St.
Downsview, Ont. M3H 5S1

Send for FREE Literature

HAMFEST

WESTERN N. Y.
HAMFEST and
VHF CONFERENCE

MAY 12, 1973

Monroe County
Fairgrounds
Rt. 15A
Rochester, N. Y.
(Near Thruway Exit 46)

- Huge Flea Market
- Top Programs
- Award Presentations
- Banquet
- Friday Night Cocktails

WRITE:
WNY HAMFEST
BOX 1388
ROCHESTER, N. Y.
14603

400% MORE AVERAGE SSB POWER OUTPUT

USE A **MAGNUM SIX**
THE QUALITY R F SPEECH PROCESSOR



Collins-Heath	\$139.95
Drake T4X/T4XB	\$154.95
Drake TR4	\$159.95
Yaesu FT101	\$139.95
Kenwood TS699, TS-611	\$139.95
Add 5% Tax in Washington	

- 4 TIMES THE SSB POWER ON ALL BANDS
- ADDED PUNCH FOR PILE-UPS
- EXCELLENT VOICE QUALITY
- SPLATTER FREE, NARROW BAND OUTPUT SIGNAL
- SOLID STATE DESIGN
- PUT YOUR TRANSMITTER TO WORK FOR THE FIRST TIME IN ITS LIFE. POWER UP WITH A MAGNUM SIX FOR MORE ADDED POWER PER \$ THAN ANY OTHER METHOD!

Send for FREE Brochure
Communication Technology Group
31218 Pacific Highway South
Federal Way, Washington 98002



A Division of Bitcil Systems Inc.

Advertisers check-off

... for literature, in a hurry —
we'll rush your name to the companies
whose names you "check-off"

INDEX

—Amateur-Wholesale	—Janel
—Antenna Engineering	—Johnston
—Antenna King	—K-Enterprises
—Arizona	—K. E.
—Babylon	—KW
—B & W	—L. A.
—Barry	—Linear
—Bauman	—MFJ
—CFP	—MPQ
—CTG Bitcil	—Matric
—Camp Butler	—Meshna
—Caringella	—Miida
—Chronometric	—PM
—Circuit Specialists	—Palomar
—Command	—Peter Meacham
—Communications	—Poly Paks
—Specialists	—RP
—Communications	—Racom
—World	—Callbook
—Comtec	—Raytheon
—Curtis	—Rochester
—Cushcraft	—Sams
—Data	—Saroc
—Dayton	—Savoy
—Display	—Signal Systems
—Dycomm	—Solid State
—Ehrhorn	—Space-Military
—Eimac	—Spacetron
—E S P	—Spectronics, FM
—Fair	—Spectrum International
—Frank	—Star-Tronics
—Gateway	—Standard
—Gray	—Stoner-Goral
—H & L	—Structural Glass
—HAL	—Swan
—Ham Radio	—Tobel
—Heath	—VHF Engineering
—Henry	—Vanguard
—Hobby	—Weinschenker
—Hy-Gain	—Wolf
—Icom	—World QSL
—International Crystal	—Y & C
—Jan	

Limit 15 inquiries per request.

April 1973

Please use before May 31, 1973

Tear off and mail to
HAM RADIO MAGAZINE — "check off"
Greenville, N. H. 03048

NAME.....

CALL.....

STREET.....

CITY.....

STATE.....ZIP.....

Advertisers iNdex

ATV Research	89
Amateur-Wholesale Electronics	90
Antenna King	56
Arizona Semi-Conductor	84
Babylon Electronics	89
Barker & Williamson, Inc.	84
Barry	89
Bauman, R. H. Sales	94
CFP Enterprises	86
CTG Bitcil	109
Camp Albert Butler	84
Caringella Electronics	81
Chronometric Products	92
Circuit Specialists Co.	108
Command Productions	101
Communications Specialists	96
Communications World, Inc.	66
Comtec	82, 83, 104, 105
Curtis	96
Cushcraft	101
Data Engineering, Inc.	40, 41
Dayton Hamvention	94
Display Electronics	101
Dycomm	94
Ehrhorn Technological Operations, Inc.	1
Eimac, Div. of Varian Assoc.	Cover IV
Emporium Sounds of Pompano	76
Fair Radio Sales	105
Frank Electronics	96
G & G Radio Supply Co.	90
Gateway Electronics	80
Goodheart Co., Inc. R. E.	96
Gray Electronics	86
H & L Associates	92
HAL Communications Corp.	91
Ham Radio	87, 103
Heath Company	2, 46, 47
Henry Radio Stores	Cover III
Hobby Industry	75
Hy-Gain Electronics Corp.	26, 27, 106, 107
Icom	105
International Crystal Mfg. Co. Inc.	112
Jan Crystals	90
Janel Labs	89
K-Enterprises	96
K. E. Electronics	92
KW Electronics	109
L. A. Electronix Sales	111
Linear Systems, Inc.	85
MFJ Enterprises	92
MPQ	94
Matric	104
Meshna, John, Jr.	84
Miida Electronics	93
PM Electronics, Inc.	66
Palomar Engineers	80
Payne Radio	78
Peter Meacham Associates	101
Poly Paks	98
RP Electronics	76
Racom Electronics, Inc.	89
Radio Amateur Callbook	81, 96
Raytheon Company	5
Rochester Hamfest	109
Sams, Howard W. and Co., Inc.	100
Saroc	86
Savoy Electronics	Cover II
Signal Systems	92
Solid State Systems, Inc.	102
Space-Military Electronics	101
Spectronics, FM	95
Spectrum International	77
Star-Tronics	86
Standard Communications Corp.	97
Structural Glass	67
Swan Electronics	37
VHF Engineering	86
Vanguard Labs	104
Weinschenker, M.	79
Wolf, S.	90
World QSL Bureau	96
Y & C Electronics	78

BONUS THE BEST ANTENNA PACKAGES YET!


**OPTIMUM PERFORMANCE
GUARANTEED SAVINGS**



ALL NEW, engineered for optimum performance with TRI-EX's Certified* Antenna Towers & HY-GAIN's TOP Performance Antennas. The utmost in craftsmanship and construction for your satisfaction. . . .

Local Bank Financing - 15% Down or Trade-In Down - Good Reconditioned Equipment. Nearly all makes and models. Our reconditioned equipment carries a 30 day warranty and may be traded back within 90 days for full credit toward the purchase of NEW equipment. Inquiries invited.

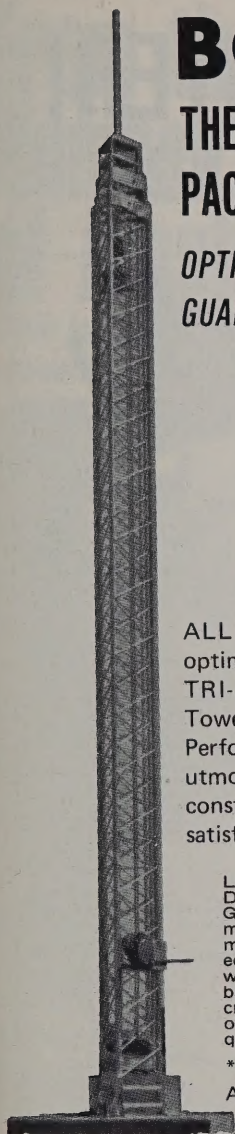* Certified Welders & Approved by L.A. City



W51 SHOWN

LAE MW35 "STANDARD" Package
(Free Standing Crank-Up Tower
9.5 Sq. Ft. - 50 MPH) (35 Ft.)

CDR AR-22R Rotator*

100 ft. RG-58A/U Coax

100 ft. 4 Cond. rotor cable

Complete with one of the following antennas:

HY-GAIN TH2MK3	\$290
HY-GAIN TH3JR	\$290
HY-GAIN DB10-15A	\$299
HY-GAIN HY QUAD	\$329
HY-GAIN TH3MK3	\$339

*TR-44 rotor w/cable add: \$ 35
HAM-M rotor w/cable add: \$ 65

LAE W51 "DELUXE" 51 Ft. Package
(Free Standing, 9 Sq. Ft. - 50 MPH)

CDR TR-44 rotor*

100 ft. RG58A/U coax cable

100 ft. control cable

Complete with one of the following antennas:

HY-GAIN DB 10-15A	\$620
HY-GAIN HY QUAD	\$650
HY-GAIN 204BA	\$660
HY-GAIN TH3MK3	\$655
HY-GAIN TH6DXX	\$675

Free stdg. base incld. NO/CHARGE

*HAM-M rotor w/RG8/U add: \$ 60

LAE LM354 "SUPER" 54 Ft. Package
(16 Sq. Ft. - 60 MPH)

CDR HAM-M Rotor

100 ft. RG8/U coax cable


100 ft. control cable

Complete with one of the following antennas:

HY-GAIN TH3MK3	\$835
HY-GAIN 204BA	\$839
HY-GAIN TH6DXX	\$860

Freight PREPAID to your door in the Continental USA west of the Rockies. For shipment east of the Rockies, add \$15.00. Substitutions may be made. . . write for prices.

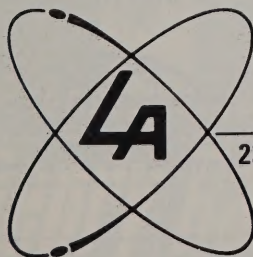"WEST COAST'S FASTEST GROWING AMATEUR RADIO DISTRIBUTOR"
"WE SELL ONLY THE BEST"



Electronix Sales


23044 S. CRENSHAW BLVD., TORRANCE, CALIF. 90505

Phone: (213) 534-4402

HOME of LA AMATEUR RADIO SALES


for the EXPERIMENTER!

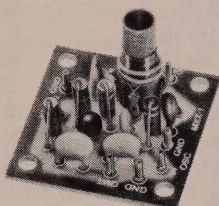INTERNATIONAL EX CRYSTAL & EX KITS OSCILLATOR • RF MIXER • RF AMPLIFIER • POWER AMPLIFIER



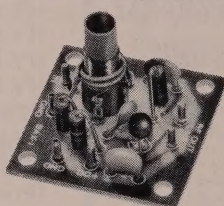
1. MXX-1 TRANSISTOR RF MIXER

A single tuned circuit intended for signal conversion in the 3 to 170 MHz range. Harmonics of the OX oscillator are used for injection in the 60 to 170 MHz range. Lo Kit 3 to 20 MHz, Hi Kit 20 to 170 MHz (Specify when ordering).....\$3.50



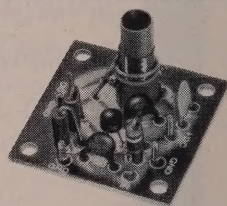
2. SAX-1 TRANSISTOR RF AMP

A small signal amplifier to drive MXX-1 mixer. Single tuned input and link output. Lo Kit 3 to 20 MHz, Hi Kit 20 to 170 MHz (Specify when ordering).....\$3.50



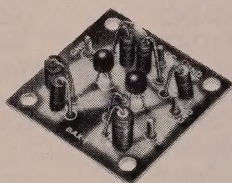
3. PAX-1 TRANSISTOR RF POWER AMP

A single tuned output amplifier designed to follow the OX oscillator. Outputs up to 200 mw, depending on the frequency and voltage. Amplifier can be amplitude modulated. Frequency 3,000 to 30,000 KHz.....\$3.75



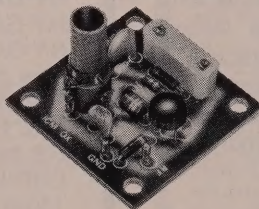4. BAX-1 BROADBAND AMP

General purpose unit which may be used as a tuned or untuned amplifier in RF and audio applications 20 Hz to 150 MHz. Provides 6 to 30 db gain. Ideal for SWL, Experimenter or Amateur\$3.75



5. OX OSCILLATOR

Crystal controlled transistor type. Lo Kit 3,000 to 19,999 KHz, Hi Kit 20,000 to 60,000 KHz. (Specify when ordering).....\$2.95



6. TYPE EX CRYSTAL

Available from 3,000 to 60,000 KHz. Supplied only in HC 6/U holder. Calibration is $\pm .02\%$ when operated in International OX circuit or its equivalent. (Specify frequency)\$3.95

for the COMMERCIAL user...

INTERNATIONAL PRECISION RADIO CRYSTALS

International Crystals are available from 70 KHz to 160 MHz in a wide variety of holders. Crystals for use in military equipment can be supplied to meet specifications MIL-C-3098E.

CRYSTAL TYPES: (GP) for "General Purpose" applications
(CS) for "Commercial Standard"
(HA) for "High Accuracy" close temperature tolerance requirements.




write for
CATALOG



CRYSTAL MFG. CO., INC.
10 NO. LEE • OKLA. CITY, OKLA. 73102

From the World's Number One Manufacturer of Amplifiers

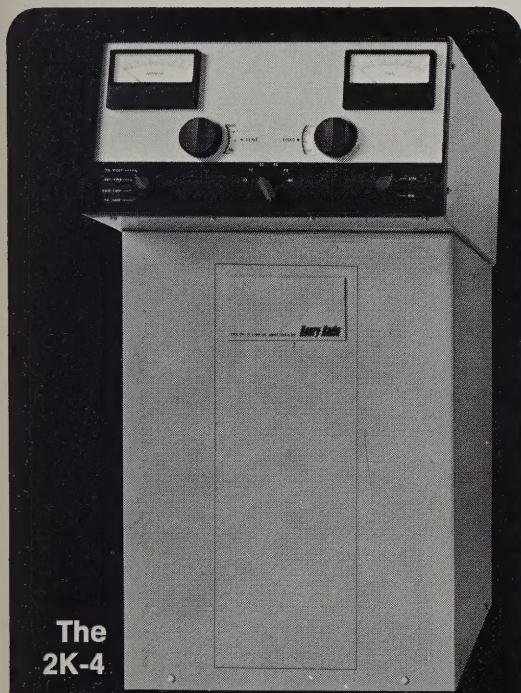The biggest, broadest, finest line of amateur
power amplifiers



The
2K-4



The
2K-ULTRA

2K-4... THE "WORKHORSE"

The 2K-4 linear amplifier offers engineering, construction and features second to none, and at a price that makes it the best amplifier value ever offered to the amateur. Constructed with a ruggedness guaranteed to provide a long life of reliable service, its heavy duty components allow it to loaf along even at full legal power. If you want to put that strong clear signal on the air that you've probably heard from other 2K users, now is the time. Move up to the 2K-4. Floor console or desk model... \$845.00

2K-ULTRA... THE "ULTIMATE"

There has never been an amateur linear amplifier like the new 2K-ULTRA. Small and lightweight, yet rugged and reliable... all that the name implies. The ULTRA loafs along at full legal power without even the sound of a blower. Its anode heat is silently and efficiently conducted to a heat sink through the use of a pair of Eimac 8873 tubes. In fact, all of its components are the very best obtainable. The price... \$845.00

TEMPO/2001

Small but powerful, reliable but inexpensive, this amplifier is another top value from Henry Radio. Using two 8874 grounded grid triodes from Eimac, the Tempo 2001 offers a full kilowatt of power for SSB operation in an unbelievably compact package (total volume is .8 cu. ft.). The 2001 has a built-in solid state power supply, a built-in antenna relay, and built-in quality to match much more expensive amplifiers. This equipment is totally compatible with the Tempo One as well as most other amateur transceivers. Completely wired and ready for operation, the 2001 includes an internal blower, a relative RF power indicator, and full amateur band coverage from 80-10 meters. \$545.00

TEMPO/6N2

The Tempo 6N2 combines most of the fine features of the 2001 for 6 and 2 meter amateur operation. The amplifier uses the same small cabinet, the same modern tubes, the same inherent quality for 2000 watts PEP input on SSB or 1000 watts input on FM or CW. The rig is completely wired in one small package with an internal solid-state power supply, built-in blower, and RF relative power indicator. \$595.00

3K-A COMMERCIAL/MILITARY AMPLIFIER


A high quality linear amplifier designed for commercial and military uses. The 3K-A employs two rugged Eimac 3-500Z grounded grid triodes for superior linearity and provides a conservative three kilowatts PEP input on SSB with efficiencies in the range of 60%. This results in PEP output in excess of 2000 watts. In addition, the 3K-A provides a heavy duty power supply capable of furnishing 2000 watts of continuous duty input for either RTTY or CW with 1200 watts output. Price... \$1080.00

Prices subject to change without notice

Henry Radio

"World's Largest Distributor of Amateur Radio Equipment"

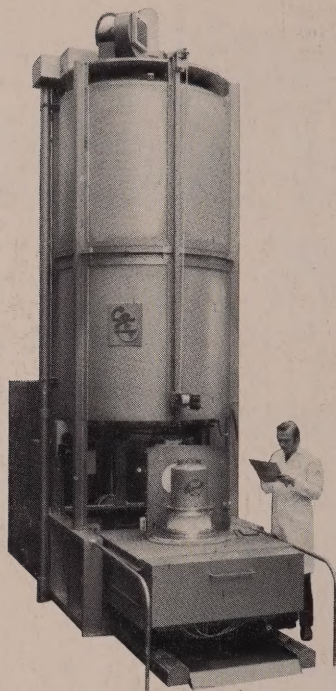11240 W. Olympic Blvd., Los Angeles, Calif. 90064 213/477-6701
931 N. Euclid, Anaheim, Calif. 92801 714/772-9200
Butler, Missouri 64730 816/679-3127



This is the world's most powerful shortwave transmitter.

This compact, single tube amplifier, located in the EIMAC facility, develops over 1300 kilowatts of 100% modulated carrier. It is quickly and easily tunable over the range of 15 to 30 MHz. Drive power at the grid of the tube is less than 5 kilowatts.

Using a single EIMAC X-2159 super-power tetrode in a Continental Electronics transmission line-cavity configuration, this amplifier combines high power gain with excellent operating stability and complete freedom from circuit parasitics.

A single amplifier stage using two EIMAC X-2159 tubes is capable of over 2.5 megawatts of 100% modulated

carrier. Two amplifiers combined would make a 5 megawatt transmitter a practical reality.

The EIMAC X-2159 super-power tetrode is designed for MF and HF broadcast service, VLF communications, SSB linear service and extremely high power pulse modulator applications.

The X-2159 is another example of tomorrow's tube that's ready today at EIMAC. For complete information, contact EIMAC Division of Varian, 301 Industrial Way, San Carlos, California 94070. Or any of the more than 30 Varian/EIMAC Electron Tube and Device Group Sales Offices throughout the world.

